

# AN10881

## TEA1713 resonant power supply control IC with PFC

Rev. 2 — 26 September 2011

Application note

### Document information

Info	Content
<b>Keywords</b>	TEA1713, adapter, LCD TV, Plasma TV, resonant, converter, PFC, Burst mode
<b>Abstract</b>	<p>The TEA1713 integrates a controller for Power Factor Correction (PFC) and a controller for a half-bridge resonant converter (HBC).</p> <p>It provides the drive function for the discrete MOSFET for the up-converter and for the two discrete power MOSFETs in a resonant half-bridge configuration.</p> <p>The resonant controller part is a high-voltage controller for a zero voltage switching LLC resonant converter. The resonant controller part of the IC includes a high-voltage level shift circuit and several protection features such as overcurrent protection, open-loop protection, Capacitive mode protection and a general purpose latched protection input.</p> <p>In addition to the resonant controller, the TEA1713 also contains a Power Factor Correction (PFC) controller. The efficient operation of the PFC is obtained by functions such as quasi-resonant operation at high power levels and quasi-resonant operation with valley skipping at lower power levels. Overcurrent protection, overvoltage protection and demagnetization sensing, ensures safe operation in all conditions.</p> <p>The proprietary high-voltage BCD Powerlogic process makes direct start-up possible from the rectified universal mains voltage in an efficient way. A second low voltage Silicon-On-Insulator (SOI) IC is used for accurate, high speed protection functions and control.</p> <p>The combination of PFC and a resonant controller in one IC makes the TEA1713 suitable for power supplies in LCD TV, plasma televisions, PC power supplies, high-power office equipment and adapters.</p> <p>This application note discusses the TEA1713 functions for applications.</p>



Table 1. Revision history

Rev	Date	Description
02	20110926	Second, updated release
01	20100322	First release

## Contact information

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: [salesaddresses@nxp.com](mailto:salesaddresses@nxp.com)

## 1. Introduction

### 1.1 Scope and setup

This application note discusses the TEA1713 functions for applications in general. Because the TEA1713 provides extensive functionality, many subjects are discussed.

This document is set up in such a way, that a chapter or paragraph of a selected subject can be read as a standalone explanation with a minimum of cross-references to other document parts or the data sheet. This leads to some repetition of information within the application note and to descriptions or figures that are similar to those published in the TEA1713 data sheet. In most cases typical values are given to enhance the readability.

- [Section 1 “Introduction”](#)
- [Section 2 “TEA1713 highlights and features”](#)
- [Section 3 “Pin overview with functional description”](#)

An overview of the TEA1713 pins with a summary of the functionality.

- [Section 4 “Application diagram and block diagrams”](#)
- [Section 5 “Supply functions”](#)

Sections 6, 7, 8, 9, and 10 describe the main functions of the TEA1713, providing an in-depth explanation of the issues relating to the subject. The functions are written from an application point of view.

- [Section 6 “MOSFET drivers GATEPFC, GATELS and GATEHS”](#)
- [Section 7 “PFC functions”](#)
- [Section 8 “HBC functions”](#)
- [Section 9 “Burst mode operation”](#)
- [Section 10 “Protection functions”](#)

An overview of the protection functions of the TEA1713 with an extended explanation and related issues on the subject. These functions are described and seen from an applications point of view.

- [Section 11 “Miscellaneous advice and tips”](#)

A collection of subjects related to PCB design and debugging are discussed, including proposals for the way of working.

- [Section 12 “Application examples and topologies”](#)

This section contains examples of applications (circuit diagrams) and possible topologies.

- [Section 13 “Differences between TEA1713T and TEA1713LT”](#)

An overview of the differences between the TEA1713T and the TEA1713LT.

**Remark:** All values provided throughout this document are typical values unless otherwise stated.

## 1.2 Related documents

Additional information and tools can be found in other TEA1713 documents such as:

- Data sheet
- User manual of demo board
- Calculation sheet

## 2. TEA1713 highlights and features

### 2.1 Resonant conversion

Today's market demands high-quality, reliable, small, lightweight and efficient power supplies.

In principle, the higher the operating frequency, the smaller and lighter the transformers, filter inductors and capacitors can be. On the other hand, the core, switching and winding losses of the transformer increase at higher frequencies and become dominant. This effect reduces the efficiency at a high frequency, which limits the minimum size of the transformer.

The corner frequency of the output filter usually determines the bandwidth of the control loop. A well-chosen corner frequency allows high operating frequencies to achieve a fast dynamic response.

Pulse Width Modulated (PWM) power converters, such as flyback, up and down converters, are widely used in low and medium power applications. A disadvantage of these converters is that the PWM rectangular voltage and current waveforms cause turn-on and turn-off losses that limit the operating frequency. The rectangular waveforms also generate broadband electromagnetic energy that can produce ElectroMagnetic Interference (EMI).

A resonant DC-to-DC converter produces sinusoidal waveforms and reduces the switching losses, which provide the possibility of operation at higher frequencies.

Recent environmental considerations have resulted in a need for high efficiency performance at low loads. Burst mode operation of the resonant converter can provide this if the converter is required to remain active as is the case for adapter applications.

Why resonant conversion?

- High power
- High efficiency
- EMI friendly
- Compact

### 2.2 Power factor correction conversion

Most switch mode power supplies result in a non-linear impedance (load characteristic) to the mains input. Current taken from the mains supply occurs only at the highest voltage peaks and is stored in a large capacitor. The energy is taken from this capacitor storage, in accordance with the switch mode power supply operation characteristics.

Government regulations dictate special requirements for the load characteristics of certain applications. Two main requirements can be distinguished:

- Mains harmonics requirements EN61000-3-2
- Power factor (real power/apparent power)

The requirements work towards a more resistive characteristic of the mains load.

Measures are required regarding the input circuit of the power supply to fulfill these requirements. Passive (often a series coil) or active (often a boost converter) circuits can be used to modify the mains load characteristics accordingly.

An additional market requirement for the added mains input circuit is that it works with a good efficiency and have a low cost.

Using a boost converter to meet these requirements provides the benefit of a fixed DC input voltage when combined with a resonant converter. The fixed input voltage provides easier design of the resonant converter (specially for wide mains input voltage range applications) and the possibility to reach a higher efficiency.

## 2.3 TEA1713 resonant power supply control IC with PFC

The TEA1713 integrates two controllers, one for Power Factor Correction (PFC) and one for a half-bridge resonant converter (HBC). It provides the drive function for the discrete MOSFET for the up-converter and for the two discrete power MOSFETs in a resonant half-bridge configuration.

The resonant controller part is a high-voltage controller for a zero voltage switching LLC resonant converter.

The resonant controller part of the IC includes a high-voltage level shift circuit and several protection features such as overcurrent protection, open-loop protection, Capacitive mode protection and a general purpose latched protection input.

In addition to the resonant controller, the TEA1713 also contains a Power Factor Correction (PFC) controller. The efficient operation of the PFC is obtained by functions such as quasi-resonant operation at high power levels and quasi-resonant operation with valley skipping at lower power levels. Overcurrent protection, overvoltage protection and demagnetization sensing ensures safe operation in all conditions.

The proprietary high-voltage BCD Powerlogic process makes direct start-up possible from the rectified universal mains voltage in an efficient way. A second internal low-voltage SOI die is used for accurate, high-speed protection functions and control.

The topology of a PFC and a resonant converter controlled by the TEA1713 is flexible and enables a broad range of applications for wide input (85 V to 264 V) AC mains voltages. The combination of PFC and resonant controller in one IC makes the TEA1713 suitable for compact power supplies with a high level of integration and functionality.

## 2.4 Features

### 2.4.1 General features

- Integrated power factor controller and resonant controller
- Universal mains supply operation
- High level of integration, resulting in a low external component count and a cost effective design
- Enable input. Also allows enabling of PFC only
- On-chip high-voltage start-up source
- Standalone operation or IC supply from external DC supply

### 2.4.2 Power factor controller features

- Boundary mode operation with on-time control for highest efficiency
- Valley/zero voltage switching for minimum switching losses
- Frequency limitation to reduce switching losses
- Accurate boost voltage regulation
- Burst mode switching with soft-start and soft-stop

### 2.4.3 Resonant half-bridge controller features

- Integrated high-voltage level shifter
- Adjustable minimum and maximum frequency
- Maximum 500 kHz half-bridge switching frequency
- Adaptive non-overlap timing
- Burst mode switching

### 2.4.4 Protection features

- Safe restart mode for system fault conditions
- General latched protection input for output overvoltage protection or external temperature protection
- Protection timer for time-out and restart
- OverTemperature Protection (OTP)
- Soft (re)start for both converters
- Undervoltage protection for mains (brownout), boost, IC supply and output voltage
- Overcurrent regulation and protection for both converters
- Accurate overvoltage protection for boost voltage
- Capacitive mode protection for resonant converter

## 2.5 Protection

The TEA1713 provides several protection functions that combine detection with a response to solve the problem. By regulating the frequency as a reaction to, for example, overpower or bad half-bridge switching, the problem can be solved or operation kept safe until it is decided to stop and restart (timer function).

## 2.6 Typical areas of application

- LCD television
- Plasma television
- High-power adapters
- Slim notebook adapters
- PC power supplies
- Office equipment

### 3. Pin overview with functional description

Table 2. Pinning overview

Pin	Name	Functional description
1	COMPPFC	<p>Frequency compensation for the PFC control-loop. Externally connected filter with typical values: 150 nF (33 k<math>\Omega</math> + 470 nF)</p>
2	SNSMAINS	<p>Sense input for mains voltage. Externally connected to resistive divided mains voltage. This pin has four functions:</p> <ul style="list-style-type: none"> <li>• Mains enable level: <math>V_{\text{start(SNSMAINS)}} = 1.15 \text{ V}</math></li> <li>• Mains stop level (brownout): <math>V_{\text{stop(SNSMAINS)}} = 0.9 \text{ V}</math></li> <li>• Mains-voltage compensation for the PFC control-loop gain bandwidth</li> <li>• Fast latch reset: <math>V_{\text{rst(SNSMAINS)}} = 0.75 \text{ V}</math></li> </ul> <p>The mains enable and mains stop level enable and disable the PFC. Enabling and disabling of the resonant controller is based on the voltage on SNSBOOST. The voltage on the SNSMAINS pin must be an averaged DC value, representing the AC line voltage. Do not use the pin for sensing the phase of the mains voltage. Open pin detection is included by an internal current source (33 nA).</p>
3	SNSAUXPFC	<p>Sense input from an auxiliary winding of the PFC coil for demagnetization timing and valley detection to control the PFC switching. It is <math>-100 \text{ mV}</math> level with a time-out of 50 <math>\mu\text{s}</math>. Connect the auxiliary winding via an impedance to the pin (recommended is a 5.1 k<math>\Omega</math> series resistor) to prevent damage of the input during surges (e.g. lightning). Open pin detection is included by an internal current source (33 nA).</p>
4	SNSCURPFC	<p>Current sense input for PFC. This input is used to limit the maximum peak-current in the PFC core. The PFCSENSE is a cycle-by-cycle protection. The PFC MOSFET is switched off when the level reaches 0.5 V. The internal logic controls a 60 <math>\mu\text{A}</math> internal current source connected to the pin. This current source is used to implement a soft-start and soft-stop function for the PFC to prevent audible noise in Burst mode. The pin is also used to enable the PFC. The PFC only starts when the internal current source (60 <math>\mu\text{A}</math>) is able to charge the soft-start capacitor to a voltage of 0.5 V. A minimum soft-start resistor of 12 k<math>\Omega</math> is required to guarantee enabling of the PFC. The value of the capacitor on SNSCURPFC provides the soft-start and soft-stop timing in combination with the parallel resistor value.</p>
5	SNSOUT	<p>Input for indirectly sensing the output voltage of the resonant converter. It is normally connected to an auxiliary winding of HBC and is also an input for the Burst mode of HBC or PFC + HBC. This pin has four functions related to internal comparators:</p> <ul style="list-style-type: none"> <li>• Overvoltage protection: <math>\text{SNSOUT} &gt; 3.5 \text{ V}</math>, latched</li> <li>• Undervoltage protection: <math>\text{SNSOUT} &lt; 2.3 \text{ V}</math>, protection timer</li> <li>• Hold HBC: <math>\text{SNSOUT} &lt; 1.0 \text{ V}</math>, stop switching HBC (Burst mode)</li> <li>• Hold HBC + PFC: <math>\text{SNSOUT} &lt; 0.4 \text{ V}</math>, stop switching HBC and PFC (Burst mode)</li> </ul> <p>The pin also contains an internal current source of 100 <math>\mu\text{A}</math> that, initially, generates a voltage up to 1.5 V across an external impedance (<math>&gt; 20 \text{ k}\Omega</math> recommended) to avoid unintended Burst mode operation.</p>

Table 2. Pinning overview ...continued

Pin	Name	Functional description
6	SUPIC	<p>IC voltage supply input and output of the internal HV start-up source.</p> <p>All internal circuits are directly or indirectly (via SUPREG) supplied from this pin, except for the high-voltage circuit.</p> <p>The buffer capacitor on SUPIC can be charged in several ways:</p> <ul style="list-style-type: none"> <li>• Internal High-Voltage (HV) start-up source</li> <li>• Auxiliary winding from HBC transformer or capacitive supply from switching half-bridge node</li> <li>• External DC supply, for example a standby supply</li> </ul> <p>The IC enables operation when the SUPIC voltage has reached the start level of 22 V (for HV-start) or 17 V (for external supply). It stops operation below 15 V and a shutdown reset is activated at 7 V.</p>
7	GATEPFC	Gate driver output for PFC MOSFET.
8	PGND	Power ground. Reference (ground) for HBC low-side and PFC driver.
9	SUPREG	<p>Output of the internal regulator: 10.9 V.</p> <p>Internal IC functions such as the MOSFET drivers use the supply created by this function . It can also be used to supply an external circuit.</p> <p>SUPREG can provide a minimum of 40 mA.</p> <p>SUPREG becomes operational after SUPIC has reached its start level.</p> <p>The IC starts full operation when SUPREG has reached 10.7 V.</p> <p>UVP: If SUPREG drops below 10.3 V after start, the IC stops operating and the current from SUPIC is limited to 5.4 mA, to allow recovery.</p>
10	GATELS	Gate driver output for low side MOSFET of HBC.
11	n.c.	Not connected, high-voltage spacer.
12	SUPHV	<p>High-voltage supply input for internal HV start-up source.</p> <p>In a standalone power supply application, this pin is connected to the boost voltage. SUPIC and SUPREG are charged with a constant current by the internal start-up source. SUPHV operates at a voltage above 25 V.</p> <p>Initially the charging current is low (1.1 mA). When the SUPIC exceeds the short circuit protection level of 0.65 V, the generated current increases to 5.1 mA. The source is switched off when SUPIC reaches 22 V which initiates a start operation. During start operation, an auxiliary supply takes over the supply of SUPIC. If the takeover is not successful, the SUPHV source is reactivated and a restart is made (SUPIC below 15 V).</p>
13	GATEHS	Gate driver output for high-side MOSFET of HBC.
14	SUPHS	High-side driver supply connected to an external bootstrap capacitor between HB and SUPHS. The supply is obtained using an external diode between SUPREG and SUPHS.
15	HB	<p>Reference for the high-side driver GATEHS.</p> <p>It is an input for the internal half-bridge slope detection circuit for adaptive non-overlap regulation and Capacitive mode protection. It is externally connected to a half-bridge node between the MOSFETs of HBC.</p>
16	n.c.	Not connected, high-voltage spacer.

Table 2. Pinning overview ...continued

Pin	Name	Functional description
17	SNSCURHBC	<p>Sense input for the momentary current of the HBC. If the voltage level (that represents the primary current) becomes too high, internal comparators determine the regulation to a higher frequency (SNSCURHBC = <math>\pm 0.5</math> V) or protect (SNSCURHBC = <math>\pm 1</math> V) by switching immediately to maximum frequency.</p> <p>The provided additional current from SNSCURHBC can compensate variations at protection level, caused by HBC input voltage variations. This current leads to a voltage offset across the external series resistance value. The current measurement resistor and an extra series resistance, which has a typical value of 1 k<math>\Omega</math>, normally provide this series resistance .</p>
18	SGND	Signal ground, reference for IC.
19	CFMIN	<p>Oscillator pin.</p> <p>The value of the external capacitor determines the minimum switching frequency of the HBC. In combination with the resistor value on RFMAX, it sets the operating frequency range.</p> <p>A triangular waveform is generated on the CFMIN capacitor (<math>V_{\text{low(CFMIN)}} = 1</math> V and <math>V_{\text{high(CFMIN)}} = 3</math> V) to facilitate switching timing. A fixed minimum (dis)charging current of 150 <math>\mu\text{A}</math> determines the minimum frequency. During special conditions, the (dis)charging current is reduced to 30 <math>\mu\text{A}</math> to slow down the charging temporarily.</p> <p>An internal function limits the operating frequency to 670 kHz.</p>
20	RFMAX	<p>Oscillator frequency pin.</p> <p>The value of the resistor connected between this pin and ground, determines the frequency range. Both the minimum and maximum frequencies of the HBC are preset. CFMIN sets the minimum frequency. The absolute maximum frequency is internally limited to 670 kHz.</p> <p>The voltage on RFMAX and the value of the resistor connected to it, determine the variable part (in addition to the fixed 150 <math>\mu\text{A}</math>) of the (dis)charging current of the CFMIN capacitor. The voltage on RFMAX can vary between 0 V (minimum frequency) and 2.5 V (maximum frequency).</p> <p>SNSFB and the SSHBC/EN function drive the RFMAX voltage (running frequency).</p> <p>The protection timer is started when the voltage level is above 1.88 V. An error is assumed when the HBC is operating at high frequency for a longer time.</p>
21	SNSFB	<p>Sense input for HBC output regulation feedback by voltage.</p> <p>Sinking a current from SNSFB creates the feedback voltage on SNSFB. The regulation voltage is produced by feeding this current through a 1.5 k<math>\Omega</math> internal resistor which is internally connected to 8.4 V.</p> <p>The regulation voltage range is from 4.1 V to 6.4 V. It corresponds with the maximum and minimum frequencies that are controlled by SNSFB. The SNSFB range is limited to 65 % of the maximum frequency preset by RFMAX.</p> <p>The provision of open-loop detection activates the protection timer when SNSFB exceeds 7.7 V.</p>

Table 2. Pinning overview ...continued

Pin	Name	Functional description
22	SSHBC/EN	<p>Combined soft-start/protection frequency control of HBC and IC enable input (PFC or PFC + HBC). Externally connected to a soft-start capacitor and an enable pull-down function.</p> <p>This pin has three functions:</p> <ul style="list-style-type: none"> <li>• Enable PFC (&gt; 1 V) and PFC + HBC (&gt; 2 V)</li> <li>• Frequency sweep during soft-start from 3.2 V to 8 V</li> <li>• Frequency control during protection between 8 V to 3.2 V</li> </ul> <p>Seven internal current sources operate the frequency control, depending on which one of the following actions is required:</p> <ul style="list-style-type: none"> <li>• Soft-start + OverCurrent Protection: high/low charge (160 <math>\mu</math>A/40 <math>\mu</math>A) + high/low discharge (160 <math>\mu</math>A/40 <math>\mu</math>A)</li> <li>• Capacitive mode regulation: high/low discharge (1800 <math>\mu</math>A/440 <math>\mu</math>A)</li> <li>• General: bias discharge (5 <math>\mu</math>A)</li> </ul>
23	RCPROT	<p>Timer presetting for time-out and restart. The values of an externally connected resistor and capacitor determine the timing.</p> <p>A 100 <math>\mu</math>A charge current activates the timer during certain protection events:</p> <ul style="list-style-type: none"> <li>• Overcurrent regulation (SNSCURHBC)</li> <li>• High-frequency protection (RFMAX)</li> <li>• Open-loop protection (SNSFB)</li> <li>• Undervoltage protection (SNSOUT)</li> </ul> <p>When the level of 4 V is reached the protection is activated. The resistor discharges the capacitor and at a level of 0.5 V, a restart is made.</p> <p>If an SCP (SNSBOOST) occurs, the RCPROT capacitor is quickly charged by 2.2 mA. After it reaches the 4 V level, the capacitor is discharged after which a new start is initiated.</p>
24	SNSBOOST	<p>Sense input for boost voltage regulation (output voltage of the PFC stage). It is externally connected to a resistive divided boost voltage.</p> <p>This pin has four functions:</p> <ul style="list-style-type: none"> <li>• Pin SNSBOOST short detection: <math>V_{SCP(SNSBOOST)} \leq 0.4</math> V</li> <li>• Regulation of PFC output voltage: <math>V_{reg(SNSBOOST)} = 2.5</math> V</li> <li>• PFC soft-OVP (cycle-by-cycle): <math>V_{OVP(SNSBOOST)} \geq 2.63</math> V</li> <li>• Brownout function for HBC: converter enable voltage: <math>V_{start(SNSBOOST)} = 2.3</math> V and converter disable voltage: <math>V_{UVP(SNSBOOST)} = 1.6</math> V</li> </ul>

### 4. Application diagram and block diagrams

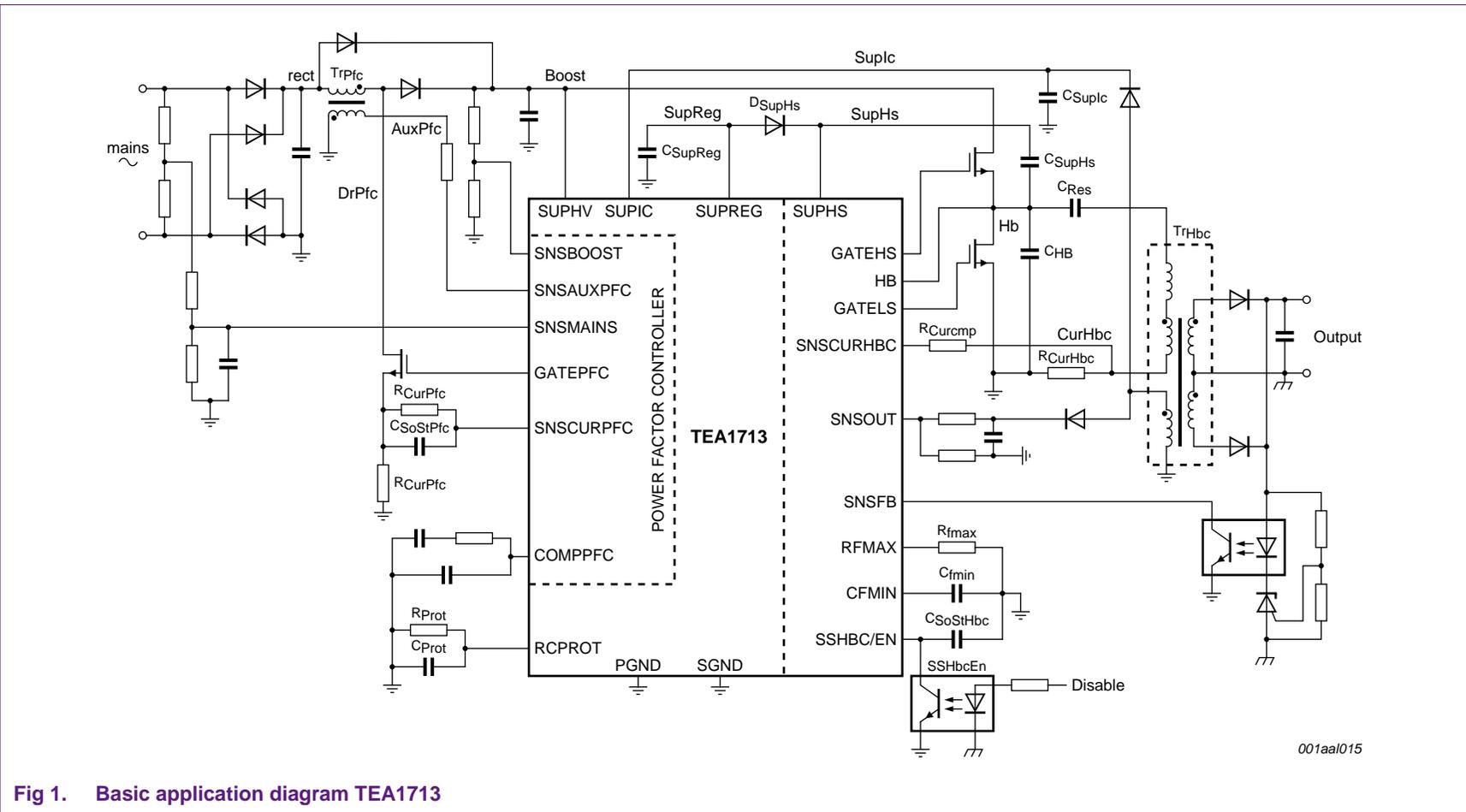


Fig 1. Basic application diagram TEA1713

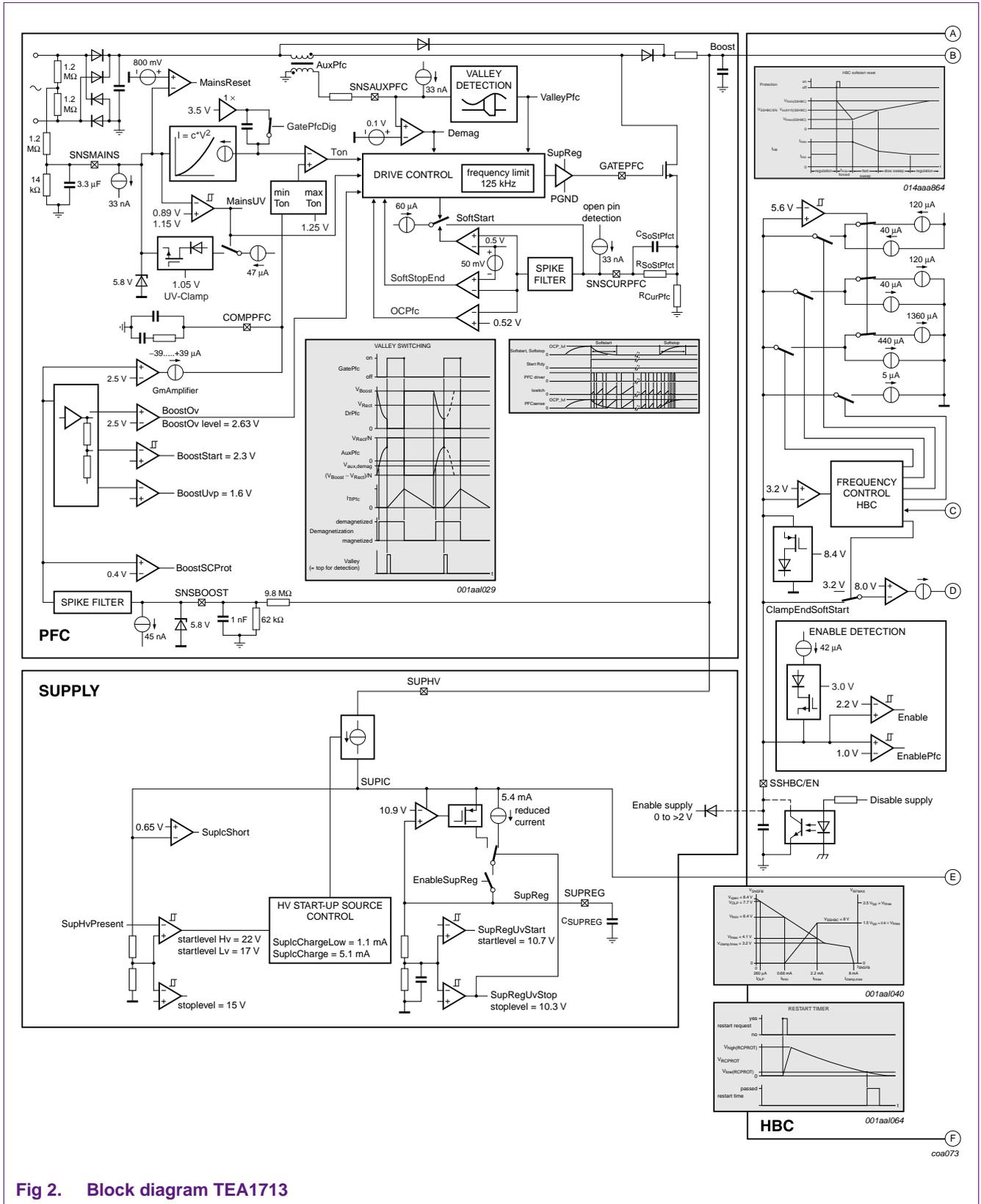


Fig 2. Block diagram TEA1713


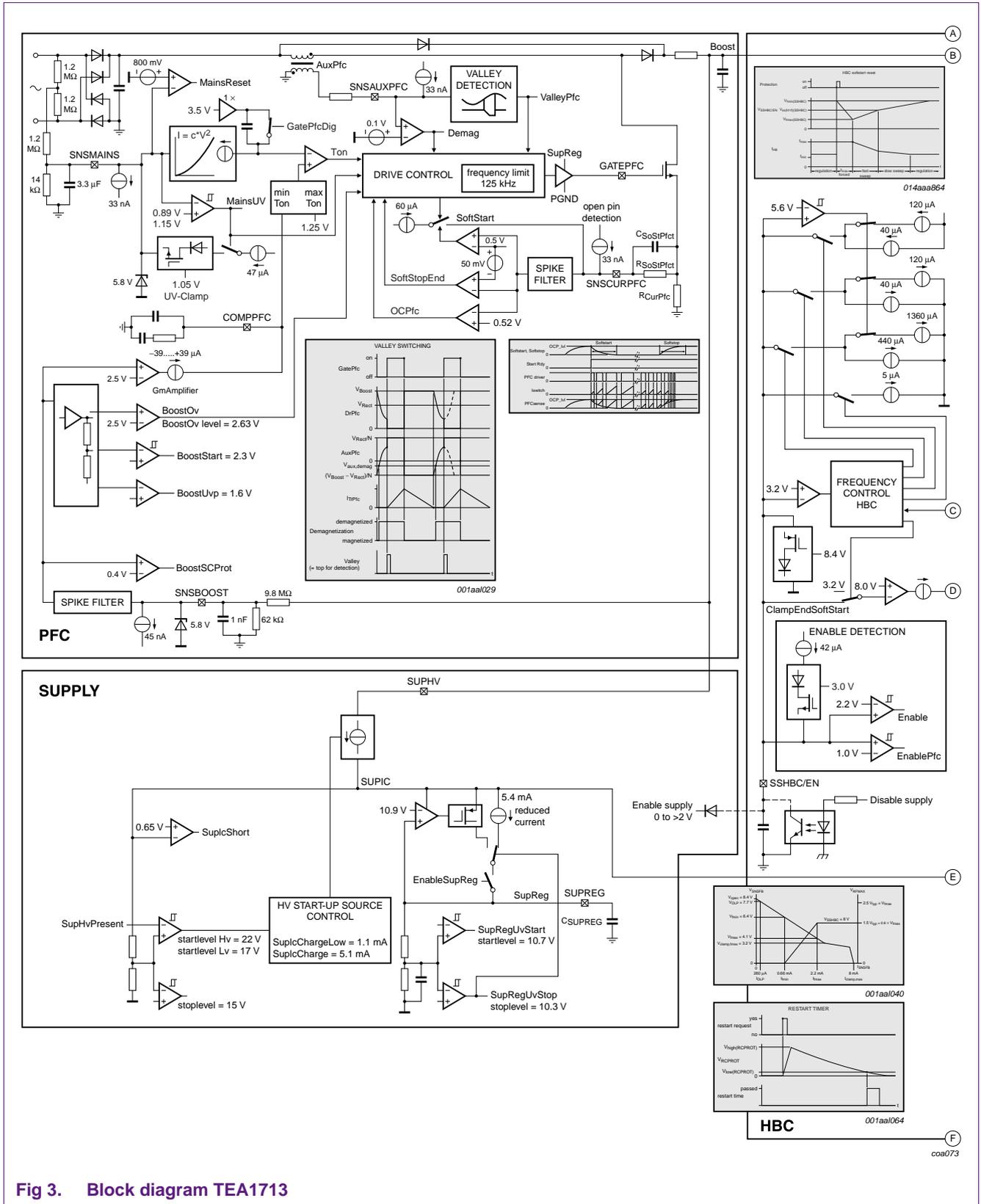


Fig 3. Block diagram TEA1713

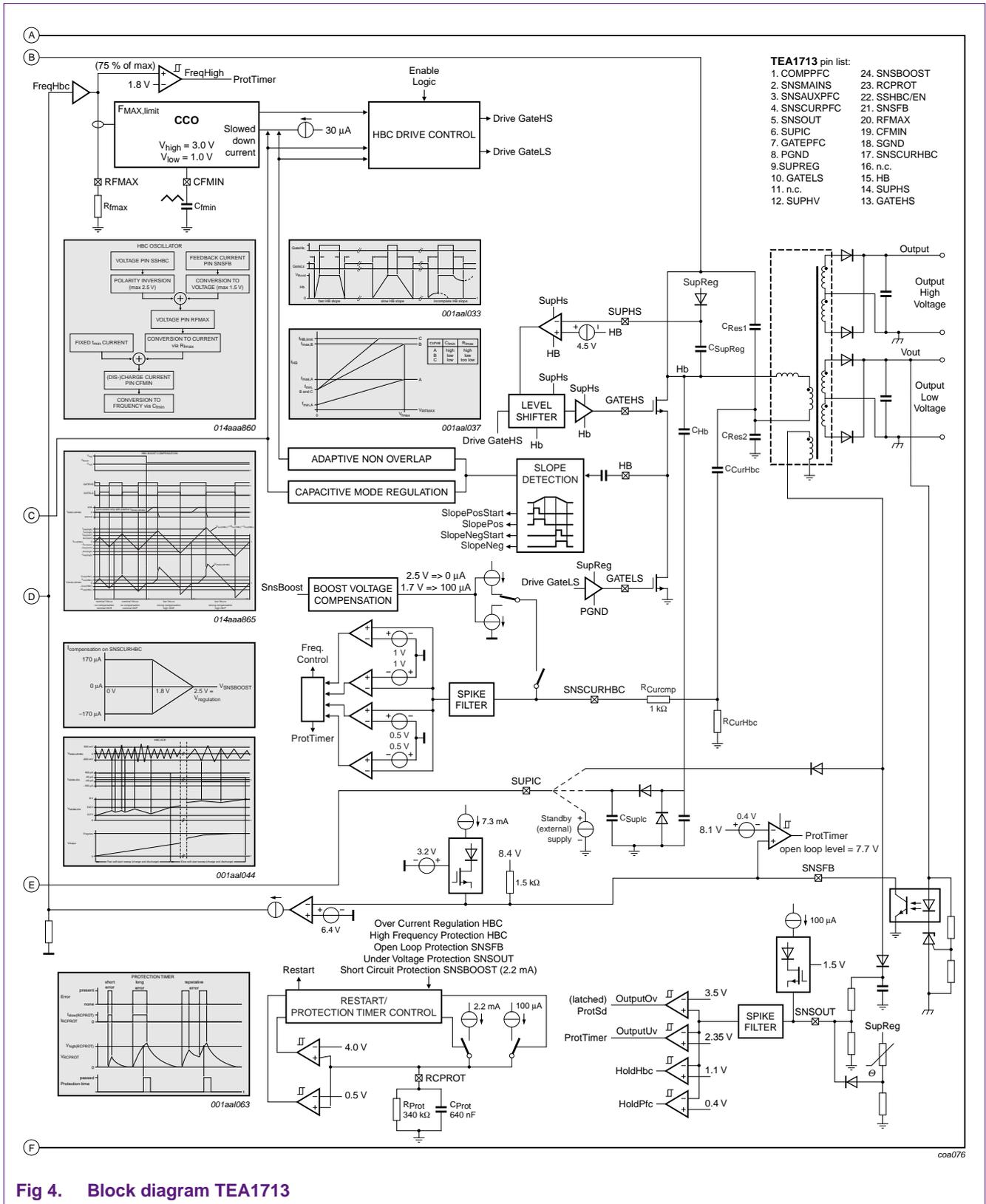

5. Supply functions

5.1 Basic supply system overview

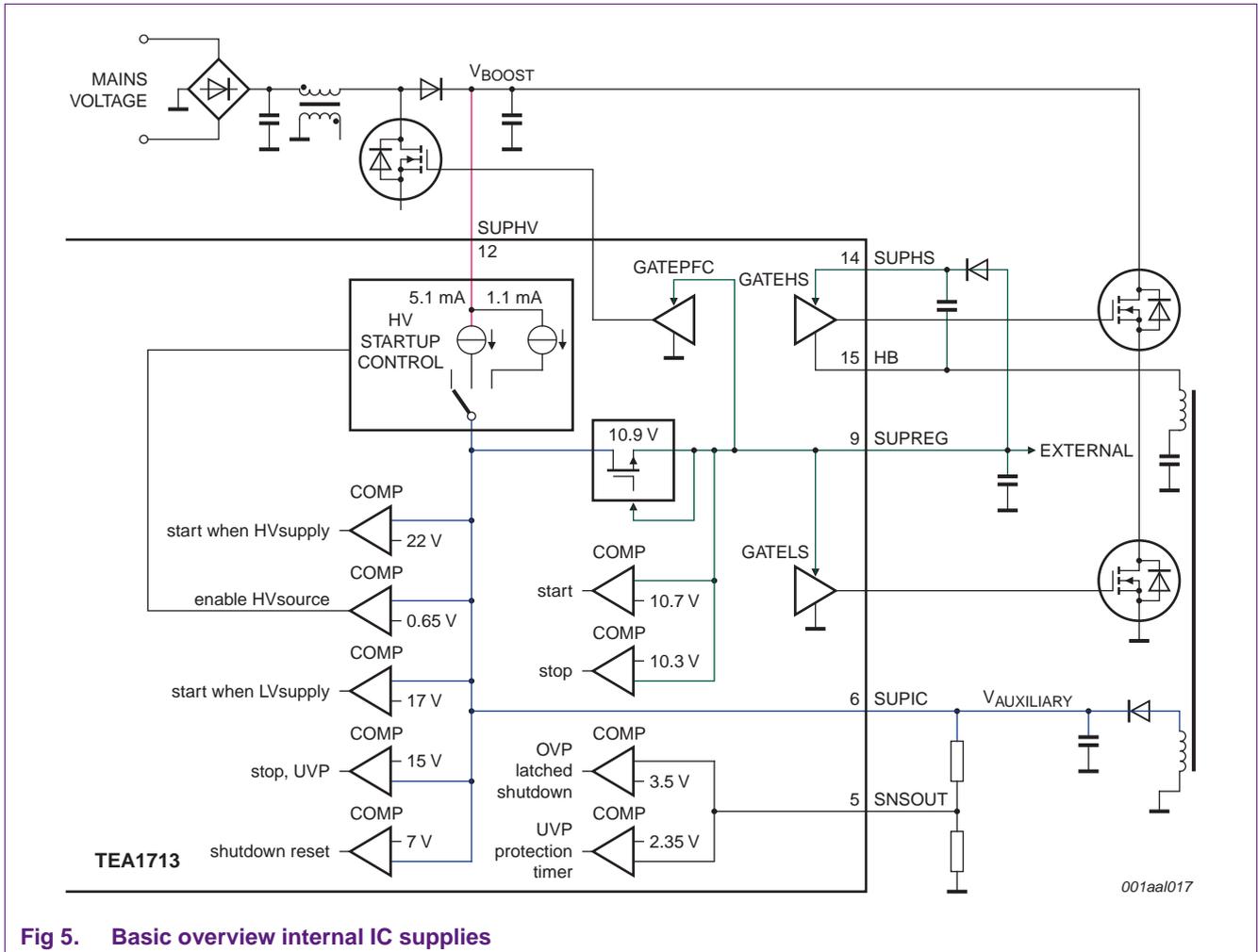


Fig 5. Basic overview internal IC supplies

5.1.1 TEA1713 supplies

The main supply for the TEA1713 is SUPIC.

SUPHV can be used to charge SUPIC for starting the supply. During operation a supply voltage is applied to SUPIC and the SUPHV source is switched off. The SUPHV source is only switched on again at a new start-up.

The internal regulator SUPREG generates a fixed voltage of 10.9 V to supply the internal MOSFET drivers: GATEPFC, GATELS and GATEHS. A bootstrap function with an external diode is used to make supply SUPHS. This is used to supply GATEHS.

SUPIC and SUPREG also supply other internal TEA1713 circuits.

### 5.1.2 Supply monitoring and protection

The supply voltages are internally monitored to determine when to initiate certain actions, such as starting, stopping or protection.

In several applications (e.g. when using an auxiliary winding construction) the SUPIC voltage can also be used to monitor the HBC output voltage by protection input SNSOUT.

## 5.2 SUPIC - the low voltage IC supply

SUPIC is the main IC supply. Except for the SUPHV circuit, all internal circuits are either directly or indirectly supplied from this pin.

### 5.2.1 SUPIC start-up

Connect SUPIC to an external buffer capacitor. This buffer capacitor can be charged in several ways:

- Internal high-voltage (HV) start-up source
- Auxiliary supply, e.g. from a winding on the HBC transformer
- External DC supply, e.g. from a standby supply

The IC starts operating when the SUPIC and SUPREG voltage have reached the start level. The start level value of SUPIC depends on the condition of the SUPHV pin.

#### 5.2.1.1 SUPHV $\geq 25 V_{\max}$

This is the case in a standalone application where the HV start-up source initially charges SUPIC. The SUPIC start level is 22 V. The large difference between start level and stop level (15 V) is used to allow discharge of the SUPIC capacitor until the auxiliary supply can take over the IC supply.

#### 5.2.1.2 SUPHV not connected/used

This is the case when the TEA1713 is supplied from an external DC supply. The SUPIC start level is now 17 V. During start-up and operation the IC is continuously supplied by the external DC supply. The SUPHV pin must not be connected for this kind of application.

### 5.2.2 SUPIC stop, UVP and SCP

The IC stops operating when the SUPIC voltage drops below 15 V which is the UnderVoltage Protection (UVP) of SUPIC. While in the process of stopping, the HBC continues until the low-side MOSFET is active, before stopping the PFC and HBC operation.

SUPIC has a low level detection at 0.65 V to detect a short circuit to ground. This level also controls the current source from the SUPHV pin.

### 5.2.3 SUPIC current consumption

The SUPIC current consumption depends on the state of the TEA1713.

- Disabled IC state:  
When the IC is disabled via the SSHBC/EN pin, the current consumption is low at 250  $\mu$ A.
- SUPIC charge, SUPREG charge, thermal hold, restart and shutdown state:  
During the charging of SUPIC and SUPREG before start-up, during a restart sequence or during shutdown after activation of protection, only a small part of the IC is active. The PFC and HBC are disabled. The current consumption from SUPIC in these states is small at 400  $\mu$ A.
- Boost charge state:  
PFC is switching and HBC is still off. The current from the high-voltage start-up source is large enough to supply SUPIC, so current consumption is below the maximum current (5.1 mA) that SUPHV can deliver.
- Operating supply state:  
Both PFC and HBC are switching. The current consumption is larger. The MOSFET drivers are dominant in the current consumption (see [Section 5.5.5](#)), especially during soft-start of the HBC, when the switching frequency is high, and also during normal operation. Initially, the stored energy in the SUPIC capacitor delivers the SUPIC current. After a short time the current supply is taken over by the supply source on SUPIC during normal operation.

## 5.3 SUPIC supply using HBC transformer auxiliary winding

### 5.3.1 Start-up by SUPHV

In a standalone power supply application, the IC can be started by a high-voltage source such as the rectified mains voltage by connecting the high-voltage input SUPHV to the boost voltage (PFC output voltage).

The internal HV start-up source, which delivers a constant current from SUPHV to SUPIC, charges the SUPIC and SUPREG. SUPHV is operational at a voltage > 25 V.

As long as the voltage at SUPIC is below the short circuit protection level (0.65 V), the current from SUPHV is low (1.1 mA). This is to limit the dissipation in the HV start-up source when SUPIC is shorted to ground.

During normal conditions, SUPIC quickly exceeds the protection level and the HV start-up source switches to normal current (5.1 mA). The HV start-up source switches off when SUPIC has reached the start level (22 V). The current consumption from SUPHV is low (7  $\mu$ A) when switched off.

When SUPIC has reached the start level (22 V), SUPREG is charged. When SUPREG reaches the level of 10.7 V, it enables operation of HBC and PFC.

The auxiliary winding supply of the HBC transformer must take over the supply of SUPIC before it is discharged to the SUPIC under voltage stop level (15 V).

5.3.2 Block diagram for SUPIC start-up

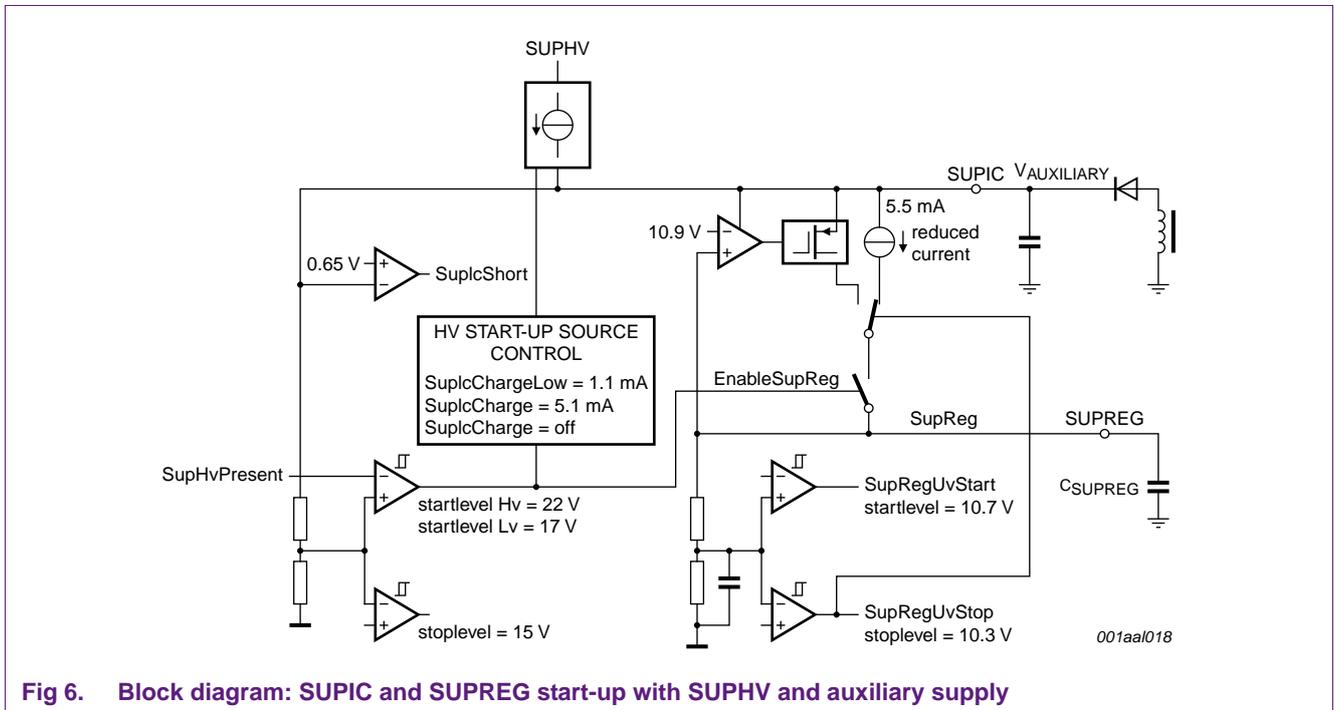


Fig 6. Block diagram: SUPIC and SUPREG start-up with SUPHV and auxiliary supply

5.3.3 Auxiliary winding on the HBC transformer

An auxiliary winding on the HBC transformer can be used to obtain a supply voltage for SUPIC during operation. As SUPIC has a wide operational voltage range (15 V to 38 V), this is not a critical parameter.

But:

- The voltage on SUPIC must be low for low power consumption.
- The auxiliary supply must be made accurately representing the output voltage to use the voltage from the auxiliary winding for IC supply and HBC output voltage measurement (by SNSOUT). Place this winding on the secondary (output) side to ensure good coupling.
- When mains insulation is included in the HBC transformer, it can impact the construction of the auxiliary winding. Triple insulated wire is needed when the auxiliary winding is placed on the mains-insulated area of the transformer construction.

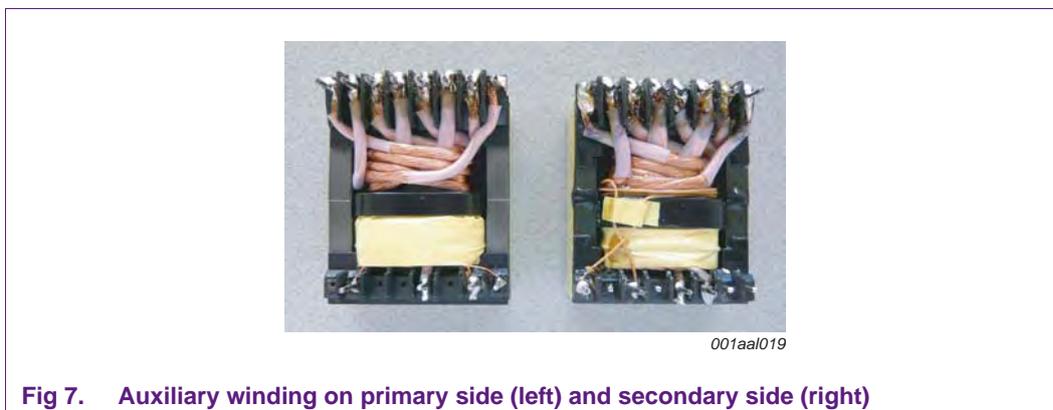


Fig 7. Auxiliary winding on primary side (left) and secondary side (right)

### 5.3.3.1 SUPIC and SNSOUT by auxiliary winding

The SNSOUT input provides a combination of four functions:

- Overvoltage protection:  $\text{SNSOUT} > 3.5 \text{ V}$ , latched
- Undervoltage protection:  $\text{SNSOUT} < 2.35 \text{ V}$ , protection timer
- Hold HBC:  $\text{SNSOUT} < 1.1 \text{ V}$ , stop switching HBC (for Burst mode)
- Hold HBC + PFC:  $\text{SNSOUT} < 0.4 \text{ V}$ , stop switching HBC and PFC (for Burst mode)

**Remark:** A more detailed explanation of the SNSOUT functions can be found in [Section 10.3.1](#) and [Section 10.3.2](#).

Often, a circuit is used which combines SUPIC and the output voltage monitoring by SNSOUT, with one auxiliary winding on the HBC transformer. But an independent construction for SUPIC and SNSOUT is also possible. This could be in a situation where SUPIC is supplied by a separate standby supply and an auxiliary winding is only used for output voltage sensing. It is also possible not to use SNSOUT for output sensing but as a general-purpose protection input. See [Section 10.3.3](#) for more information.

In a combined function of SUPIC and SNSOUT by an auxiliary winding on the HBC transformer, some issues must be addressed to obtain a good representation of the output voltage for SNSOUT measurement.

The advantage of a good coupling/representation of the auxiliary winding with the output windings is also that a stable auxiliary voltage is obtained for SUPIC. A low SUPIC voltage value can be designed more easily for lowest power consumption.


### 5.3.3.2 Auxiliary supply voltage variations by output current

At high (peak) current loads, the voltage drop across the series components of the HBC output stage (resistance and diodes) is compensated by regulation. This results in a higher voltage on the windings at higher output currents due to the higher currents causing a larger voltage drop across the series components. An auxiliary winding supply shows this variation caused by the HBC output.
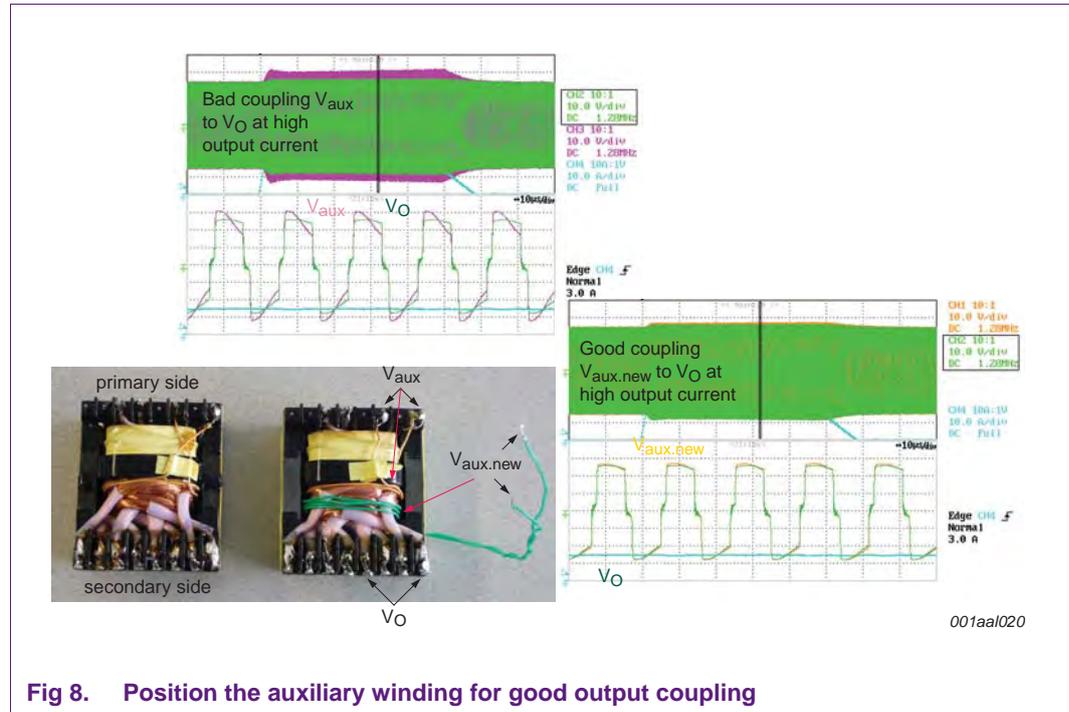
### 5.3.3.3 Voltage variations by auxiliary winding position: primary side component

Due to a less optimal position of the auxiliary winding, the voltage for SNSOUT and/or SUPIC can contain a certain amount of undesired primary voltage component. This can seriously endanger the feasibility of the SNSOUT sensing function.

The coupling of the auxiliary winding with the primary winding must be as small as possible to avoid a primary voltage component on the auxiliary voltage. Place the auxiliary winding on the secondary winding(s) and as physically remote as possible from the primary winding to obtain this. See differences in results given by comparison on secondary side position in [Figure 8](#).



### 5.3.4 Difference between UVP on SNSOUT and SNSCURHBC OCP/OCR

In a system that uses output voltage sensing with the SNSOUT function, there can be an overlap in functionality in an over power or short-circuit situation. In such a situation, often both the SNSOUT UVP and the OCP/OCR on SNSCURHBC, activate the protection timer.

There are basic differences between both functions:

- SNSOUT monitors (indirectly) the HBC output voltage or another external protection circuit (such as NTC temperature measurement)
- OCP/OCR monitors the power in the system by sensing the primary current in detail

SNSOUT is a more general usable protection input while SNSCURHBC is specifically designed for HBC operation. In addition, SNSOUT also offers three other functions:

- OVP (latched)
- hold HBC
- hold HBC + PFC (for Burst mode)

## 5.4 SUPIC supply by external voltage

### 5.4.1 Start-up

When the TEA1713 is supplied by an external DC supply, the SUPHV pin can remain unconnected. The SUPIC start level is now 17 V.

When the SUPIC exceeds 17 V the internal regulator is activated and charge SUPREG.

At  $SUPREG \geq 10.7$  V, GATELS is switched on for the bootstrap function to charge SUPHS. And at the same time the PFC operation is internally enabled. When all enable conditions are met, the TEA1713 starts the PFC function and when  $V_{boost}$  reaches approximately 90 % ( $SNSBOOST \geq 2.3$  V) of its nominal value, the HBC starts.

### 5.4.2 Stop

Operation of the TEA1713 can be stopped by switching off the external source for SUPIC. When the voltage level on SUPIC drops below 15 V, operation is stopped.

In case of shutdown (because of protection), this state is reset by internal logic when the SUPIC voltage drops below 7 V.

## 5.5 SUPREG

SUPIC has a wide voltage range for easy application. Because of this, SUPIC cannot be directly used to supply the internal MOSFET drivers as this would exceed the allowed gate voltage of many external MOSFETs.

The TEA1713 contains an integrated series stabilizer to avoid this issue and to create a few other benefits. The series stabilizer generates an accurate regulated voltage on SUPREG on the external buffer capacitor.

This stabilized SUPREG voltage is used for:

- Supply of internal PFC driver
- Supply of internal low-side HBC driver
- Supply of internal high-side driver via external components
- Reference voltage for optional external circuits

The series stabilizer for SUPREG is enabled after SUPIC has been charged. In this way optional external circuitry at SUPREG does not consume from the start-up current during the charging of SUPIC. The capacitor on SUPIC acts as a buffer at charge of SUPREG and start-up of the IC.


The SUPREG voltage must reach the  $V_{start(SUPREG)}$  level before the IC starts operating to ensure that the external MOSFETs receive sufficient gate drive, provided that the SUPIC voltage has also reached the start level.

The SUPREG has an UnderVoltage Protection. When the SUPREG voltage drops below the 10.3 V two actions take place:

- The IC stops operating to prevent unreliable switching due to too low gate driver voltage. The PFC controller stops switching immediately, but the HBC continues until the low-side stroke is active.
- The maximum current from the internal SUPREG series stabilizer is reduced to 5.4 mA. In case of an overload at SUPREG in combination with an external DC supply for SUPIC, this action reduces the dissipation in the series stabilizer.

It is important to realize that in principle, SUPREG can only source current.

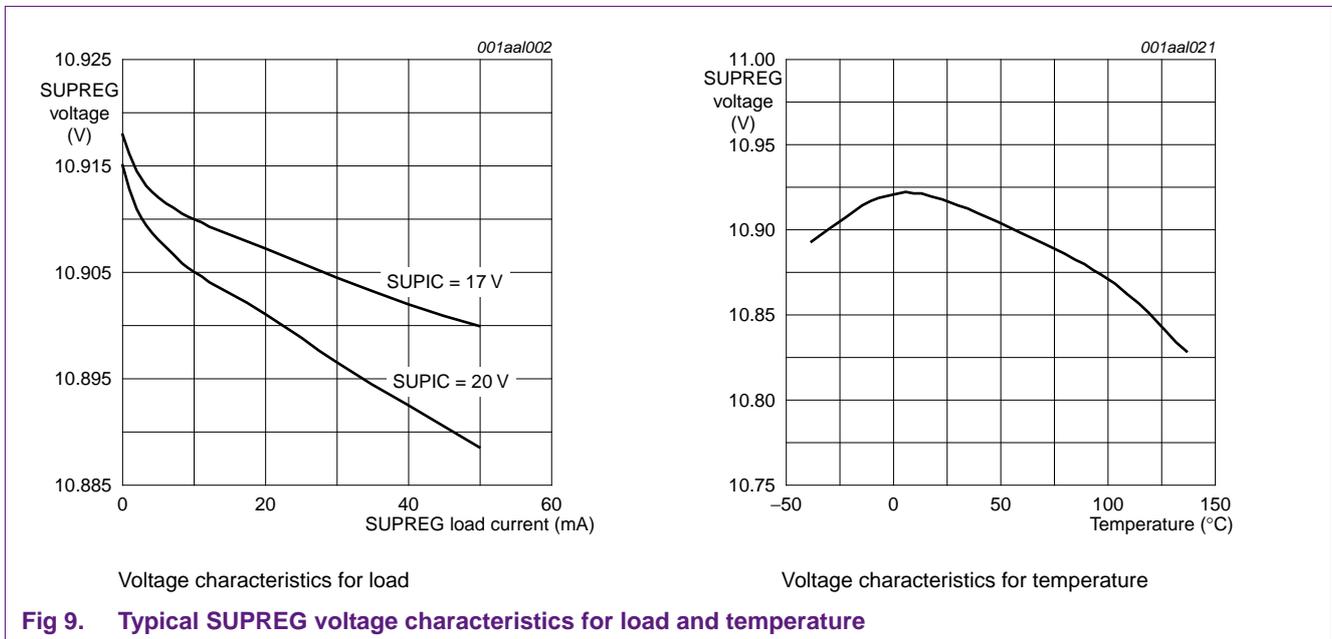The drivers of GATELS and GATEPFC are supplied by this voltage and draw current from it during operation depending on the operating condition. Some change in value can be expected due to current load and temperature:



5.5.1 Block diagram of SUPREG regulator

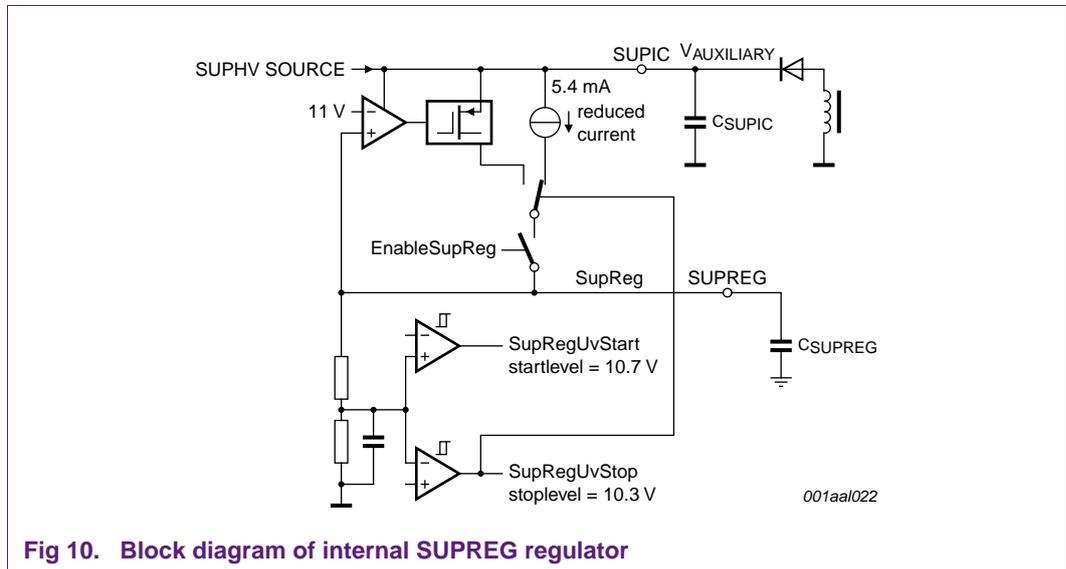


Fig 10. Block diagram of internal SUPREG regulator

5.5.2 SUPREG during start-up

SUPREG is supplied by SUPIC. SUPIC is the unregulated external power source that provides the input voltage for the internal voltage regulator that provides SUPREG.

At start-up SUPIC must reach a specific voltage level before SUPREG is activated:

- Using the internal HV supply, SUPREG is activated when SUPIC  $\geq$  22 V
- Using an external low voltage supply, SUPREG is activated when SUPIC  $\geq$  17 V

5.5.3 Supply voltage for the output drivers: SUPREG

The TEA1713 has a powerful output stage for GATEPFC and GATELS to drive large MOSFETs. These internal drivers are supplied by SUPREG that provides a fixed voltage.

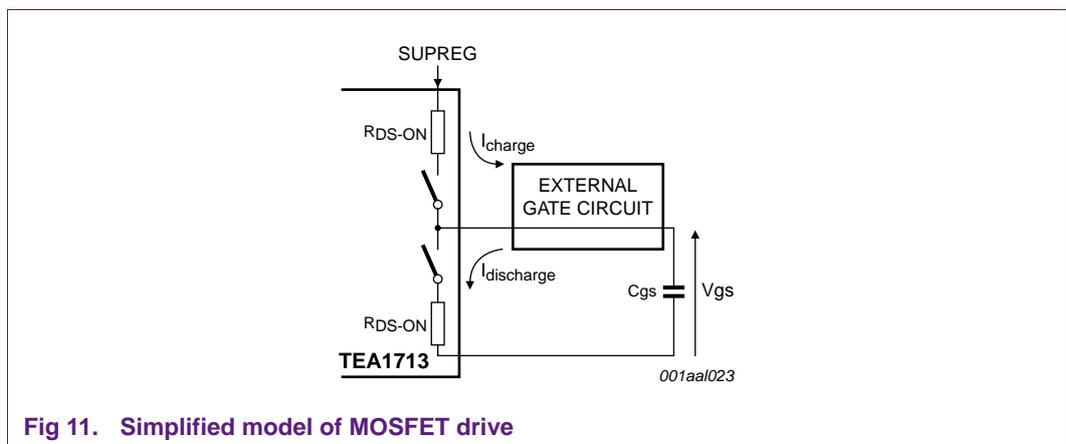


Fig 11. Simplified model of MOSFET drive

It can be seen from [Figure 11](#) that current is taken from SUPREG when the external MOSFET is switched on by charging the gate to a high voltage.

The shape of the current from SUPREG at switch-on is related to:

- The supply voltage for the internal driver (10.9 V)
- The characteristic of the internal driver
- The gate capacitance to be charged
- The gate threshold voltage for the MOSFET to switch on
- The external circuit to the gate

**Remark:** The switching moments of GATEPFC and GATELS are independent in time. The charging of SUPHS for GATEHS is synchronized in time with GATELS but has a different shape because of the bootstrap function.

#### 5.5.4 Supply voltage for the output drivers: SUPHS

The high-side driver is supplied by an external bootstrap buffer capacitor. The bootstrap capacitor is connected between the high-side reference pin HB and the high-side driver supply input pin SUPHS. During the time that HB is low an external diode from SUPREG charges this capacitor. By selecting a suitable external diode, the voltage drop between SUPREG and SUPHS can be minimized. This is especially important when using a MOSFET that needs a large amount of gate charge and/or when switching at high frequencies.

Instead of using SUPREG as the power source for charging SUPHS, another supply source can be used. In such a construction it is important to check for correct start/stop sequences and to prevent the voltage exceeding the maximum value of HB +14 V.

**Remark:** The current taken from SUPREG to charge SUPHS differs for each cycle in time and shape from the current taken by drivers GATEPFC and GATELS.

##### 5.5.4.1 Initial charging of SUPHS

At start-up, SUPHS is charged by the bootstrap function by setting GATELS high to switch on the low side MOSFET. While SUPHS is being charged, GATELS is switched on for charging and the PFC operation is started. The time between start charging and start HBC operation is normally sufficient to charge SUPHS completely. Start HBC operation is when SNSBOOST reaches 2.3 V which is approximately 90 % of the nominal  $V_{\text{boost}}$ .

##### 5.5.4.2 Current load on SUPHS

The current taken from SUPHS consists of two parts:

- Internal MOSFET driver GATEHS
- Internal circuit to control GATEHS (37  $\mu\text{A}$ , quiescent current)

[Figure 12](#) shows that the current taken by the driver GATEHS occurs at switch-on. The shape of the current from SUPHS at switch-on is related to:

- The value of the supply voltage for the internal driver
- The characteristic of the internal driver
- The gate capacitance to be charged
- The gate threshold voltage for the MOSFET to switch on
- The external circuit to the gate

The voltage value of SUPHS can vary.

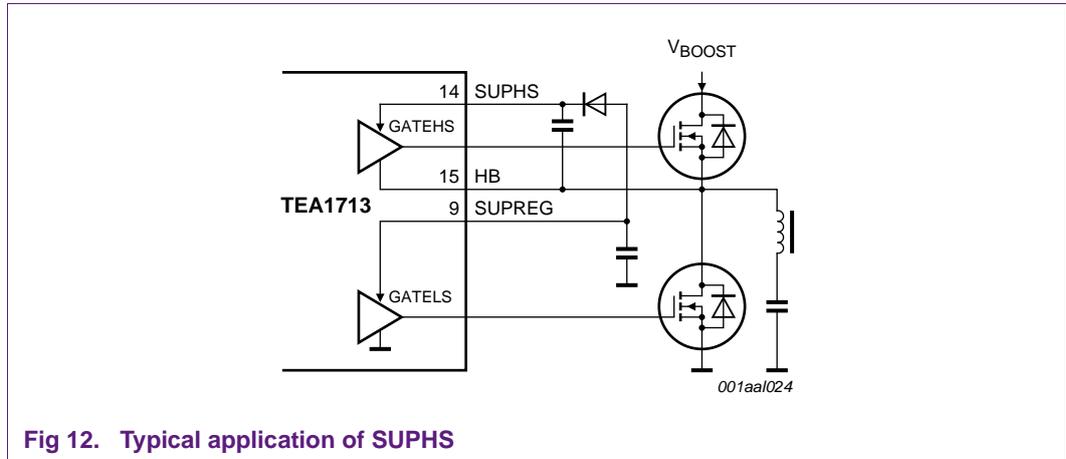


Fig 12. Typical application of SUPHS

5.5.4.3 Lower voltage on SUPHS

During normal operation, each time the Half-Bridge (HB) node is switched to ground level, the bootstrap function charges the SUPHS capacitor. Because of the voltage drop across the bootstrap diode, the value of SUPHS is normally lower than SUPREG (or other bootstrap supply input).

The voltage drop across the bootstrap diode is directly related to the amount of current that is required to charge SUPHS. The resultant SUPHS voltage also has a relation to the time available for charging.

A large voltage drop occurs when an external MOSFET with a large gate capacitance has to be switched at high frequency (high current and a short time).

Also, during Burst mode operation, a low voltage on SUPHS can occur. In Burst mode there are (long) periods of not switching and therefore no charging of SUPHS. During this time the circuit supplied by SUPHS slowly discharges the supply voltage capacitor. When a new burst starts, the SUPHS voltage is lower than during normal operation. During the first switching cycles SUPHS is recharged to its normal level. During Burst mode, at low output power, the switching frequency is normally rather high which limits a fast recovery of the SUPHS voltage.

Although in most applications the voltage drop is limited, it is an important issue to be evaluated. It can influence the selection of the best diode type for the bootstrap function and the value of the buffer capacitor on SUPHS.

5.5.5 SUPREG power consumed by MOSFET drivers

During operation the drivers GATEPFC, GATELS and GATEHS charging the gate capacitances of the external MOSFETs are a major part of the power consumption from SUPREG. The amount of energy required in time is linear to the switching frequency. Often, for the MOSFETs used, the total charge is specified for certain conditions. With this figure an estimation can be made for the amount of current needed from SUPREG.

5.5.5.1 GATELS and GATEHS (driving a total of two MOSFETs)

$$\Delta I_{SUPIC} = 2 \times Q_{gate} \times f_{bridge} \tag{1}$$

Example:

- $Q_{\text{gate}} = 40 \text{ nC}$
- $f_{\text{bridge}} = 100 \text{ kHz}$

$$\Delta I_{\text{SUPIC}} = 2 \times 40 \text{ nC} \times 100 \text{ kHz} = 8 \text{ mA}$$

**Remark:** The calculated value is generally higher than the practical value, because the switching operation deviates from the MOSFET specification for  $Q_{\text{gate}}$ .

### 5.5.5.2 GATEPFC

$$\Delta I_{\text{SUPIC}} = Q_{\text{gate}} \times f_{\text{PFC}} \quad (2)$$

Example:

- $Q_{\text{gate}} = 40 \text{ nC}$
- $f_{\text{bridge}} = 100 \text{ kHz}$

$$\Delta I_{\text{SUPIC}} = 40 \text{ nC} \times 100 \text{ kHz} = 4 \text{ mA}$$

## 5.5.6 SUPREG supply voltage for other circuits

The regulated voltage of SUPREG can also be used as a regulated supply for an external circuit. The load of the external circuits affects the start-up (time) and the total load (IC + external circuit) of SUPREG during operation.

### 5.5.6.1 Current available for supplying an external circuit from SUPREG

The total current available from SUPREG is a minimum of 40 mA. How much current the IC is using must be determined to ensure how much current is available for an external circuit.

$$I_{\text{SUPREG\_for\_external}} = 40 \text{ mA} - I_{\text{SUPREG\_for\_IC}}$$

With respect to the IC, by far the greatest amount of current from SUPREG is consumed by the MOSFET drivers (GATELS, GATEHS and GATEPFC). Other circuit parts in the IC, consume a maximum of 3 mA.

$$I_{\text{SUPREG\_for\_IC}} = I_{\text{SUPREG\_for\_MOSFET-drivers}} + I_{\text{SUPREG\_for\_other\_IC-circuits}}$$

$$I_{\text{SUPREG\_for\_IC}} = I_{\text{SUPREG\_for\_MOSFET-drivers}} + 4 \text{ mA}_{\text{max}}$$

$I_{\text{SUPREG\_for\_MOSFET-drivers}}$  can be estimated by the method provided in [Section 12](#)

### 5.5.6.2 An estimation by measurement

The current used by SUPIC, while supplying the circuit from an external power supply, can be assumed as a first approximation of how much current the IC circuits take from SUPREG. Using this value, an estimation can be made of the power available for external circuits.

**Remark:** The highest power consumption value is reached when the MOSFET drivers are switching at the highest frequency.

Example:

$$I_{SUPIC(\text{maximum measured})} = 18 \text{ mA}$$

$$I_{SUPREG(\text{for IC circuits})} = I_{SUPIC(\text{maximum measured})} = 18 \text{ mA}$$

$$I_{SUPREG(\text{for externals})} = 40 \text{ mA} - I_{SUPREG(\text{for IC circuits})} = 40 \text{ mA} - 18 \text{ mA} = 22 \text{ mA}$$

**Remark:** SUPREG must remain above the undervoltage protection level of 10.3 V to maintain full functionality. During start-up, high external current loads can lead to problems.

## 5.6 Value of the capacitors on SUPIC, SUPREG and SUPHS

Some practical examples are provided in [Section 12](#).

### 5.6.1 Value of the capacitor on SUPIC

#### 5.6.1.1 General

Use two types of capacitors on SUPIC. An SMD ceramic type with a smaller value located close to the IC and an electrolytic type with the major part of the capacitance.

#### 5.6.1.2 Start-up

When the supply is initially provided by an HV source, before being handled by an auxiliary winding, a larger capacitor is needed. The capacitor value must be large enough to handle the start-up before the auxiliary winding takes over the supply of SUPIC.

Example:

- $I_{SUPIC(\text{start-up})} = 10 \text{ mA}$
- $\Delta V_{SUPIC(\text{start-up})} = 22 \text{ V} - 15 \text{ V} = 7 \text{ V}$
- $\Delta t_{V_{aux} > 15 \text{ V}} = 70 \text{ ms}$

$$C_{SUPIC} > I_{SUPIC(\text{start-up})} \times \frac{\Delta t_{V_{aux} > 15 \text{ V}}}{\Delta V_{SUPIC(\text{start-up})}} = 10 \text{ mA} \times \frac{70 \text{ ms}}{7 \text{ V}} = 100 \text{ } \mu\text{F} \quad (3)$$

#### 5.6.1.3 Normal operation

The main purpose of the capacitors on SUPIC for normal operation is to keep the current load variations (e.g. gate drive currents) local.

#### 5.6.1.4 Burst mode operation

When Burst mode operation is applied, the supply construction often uses an auxiliary winding and start-up from an HV source. While in Burst mode there is a long period during which the auxiliary winding is not able to charge the SUPIC because there is no HBC switching (time between two bursts). Therefore, the capacitor value on SUPIC must be large enough to keep the voltage above 15 V to prevent activating the SUPIC undervoltage stop level.

Example:

- $I_{SUPIC(\text{between 2 bursts})} = 4 \text{ mA}$
- $\Delta V_{SUPIC(\text{burst})} = V_{aux \text{ burst}} - 15 \text{ V} = 19 \text{ V} - 15 \text{ V} = 4 \text{ V}$
- $\Delta t_{\text{between 2 bursts}} = 25 \text{ ms}$

$$C_{SUPIC} > I_{SUPIC(\text{start-up between 2 bursts})} \times \frac{\Delta t_{\text{between 2 bursts}}}{\Delta V_{SUPIC(\text{burst})}} = 4 \text{ mA} \times \frac{25 \text{ ms}}{4 \text{ V}} = 25 \text{ } \mu\text{F} \quad (4)$$

### 5.6.2 Value of the capacitor for SUPREG

The capacitor on SUPREG must not be larger than the capacitor on SUPIC to support charging of SUPREG during an HV source start. This is to prevent a severe voltage drop on SUPIC due to the charge of SUPREG. If SUPIC is supplied by an external (standby) source, this is not important.

SUPREG is the supply for the current of the gate drivers. Keeping current peaks local can be achieved using an SMD ceramic capacitor supported by an electrolytic capacitor. This is necessary to provide sufficient capacitance to prevent voltage drop during high current loads. The value of the capacitor on SUPREG must be much larger than the (total) capacitance of the MOSFETs that must be driven (including the SUPHS parallel load and capacitor bootstrap construction) to prevent significant voltage drop.

When considering the internal voltage regulator, the value of the capacitance on SUPREG must be  $\geq 1 \text{ } \mu\text{F}$ . Often a much larger value is used for the reasons mentioned previously.

### 5.6.3 Value of the capacitor for SUPHS

The SUPHS capacitor must be much larger than the gate capacitance to support charging the gate of the high side MOSFET. This is to prevent a significant voltage drop on SUPHS by the gate charge. When Burst mode is applied, SUPHS is discharged by  $37 \text{ } \mu\text{A}$  during the time between two bursts.

## 6. MOSFET drivers GATEPFC, GATELS and GATEHS

The TEA1713 provides three outputs for driving external high-voltage power MOSFETs:

- GATEPFC for driving the PFC MOSFET
- GATELS for driving the low side of the HBC MOSFET
- GATEHS for driving the low side of the HBC MOSFET

### 6.1 GATEPFC

The TEA1713 has a strong output stage for PFC to drive a high-voltage power MOSFET. It is supplied by the fixed voltage from SUPREG = 10.9 V.

### 6.2 GATELS and GATEHS

Both drivers have identical driving capabilities for the gate of an external high-voltage power MOSFET. The low-side driver is referenced to pin PGND and is supplied from SUPREG. The high-side driver is floating, referenced to HB, the connection to the midpoint of the external half-bridge. The high-side driver is supplied by a capacitor on SUPHS that is supplied by an external bootstrap function by SUPREG. The bootstrap diode charges the capacitor on SUPHS when the low-side MOSFET is on.

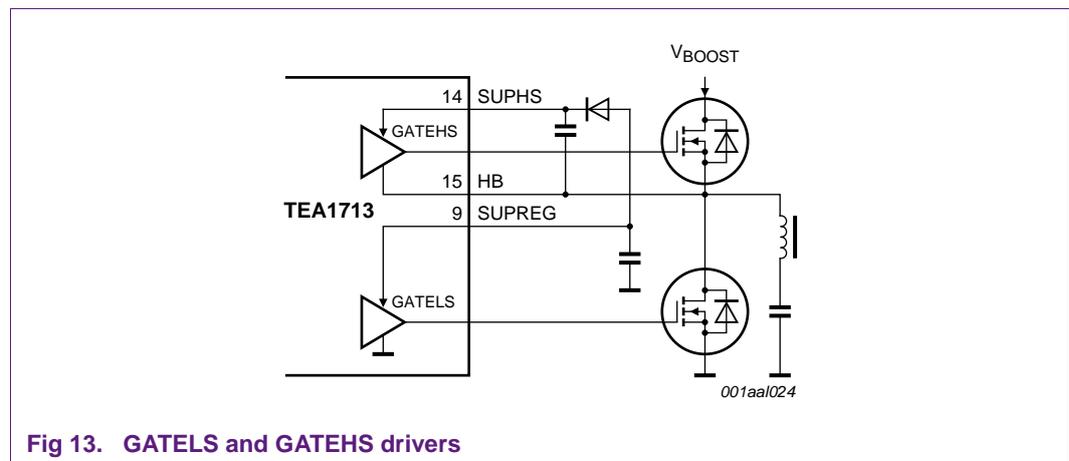


Fig 13. GATELS and GATEHS drivers

Both HBC drivers have a strong current source capability and an extra strong current sink capability. In general operation of the HBC, fast switch-on of the external MOSFET is not critical, as the HB node swings automatically to the correct state after switch-off. Fast switch off however, is important to limit switching losses and prevent delay especially at high frequency.

### 6.3 Supply voltage and power consumption

See [Section 5.5.3](#) and [Section 5.5.5](#) for a description of the supply voltages and power consumption by the MOSFET drivers.

6.4 General subjects on MOSFET drivers

6.4.1 Switch on

The time to switch on depends on:

- The supply voltage for the internal driver
- The characteristic of the internal driver
- The gate capacitance to be charged
- The gate threshold voltage for the MOSFET to switch on
- The external circuit to the gate

6.4.2 Switch off

The time to switch off depends on:

- The characteristic of the internal driver
- The gate capacitance to be discharged
- The voltage on the gate just before discharge
- The gate threshold voltage for the MOSFET to switch off
- The external circuit to the gate

Because the timing for switching off the MOSFET is more critical than switching it on, the internal driver can sink more current than it can source. At higher frequencies and/or short on-time, timing becomes more critical for correct switching. Sometimes a compromise must be made between fast switching and EMI effects. A gate circuit between the driver output and the gate can be used to optimize the switching behavior.

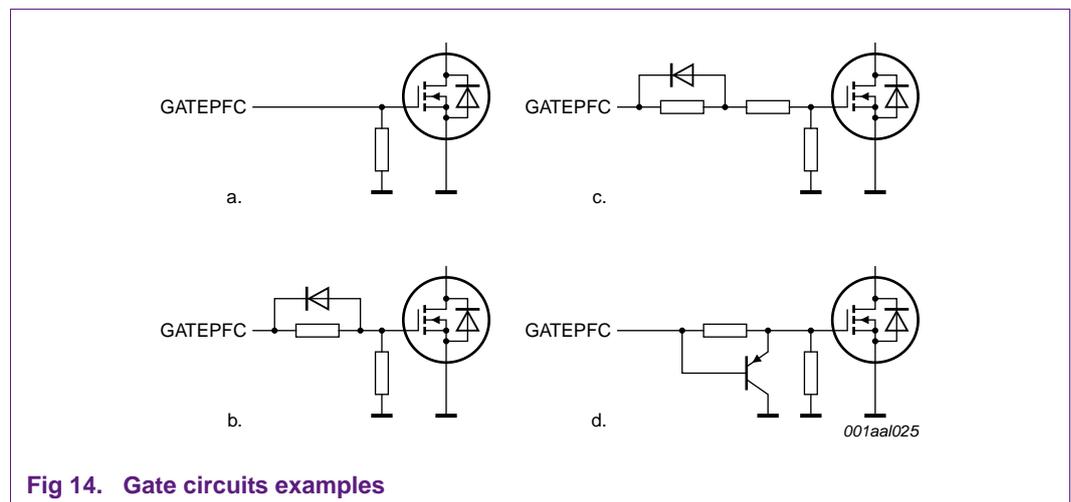


Fig 14. Gate circuits examples

Switching the MOSFETs on and off by the drivers can be approximated by alternating charge and discharge of a (gate-source) capacitance of the MOSFET through a resistor ( $R_{DSon}$  of the internal driver MOSFET).

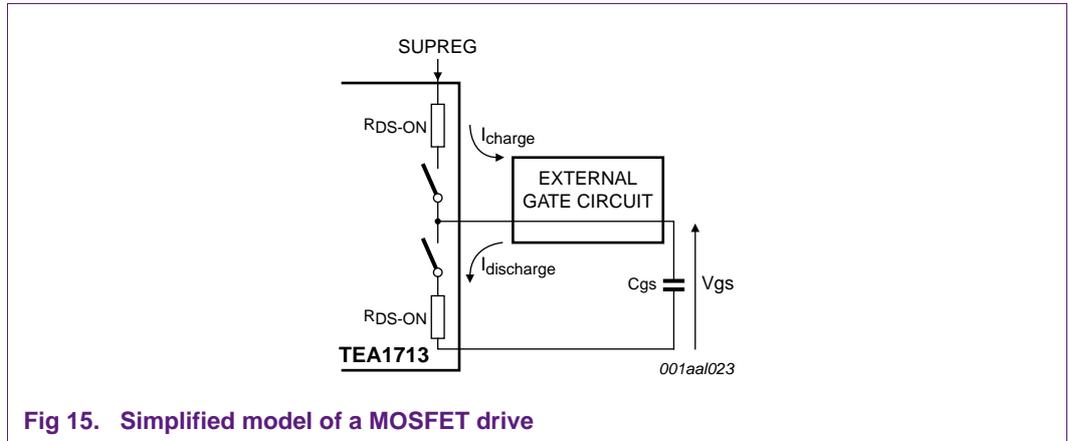


Fig 15. Simplified model of a MOSFET drive

### 6.5 Specifications

The main function of the internal MOSFET drivers is to source current and sink current to switch the external MOSFET switch on and off.

The amount of current that can be sunk and sourced is specified to show the capability of the internal driver.

The simplified model in [Figure 15](#) demonstrates that the values of the charge current and discharge current are strongly dependant upon the conditions of the supply voltage and gate voltage. The value of the source current is highest when the supply voltage is highest and the gate voltage 0 V. The value of the sink-current is highest when the gate voltage is highest.

Table 3. PFC and HBC driver specifications

Symbol	Parameter	Conditions	Min	Typ	Max	Unit
<b>PFC driver (pin GATEPFC)</b>						
$I_{source(GATEPFC)}$	source current on pin GATEPFC	$V_{GATEPFC} = 2\text{ V}$	-	-0.5	-	A
$I_{sink(GATEPFC)}$	sink current on pin GATEPFC	$V_{GATEPFC} = 2\text{ V}$	-	0.7	-	A
		$V_{GATEPFC} = 10\text{ V}$	-	1.2	-	A
<b>HBC high-side and low-side driver (pins GATEHS and GATELS)</b>						
$I_{source(GATEHS)}$	source current on pin GATEHS	$V_{GATEHS} - V_{HB} = 4\text{ V}$	-	-310	-	mA
$I_{source(GATELS)}$	source current on pin GATELS	$V_{GATELS} - V_{PGND} = 4\text{ V}$	-	-310	-	mA
$I_{sink(GATEHS)}$	sink current on pin GATEHS	$V_{GATEHS} - V_{HB} = 2\text{ V}$	-	560	-	mA
		$V_{GATEHS} - V_{HB} = 11\text{ V}$	-	1.9	-	A
$I_{sink(GATELS)}$	sink current on pin GATELS	$V_{GATELS} - V_{PGND} = 2\text{ V}$	-	560	-	mA
		$V_{GATELS} - V_{PGND} = 11\text{ V}$	-	1.9	-	A

The supply voltage provided by SUPREG for GATEPFC and GATELS is constant at 10.9 V. The supply voltage for GATEHS is lower and depends on the operating conditions (see [Section 5.5.4](#)).

## 6.6 Mutual disturbance of PFC and HBC

The charge and discharge currents for the MOSFET gate of the PFC and HBC are independently driven in time. Due to these current peaks being high, they can give disturbance on control and sense signals. As both the PFC controller and the HBC controller are integrated in the TEA1713, the (large) driver currents of GATEPFC and GATELS can also give mutual disturbance on the operation of the controllers.

Gate circuits and PCB layout (see [Section 11.1](#)) must be designed to prevent this.

A construction similar to this provided by [Figure 14](#) helps keeping the (fast and high) switch-off current local, for a high-power PFC MOSFET.

## 7. PFC functions

The PFC operates in Quasi Resonant (QR) or Discontinuous Conduction Mode (DCM) with valley detection to reduce the switch-on losses. The maximum switching frequency of the PFC is limited to 125 kHz which reduces switching losses by valley skipping. This is mainly near the zero crossings of the mains voltage and effective at low mains input voltage and medium/low output load condition.

The PFC is designed as a boost converter with a fixed output voltage. An advantage of such a fixed boost is that the HBC can be designed to a high input voltage. This makes the HBC design easier.

Another advantage of the fixed boost is the possibility to use a smaller boost capacitor value or to have a significant longer hold-up time.

In the TEA1713 system the PFC is always active. The PFC is switched on first when the mains voltage is present. The HBC is switched on after the boost capacitor is charged to approximately 90 % of its normal value.

The system can be operated in Burst mode for improved efficiency at low output loads. During this mode the HBC determines the on/off sequences and the PFC can be made to burst simultaneously for even better efficiency results.

### 7.1 PFC output power and voltage control

The PFC of the TEA1713 is time controlled and therefore it is not necessary to measure the mains phase angle. The on-time is kept constant for a given mains voltage and load condition during the half sine wave to obtain a good Power Factor (PF) and Mains Harmonics Reduction (MHR).

With a constant on time, the switching current to the PFC output is proportional to the sine waveform input voltage.

An essential parameter for the PFC coil design is the highest peak current. This current occurs at the lowest input voltage with maximum power.

The maximum peak current  $I_{p(max)}$  for a PFC operating in Critical conduction mode can be calculated with the following equation:


$$I_{p(max)} = \frac{2 \times \sqrt{2} \times P_{in(max)}}{V_{ac(min)}} = \frac{2 \times \sqrt{2} \times \frac{P_{out(nameplate)}}{\eta}}{V_{ac(min)}} \quad (5)$$

#### Example:

- Efficiency  $\eta = 0.9$
- $P_{out(nameplate)} = 250 \text{ W}$
- $V_{ac(min)} = 90 \text{ V}$
- $I_{p(max)} = 8.73 \text{ A}$
- $I_{p(max)} + 10 \% = 9.60 \text{ A}^1$

## 7.2 PFC regulation

### 7.2.1 Sensing $V_{BOOST}$

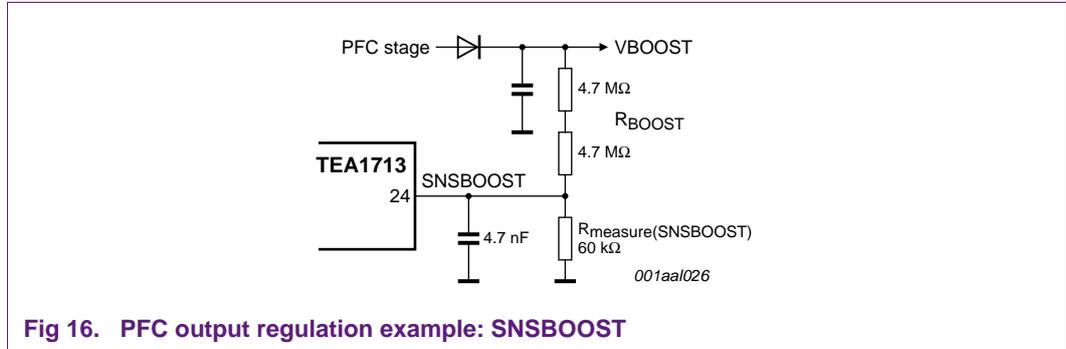

The boost output voltage value is set with a resistor divider between the PFC output voltage and pin SNSBOOST. When in regulation, the SNSBOOST voltage is kept at 2.5 V.

The resistor divider can have a total value up to 10 MΩ to limit power loss.

The measurement resistor between SNSBOOST and ground can be calculated with the following equation:

$$R_{measure(SNSBOOST)} = \frac{R_{BOOST} \times V_{reg(SNSBOOST)}}{V_{BOOST} - V_{reg(SNSBOOST)}} \tag{6}$$

Example:

- $R_{measure(RBOOST)} = 4.7 \text{ M}\Omega + 4.7 \text{ M}\Omega = 9.4 \text{ M}\Omega$
- $V_{BOOST} = 394 \text{ V}$

$$R_{measure(SNSBOOST)} = \frac{R_{BOOST} \times V_{reg(SNSBOOST)}}{V_{BOOST} - V_{reg(SNSBOOST)}} = \frac{9.4 \text{ M}\Omega \times 2.5 \text{ V}}{394 \text{ V} - 2.5 \text{ V}} = 60 \text{ k}\Omega \tag{7}$$

Use a capacitor on SNSBOOST to prevent wrong measurements due to MOSFET switching noise, mains surge events or ESD events. Also, for this reason, place the measurement resistor and the filtering capacitor close to the IC in the PCB layout.

### 7.2.2 SNSBOOST open and short circuit pin detection

The PFC does not start switching until the voltage on SNSBOOST is above 0.4 V. This serves as short circuit protection for the boost voltage and SNSBOOST pin itself.

An internal current source draws a small amount of current from SNSBOOST. This prevents switching when the pin is left open as the voltage remains lower than 0.4 V. This combination also creates an Open-Loop Protection (OLP) when, for example, one of the resistors in the boost divider network is disconnected.

1. The TEA1713 PFC, operates in Quasi Resonant (QR) mode with valley detection providing good efficiency. Valley detection needs additional ringing time within every switching cycle. This time for ringing adds short periods of no power transfer to the output capacitor. The system must compensate this with a somewhat higher peak current. A rule of thumb is that the peak current in QR mode is a maximum of 10 % higher than the calculated peak current in Critical conduction mode.

7.2.3 PFCCOMP in the PFC voltage control loop

SNSBOOST sets and controls the PFC output voltage. The internal error amplifier with a reference voltage of 2.5 V senses the voltage at SNSBOOST. The amplifier converts the input error voltage with a transconductance  $g_m = 80 \mu A/V$  to its output. This output is available at COMPPFC for adding an external loop compensation network. The current from the error amplifier results in a loop voltage at COMPPFC. This COMPPFC voltage, in combination with the voltage at pin SNSMAINS, determines the PFC switching-on time.

A compensation network, typically comprising one resistor and two capacitors at pin COMPPFC, is used to stabilize the PFC control loop.

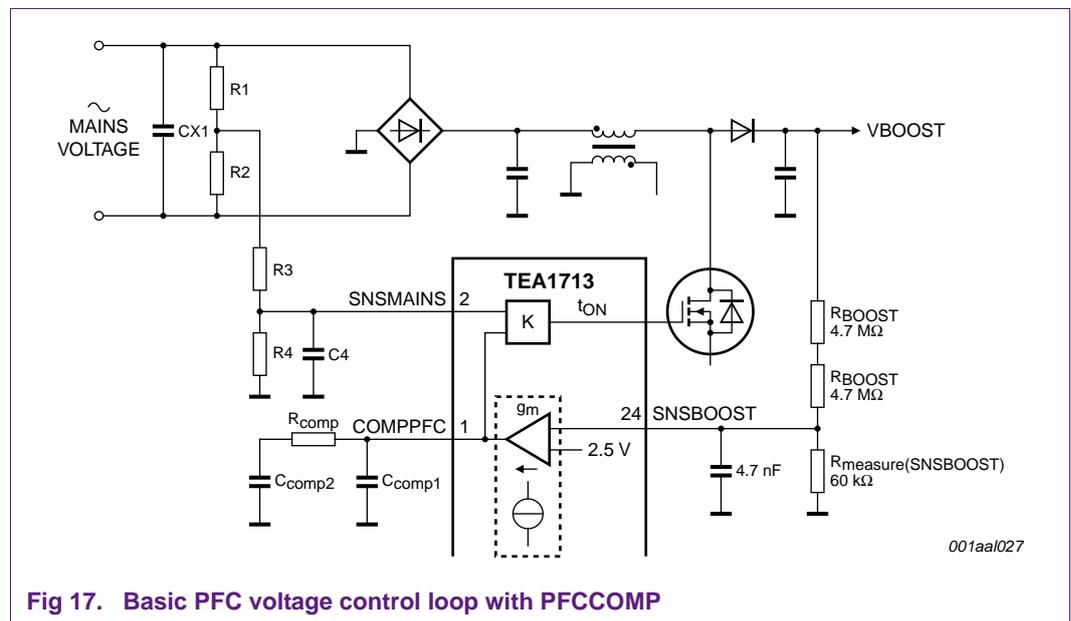


Fig 17. Basic PFC voltage control loop with PFCCOMP

The transfer function has a pole at 0 Hz, a zero by  $R_{comp}/C_{comp2}$  and a pole again by  $C_{comp1}/C_{comp2}$ . Set the zero frequency to 10 Hz while the next pole frequency is at 40 Hz. The zero point and pole frequencies of the compensation network can be calculated as follows:

$$f_z = \frac{1}{2\pi \times R_{comp} \times C_{comp2}} \tag{8}$$

$$f_p = \frac{C_{comp1} + C_{comp2}}{2\pi \times R_{comp} \times C_{comp1} \times C_{comp2}} \tag{9}$$

The choice also concerns a trade-off between power factor and transient behavior. A lower regulation bandwidth leads to a better power factor but the transient behavior becomes poorer. A higher regulation bandwidth leads to a better transient response but a poorer power factor.


**7.2.4 Mains compensation in the PFC voltage control loop**

The mathematical equation for the transfer function of a power factor corrector, contains the square of the mains input voltage.

$$K(V_{mains}) = \frac{A}{V_{mains}^2} \tag{10}$$

In a typical application this results in a low bandwidth for low mains input voltages, while at high mains input voltages the MHR requirements can be hard to meet.

The TEA1713 contains a correction circuit to compensate for the mains input voltage influence. SNSMAINS measures the average mains voltage, which is used for internal compensation. [Figure 18](#) shows the relationship between the SNSMAINS voltage, COMPPFC voltage and the on-time. With this compensation it is possible to keep the regulation loop bandwidth constant over the complete mains input voltage range, yielding a fast transient response on load steps, while still complying with class-D MHR requirements.

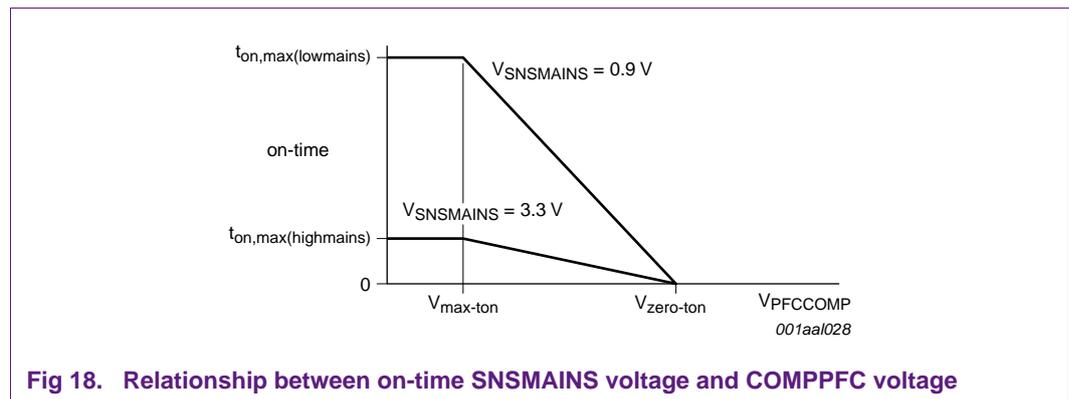

**Fig 18. Relationship between on-time SNSMAINS voltage and COMPPFC voltage**

**7.3 PFC demagnetization and valley sensing**

The PFC MOSFET is switched on for the next stroke, if the voltage at the drain of the MOSFET is at its minimum (valley switching), to reduce switching losses and EMI (see [Figure 19](#)).

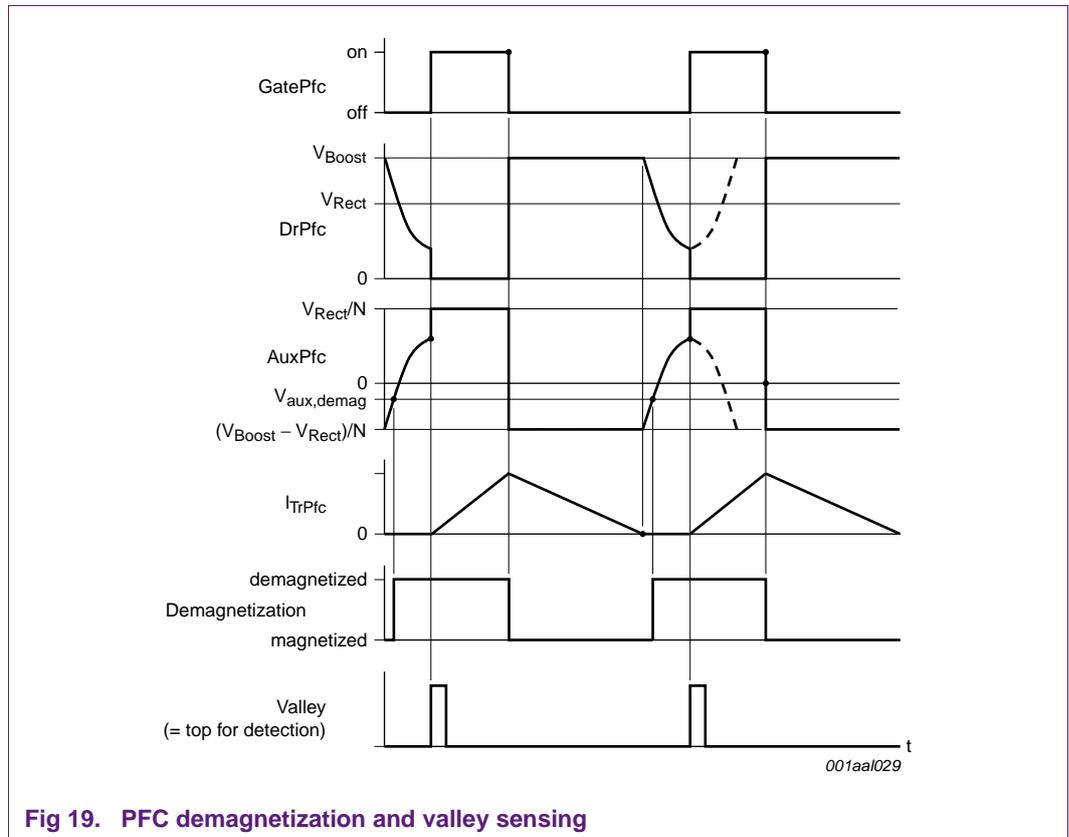


Fig 19. PFC demagnetization and valley sensing

SNSAUXPFC detects the valleys. An auxiliary winding on the PFC coil provides a measurement signal on SNSAUXPFC. It gives a reduced and inverted copy of the MOSFET drain voltage. When a valley of the drain voltage (top at SNSAUXPFC voltage) is detected, the MOSFET is switched on.

If no top (valley at the drain) is detected on SNSAUXPFC within 4 μs after demagnetization is detected, the MOSFET is forced to switch on.

### 7.3.1 PFC auxiliary sensing circuit

Add a 5 kΩ series resistor to SNSAUXPFC to protect the internal circuit of the IC against excessive voltage, for example during lightning surges. In the PCB layout, place this resistor close to the IC to prevent disturbances causing incorrect switching.

It is important to maintain valley detection even at low ringing amplitudes. Set the voltage at the SNSAUXPFC as high as possible, while taking into account its absolute maximum rating of ±25 V.

The number of turns of the auxiliary winding on the PFC coil can be calculated using the following equation:

$$N_{aux(max)} = \frac{V_{SNSAUXPFC}}{V_{Lmax}} \times N_p = \frac{25 \text{ V}}{415} \times 52 = 3.13 \rightarrow 3 \text{ turns} \tag{11}$$

Where:

- $V_{\text{SNSAUXPFC}}$  is the absolute maximum voltage rating
- $V_{L\text{max}}$  is the maximum voltage across the PFC primary winding
- $N_P$  is the number of turns on the PFC coil (for this example, a value of 52 is used)

The boost output voltage at OverVoltage Protection (OVP) determines the maximum voltage across the PFC primary winding and can be calculated using the following equation:

$$V_{L\text{max}} = \frac{V_{\text{OVP}(\text{SNSBOOST})}}{V_{\text{reg}(\text{SNSBOOST})}} \times V_{\text{BOOST}} = \frac{2.63 \text{ V}}{2.5 \text{ V}} \times 394 \text{ V} = 415 \text{ V} \quad (12)$$

In this example, a design value of 394 V is used for nominal  $V_{\text{BOOST}}$ .

When a PFC coil with a higher number of auxiliary turns is used, a resistor voltage divider can be placed between the auxiliary winding and SNSAUXPFC. The total resistive value of the divider must be less than 10 kΩ to prevent delay of the valley detection in combination with parasitic capacitances.

### 7.3.2 PFC frequency limit

The switching frequency is limited to 125 kHz to minimize the switching losses. If the frequency for quasi-resonant operation is above the 125 kHz limit, the system switches over to Discontinuous conduction mode. The PFC MOSFET is only switched on at a minimum voltage across the switch (valley switching). One or more valleys are skipped, when necessary, to keep the frequency below 125 kHz (valley skipping).

The minimum off-time is limited to 50 μs after the last PFC gate signal to ensure proper control of the PFC MOSFET under all circumstances.

## 7.4 PFC OverCurrent Regulation/Protection (OCR/OCP)

The maximum peak current, switched by the external MOSFET, is limited cycle-by-cycle by sensing the voltage across a measurement resistor  $R_{\text{SENSE(PFC)}}$  in the source of the MOSFET. SNSCURPFC measures the voltage, which is limited to 0.5 V. At this voltage level the MOSFET is switched off.

Take a small voltage margin into account to avoid false triggering of the OCP.

The value of the measurement resistor  $R_{\text{SENSE(PFC)}}$  can be calculated with [Equation 13](#):

$$R_{\text{SENSE(PFC)}} = \frac{V_{\text{OCR}(\text{SNSCURPFC})} - V_{\text{margin}}}{I_{P\text{max}}} = \frac{0.52 \text{ V} - 0.1 \text{ V}}{8.73 \text{ A}} = 48 \text{ m}\Omega \quad (13)$$

The SNSCURPFC voltage senses an initial voltage peak at the moment the PFC MOSFET switches on, because its (parasitic) capacitances are discharged. SNSCURPFC has a leading edge blanking of 310 ns to mask this event, so it does not react to this initial peak.

7.4.1 PFC soft-start and soft-stop

The PFC has a soft-start function and a soft-stop function to prevent transformer noise/rattle at start-up or during Burst mode operation. The soft-start slowly increases the primary peak current at the start of operation. The soft-stop function slowly decreases the transformer peak current before operation is stopped.

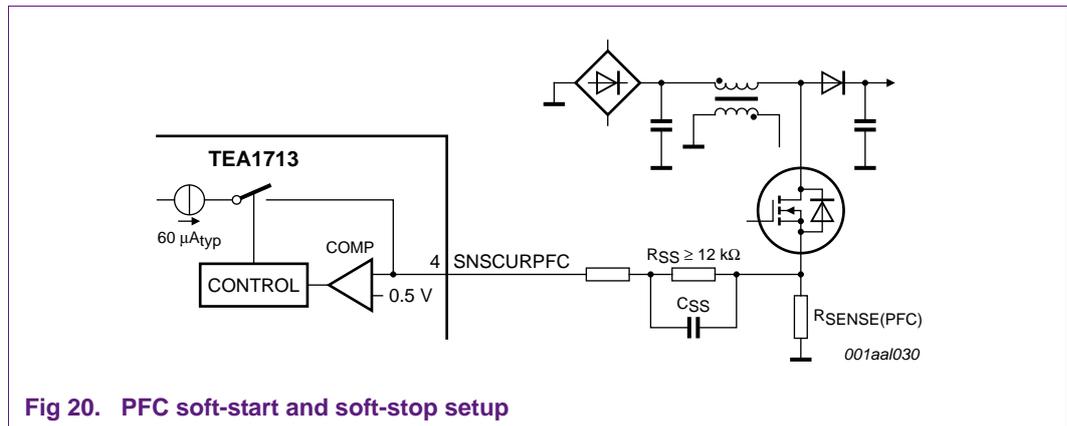


Fig 20. PFC soft-start and soft-stop setup

A resistor and a capacitor between SNSCURPFC and the current sense resistor  $R_{SENSE(PFC)}$  set both functions.

7.4.1.1 Soft-start

Before start of operation, an internal current source of  $60 \mu A$  charges the capacitor to  $V_{SNSCURPFC} = 60 \mu A \times R_{SS}$ . When SNSCURPFC exceeds the internal start voltage of 0.5 V, the operation can start. Select a resistor  $R_{SS} \geq 12 k\Omega$  to ensure that the start voltage level is reached. At start-up, the current source is stopped and the voltage on SNSCURPFC drops as  $R_{SS}$  discharges  $C_{SS}$ . During this discharge the peak current of each cycle increases until  $C_{SS}$  is discharged completely and the normal peak current regulation level (OCR/OCP), set by  $R_{SENSE(PFC)}$ , is reached.

The soft-start period can be calculated with [Equation 14](#):

$$\tau = R_{SS} \times C_{SS} \tag{14}$$

7.4.1.2 Soft-stop

Soft-stop is achieved by switching on the internal current source of  $60 \mu A$  again.

The current charges  $C_{SS}$  and the increasing capacitor voltage reduces the peak current. When SNSCURPFC reaches 0.5 V the operation is stopped.

The voltage is only measured during the off-time of the PFC power switch to prevent measurement disturbances during soft-stop.

7.4.2 SNSCURPFC open and short protection

When the SNSCURPFC pin is open, SNSCURPFC is charged to 0.5 V by the internal current source of  $60 \mu A$  for soft-start. The PFC does not start switching because of OCP.

When the SNSCURPFC pin is short circuit to ground, the PFC cannot start operation as the start level of 0.5 V has not been reached.

### 7.5 PFC boost OverVoltage Protection (OVP)

An overvoltage protection circuit is built in to prevent boost overvoltage during load steps and mains transients. When the voltage on SNSBOOST exceeds 2.63 V, the switching of the power factor correction circuit is stopped. The PFC resumes switching when the voltage on SNSBOOST drops below 2.63 V.

When the resistor between pin SNSBOOST and ground is open, the overvoltage protection also triggers. In this situation, an internal current source of 45 nA to ground can increase the voltage on SNSBOOST to the OVP protection level.

The voltage value at which PFC OVP becomes active can be calculated with the following equation:

$$V_{OVP(BOOST)} = \frac{V_{OVP(SNSBOOST)}}{V_{reg(SNSBOOST)}} \times V_{BOOST} = \frac{2.63 \text{ V}}{2.5 \text{ V}} \times 394 \text{ V} = 415 \text{ V} \tag{15}$$

In the example, a design value of 394 V is used for nominal  $V_{BOOST}$ .

### 7.6 PFC mains UnderVoltage Protection (brownout protection)

The voltage on the SNSMAINS pin is sensed continuously to prevent the PFC operating at very low mains input voltages. When the voltage on this pin drops below 0.89 V, the switching of the PFC is stopped. This mains undervoltage protection is sometimes referred to brownout protection.

The voltage on pin SNSMAINS must be an average DC value that represents the mains input voltage. The system works best with a time constant of approximately 150 ms for pin SNSMAINS. When the voltage on SNSMAINS drops, it is internally clamped to a value of 1.05 V, which is 0.1 V below the start level of 1.15 V for SNSMAINS. This allows a fast restart when the mains input voltage returns after a mains-dropout. The PFC (re)starts when the SNSMAINS voltage exceeds the start level of 1.15 V.

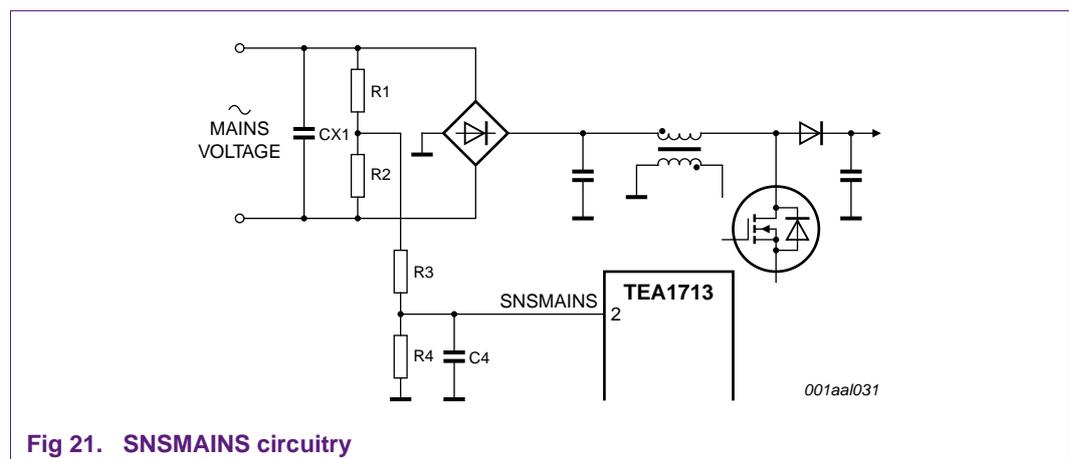


Fig 21. SNSMAINS circuitry

### 7.6.1 Undervoltage or brownout protection level

The AC input voltage is measured via R1 and R2. Each resistor alternately senses half the sine cycle and as a result, both resistors have the same value.

A typical resistor value of 2 MΩ can be applied for R1 and R2 to keep the bleeder loss low.

The average voltage sensed is calculated as follows:

$$V_{AC\ average} = \frac{2\sqrt{2}}{\pi} \times V_{AC\ rms} \quad (16)$$

The SNSMAINS brownout protection (RMS) voltage level is calculated with [Equation 17](#):

$$R_v = \frac{R1 \times R2}{R1 + R2} \quad (17)$$

$$V_{BO} = 2 \times \frac{\pi}{2\sqrt{2}} \times V_{SNSMAINS(UVP)} \times \left( \frac{R_v + R3}{R4} + I \right) \quad (18)$$

Example:

Required:  $V_{BO} = 66\text{ V (AC)}$ , with:

- $V_{SNSMAINS(UVP)} = 0.89\text{ V}$
- $R1 = R2 = 2\text{ M}\Omega \rightarrow R_v = 1\text{ M}\Omega$

$$V_{BO} = 2 \times \frac{\pi}{2\sqrt{2}} \times 0.89 \times \left( \frac{R_v + R3}{R4} + I \right) \quad (19)$$

$$66 = 1.9771 \times \left( \frac{1\text{ M}\Omega + R3}{R4} + I \right) \quad (20)$$

$R3 = 560\text{ k}\Omega$ ,  $R4 = 47\text{ k}\Omega$

The time constant for a recommended time constant of 150 ms, with  $C4 = 3300\text{ nF}$ :

$$t_{SNSMAINS} = R4 \times C4 = 47\text{ k}\Omega \times 3300\text{ nF} = 155\text{ ms}$$

### 7.6.2 Discharging the mains input capacitor

There is often an application requirement to discharge the X capacitors in the EMC input filtering within a certain time. The replacement values of R1, R2, R3 and R4 determine the resistance required for discharging the X capacitors in the input filtering. The replacement value can be calculated with [Equation 21](#):

$$R_{discharge} = R1 + \frac{R2 \times (R3 + R4)}{R2 + R3 + R4} \quad (21)$$

Example:

Required:  $t_{\text{discharge}} < 600 \text{ ms}$ , with:

- $R1 = R2 = 2 \text{ M}\Omega$
- $R3 = 560 \text{ k}\Omega$
- $R4 = 47 \text{ k}\Omega$

$$R_{\text{discharge}} = R1 + \frac{R2 \times (R3 + R4)}{R2 + R3 + R4} = 2 \text{ M}\Omega + \frac{2 \text{ M}\Omega \times (560 \text{ k}\Omega + 47 \text{ k}\Omega)}{2 \text{ M}\Omega + 560 \text{ k}\Omega + 47 \text{ k}\Omega} = 2465 \text{ k}\Omega \quad (22)$$

Where:

- $C = 220 \text{ nF}$
- The time constant equals:  $t_{\text{discharge}} = R_{\text{discharge}} \times C = 2465 \text{ k}\Omega \times 220 \text{ nF} = 542 \text{ ms}$

### 7.6.3 SNSMAINS open pin detection

The SNSMAINS pin, which senses the mains input voltage, has an integrated protection circuit to detect an open pin. When the pin is not connected, an internal current source of 33 nA either pulls the pin down below the stop level of 0.9 V or keeps it below the start level of 1.15 V.

When the SNSMAINS pin is shorted to ground, the results are similar.

## 8. HBC functions

### 8.1 HBC UVP boost

The TEA1713 begins operation when the input voltage is higher than approximately 90 % of the nominal boost voltage to ensure proper working of the HBC.

The voltage on the SNSBOOST pin is sensed continuously. When the voltage on SNSBOOST drops below 1.6 V, switching of the HBC is stopped when the low-side MOSFET is on. The HBC (re)starts when the SNSBOOST voltage exceeds the start level of 2.3 V.

### 8.2 HBC switch control

The internal control for the MOSFET drivers, determines when the MOSFETs are switched on and off. It uses the input from several functions.

1. An internal divider is used to provide the alternating switching of high-side and low-side MOSFET for every oscillator cycle.
2. The adaptive non-overlap (see [Section 8.3](#)) sensing on HB determines the switch-on moment.
3. The oscillator (see [Section 8.4](#)) determines the switch-off moment.
4. Several protection and enable functions determine if the resonant converter is allowed to switch.

### 8.3 HBC adaptive non-overlap

#### 8.3.1 Inductive mode (normal operation)

The high efficiency of a resonant converter is the result of Zero-Voltage Switching (ZVS) of the power MOSFETs, also called soft-switching. A small non-overlap time (also called dead time) is required between the on-time of the high-side MOSFET and low-side MOSFET to allow soft-switching. During this non-overlap time, the primary resonant current (dis)charges the capacitance of the half-bridge between ground and boost voltage. After the (dis)charge, the body diode of the MOSFET starts conducting and because the voltage across the MOSFET is zero, there are no switching losses.

This mode of operation is called Inductive mode because the switching frequency is above the resonance frequency and the resonant tank has an inductive impedance.

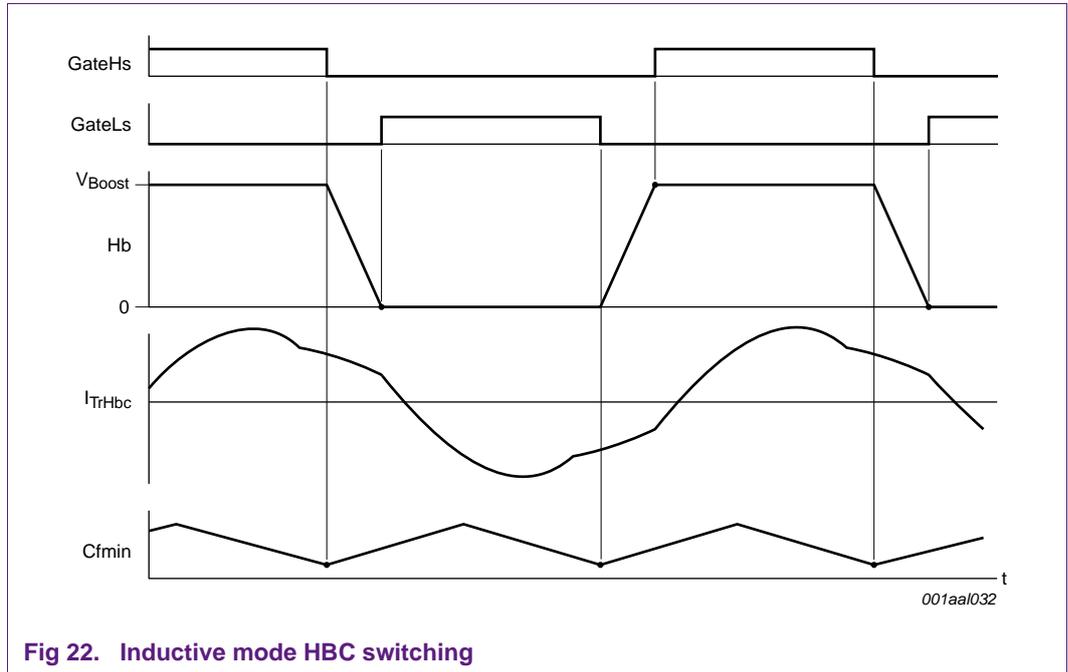


Fig 22. Inductive mode HBC switching

The time required for the transition of the HB depends on the amplitude of the resonant current at the moment of switching. There is a (complex) relationship between the amplitude, the frequency, the boost voltage and the output voltage. Ideally the IC switches on the MOSFET when the transition of the HB has reached its end value. It must not wait longer, especially at high output load, to prevent a swing back of the HB voltage.

The adaptive non-overlap function of the TEA1713 provides an automatic measurement and control function that decides when to switch on. As it uses actual measurement input the control adapts for operation changes in time.

Because of this adaptive non-overlap function, it is not necessary to preset a fixed non-overlap time, which is always a compromise between different operating conditions.

The adaptive non-overlap function senses the slope at HB after one MOSFET has been switched off. Normally, the slope at the HB starts directly. Once the transition of the HB node is complete, the slope ends. This is detected by the adaptive non-overlap sensing and the other MOSFET is switched on. In this way the non-overlap time is automatically adjusted to the best value providing the lowest switching loss, even if the HB transition cannot be fully completed.

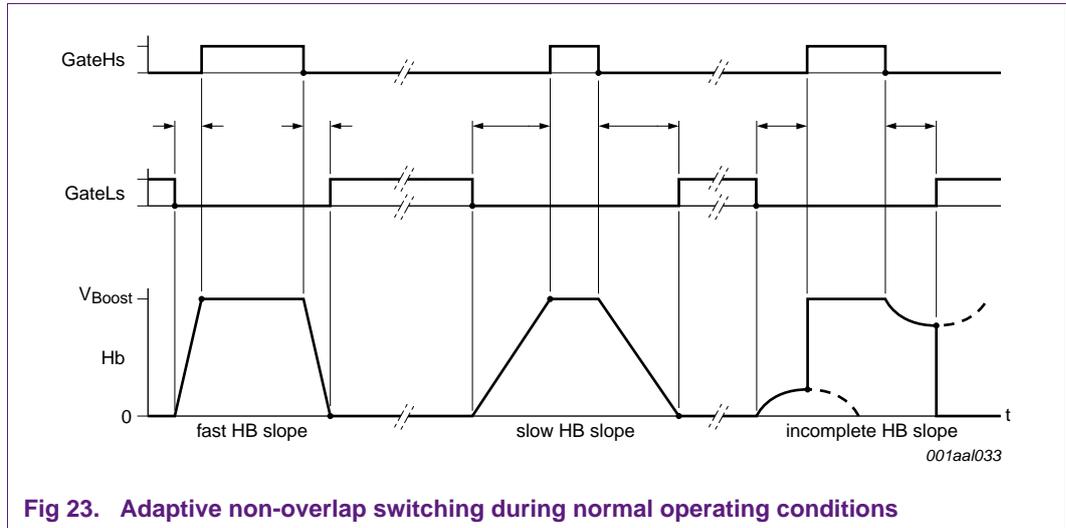


Fig 23. Adaptive non-overlap switching during normal operating conditions

The non-overlap time depends on the HB slope, but has an upper and lower time limit. An integrated minimum non-overlap time ( $160 \text{ ns}_{\text{max}}$ ) prevents accidental cross conduction in all conditions. The maximum non-overlap time is limited to the charging time of the oscillator. If the HB slope takes more time than the charging of the oscillator (25 % of HB switching period) the MOSFET is forced to switch on. In this case the MOSFET is not soft-switching. This limitation of the maximum non-overlap time ensures that at high switching frequency the on-time of the MOSFET is at least 25 % of the HB switching period.

### 8.3.2 Capacitive mode

During error conditions (e.g. output short circuit, load pulse too high) or special start-up conditions, the switching frequency can become lower than the resonance frequency. The resonant tank then has a capacitive impedance. In Capacitive mode the HB slope does not start after the MOSFET has switched off. It is not preferred to just switch on the other MOSFET. The lack of soft-switching increases dissipation in the MOSFETs. The conducting body diode in the MOSFET at the switching moment can damage or even destroy the device quickly.

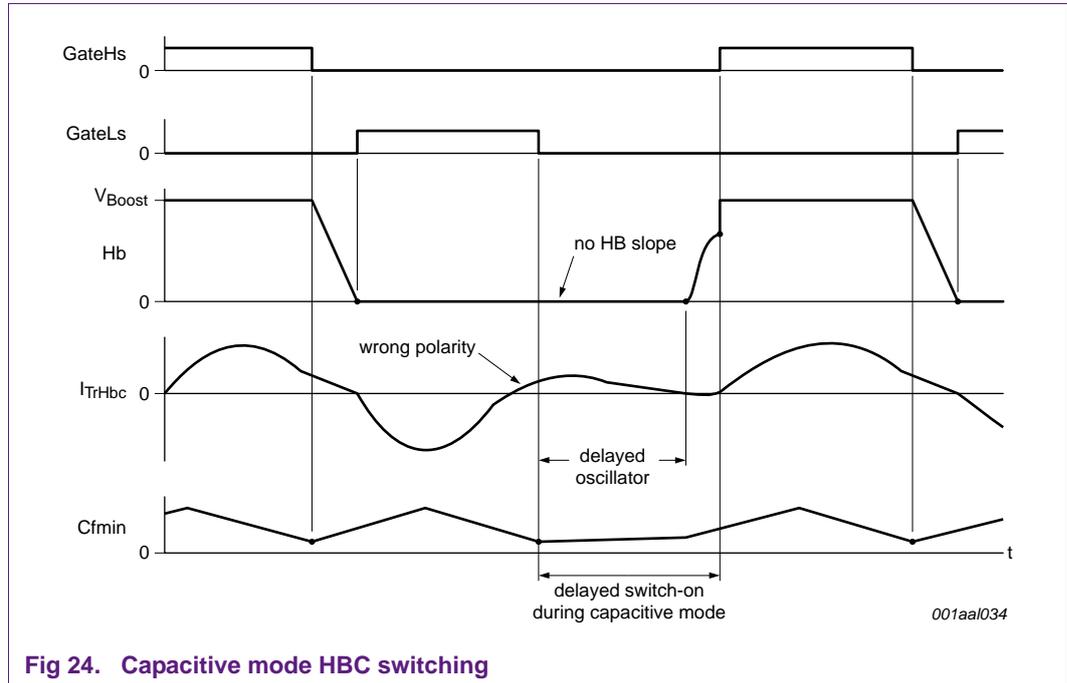


Fig 24. Capacitive mode HBC switching

The adaptive non-overlap system of the TEA1713 always waits until the slope at the half-bridge node starts. It guarantees safe/best switching of the MOSFETs in all circumstances. In Capacitive mode, it can take half the resonance period before the resonant current changes back to the correct polarity and starts charging the half-bridge node. The oscillator remains in its slow charging current mode until the half-bridge slope starts to allow this relatively long waiting time (see also [Section 8.4.2](#) and [Figure 28](#)).


The MOSFET is forced to switch on when the half-bridge slope does not start at all and the slowed-down oscillator reaches the high level.

The Capacitive Mode Regulation (CMR) function increases the oscillation frequency to bring the converter from Capacitive mode to Inductive mode operation again.

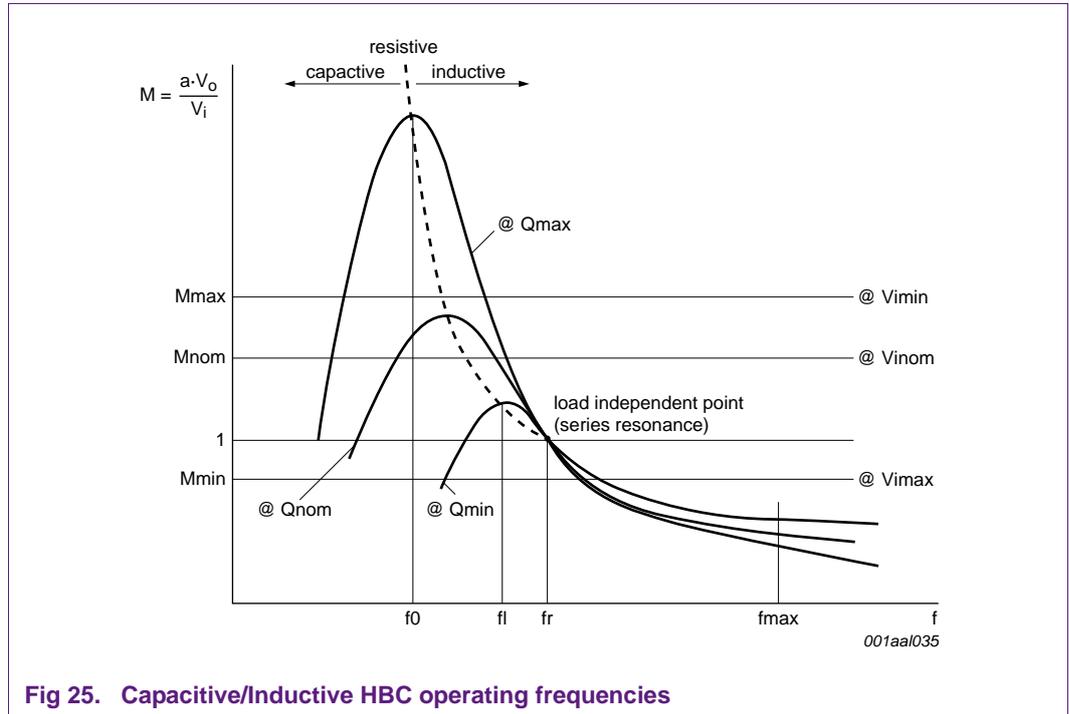
### 8.3.3 Capacitive Mode Regulation (CMR)

The adaptive non-overlap function prevents the harmful switching in Capacitive mode. However, an extra action is executed, which results in the CMR to end the Capacitive mode operation and return to Inductive mode operation.

Capacitive mode is detected when the HB slope does not start shortly (690 ns) after the MOSFET is switched-off. At detection of Capacitive mode, the switching frequency is increased quickly. This is realized by discharging SSHBC/EN with a high current (1800  $\mu$ A) from the moment  $t_{no-slope} = 690$  ns has passed before the half-bridge slope starts. The resulting frequency increase regulates the HBC back to the border between Capacitive mode and Inductive mode.



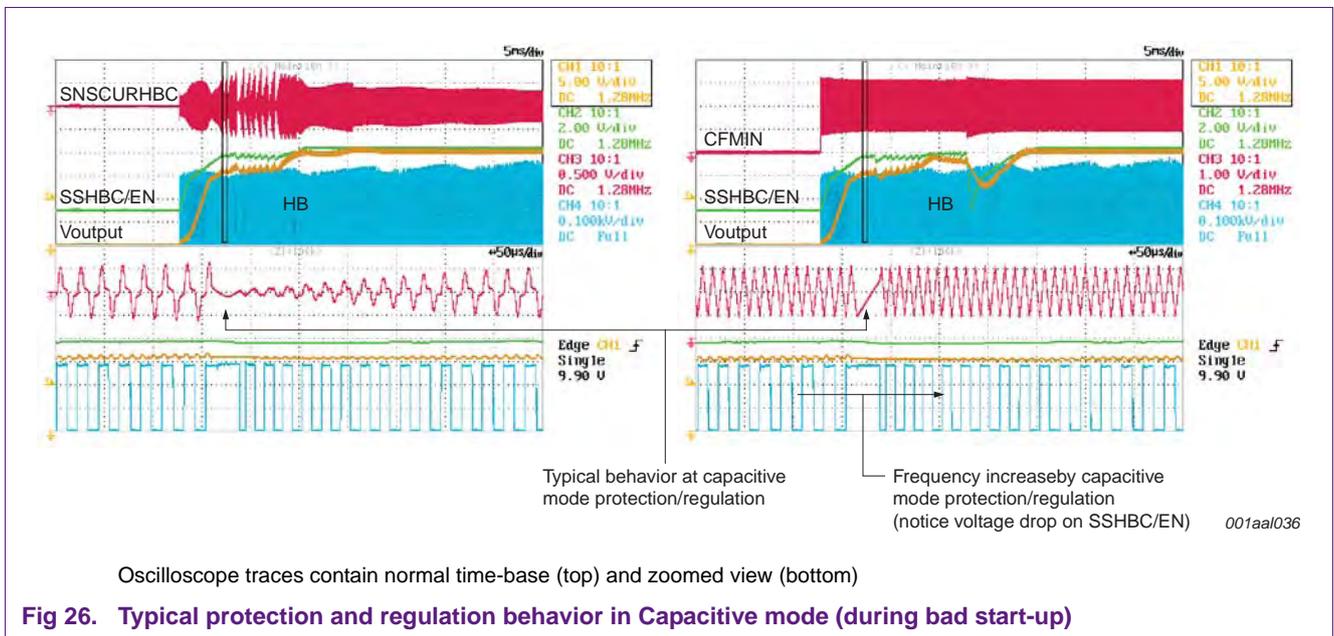CMR of the TEA1713 can be recognized by the typical slowing of the oscillator in combination with the discharging of SSHBC/EN.



### 8.4 HBC oscillator

The slope controlled oscillator determines the switching frequency of the half-bridge. The oscillator generates a triangular waveform at the external capacitor  $C_{fmin}$ .

#### 8.4.1 Presettings

Two external components determine the frequency range:

- Capacitor at CFMIN  
Sets the minimum frequency in combination with an internally trimmed current source.
- Resistor at RFMAX  
Sets the frequency range and, in combination with CFMIN, the maximum frequency.

The oscillator frequency depends on the charge and discharge current of the capacitor on CFMIN. This (dis)charge current consists of a fixed part which determines the minimum frequency, and a variable part which depends on the value of the resistor on RFMAX and the voltage at pin RFMAX.

- The voltage on RFMAX is 0 V when the oscillator frequency is minimum.
- The voltage on RFMAX is 2.5 V when the oscillator frequency is maximum.
- The value of the resistor on RFMAX determines the relationship between VRFMAX and the frequency. It also determines the maximum frequency when  $RFMAX = 2.5\text{ V}$ .

The maximum frequency of the oscillator is independent of the settings on CFMIN and RFMAX and is limited internally to a minimum of 500 kHz. Figure 27 shows the relationship between VRFMAX and  $f_{HB}$  for three different values of  $C_{fmin}$  and  $R_{fmax}$ .

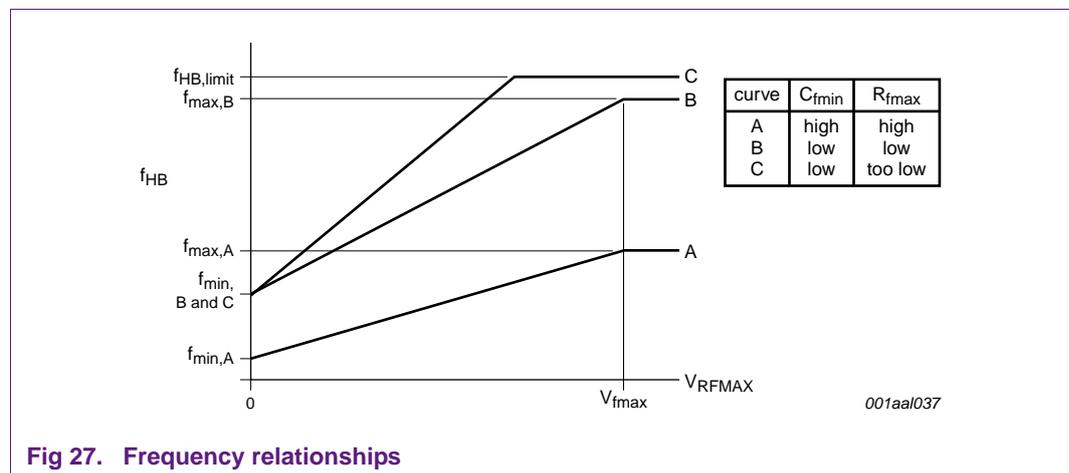


Fig 27. Frequency relationships

#### 8.4.2 Operational control

During operation, the state of the half-bridge node HB controls the oscillator. An internal slope detection circuit monitors the voltage on HB to achieve this.

The charge current of the oscillator is initially set to a low value of 30  $\mu\text{A}$ . After the start of the half-bridge slope has been detected, the charge current is increased to the normal value that corresponds to the working frequency at that moment. Feedback on SNSFB controls the working frequency. Normally, the half-bridge slope starts directly after the switch-off of the MOSFET, the time with the low oscillator current (30  $\mu\text{A}$ ) being negligible.

The similarity between GATELS and GATEHS when switching, is that the oscillator signal determines the moment of switching off. The HB sensing circuit determines the moment of switching on.

As the HB sensing (and therefore not fixed) determines the moment of switching on, the time between switching one MOSFET off and the other one on, is adaptive: adaptive non-overlap time (or dead time). This non-overlap time has no influence on the oscillator signal.

The frequency control by oscillator-frequency consists of determining the time between two moments of switching off (including a small period in which the oscillator current is only 30  $\mu\text{A}$ ).



### 8.4.3 CFMIN and RFMAX

This section explains the method of calculating the values for the capacitor on CFMIN and the resistor on RFMAX.

#### 8.4.3.1 Minimum frequency setting for CFMIN

$$f_{oscillator} = 2 \times f_{HB} \tag{23}$$

$$t_{charge} \approx t_{discharge} \approx \frac{t_{oscillator}}{2} \tag{24}$$

$$\Delta V_{oscillator} = V_{high(CFMIN)} - V_{low(CFMIN)} = 3\text{ V} - 1\text{ V} = 2\text{ V} \tag{25}$$

$$I_{oscillator(min)} = 150\ \mu\text{A} \tag{26}$$

$$CFMIN = \frac{I_{oscillator(min)}}{2 \times 2 \times f_{HB(min)} \times \Delta V_{oscillator}} = \frac{150 \mu A}{8 \times f_{HB(min)}} \quad (27)$$

Example:

Requirement:  $f_{HB(min)} = 57 \text{ kHz}$

$$CFMIN = \frac{150 \mu A}{2 \times 2 \times 57 \text{ kHz} \times 2} = \frac{0.00015}{456000} = 329 \text{ pF} \quad (28)$$

#### 8.4.3.2 Maximum frequency setting for RFMAX

$$I_{oscillator(max)} = 4.7 \times I_{RFMAX(max)} + I_{oscillator(min)} \quad (29)$$

$$I_{RFMAX(max)} = \frac{V_{f(max)}}{RFMAX} \quad (30)$$

$$RFMAX = \frac{V_{f(max)}}{I_{RFMAX(max)}} = \frac{2.5 \text{ V}}{I_{RFMAX(max)}} \quad (31)$$

Analog to the situation with  $I_{oscillator(min)}$ :

$$f_{HB(max)} = \frac{I_{oscillator(max)}}{4 \times CFMIN \times \Delta V_{oscillator}} = \frac{4.7 \times I_{RFMAX(max)} + I_{oscillator(min)}}{4 \times CFMIN \times 2} \quad (32)$$

$$I_{RFMAX(max)} = \frac{8 \times CFMIN \times f_{HB(max)} - I_{oscillator(min)}}{4.7} \quad (33)$$

$$I_{RFMAX(max)} = \frac{8 \times CFMIN \times f_{HB(max)} - 150 \mu A}{4.7} \quad (34)$$

$$RFMAX = \frac{2.5 \text{ V}}{I_{RFMAX(max)}} = \frac{11.75}{8 \times CFMIN \times f_{HB(max)} - 150 \mu A} \quad (35)$$

Example:

Requirement:  $f_{HB(max)} = 180 \text{ kHz}$  and  $CFMIN = 330 \text{ pF}$

$$I_{RFMAX(max)} = \frac{8 \times 330 \text{ pF} \times 180 \text{ kHz} - 150 \mu A}{4.7} = \frac{(475 \mu A - 150 \mu A)}{4.7} = 69.15 \mu A \quad (36)$$

$$RFMAX = \frac{2.5 \text{ V}}{69.15 \mu A} = 36 \text{ k}\Omega \quad (37)$$

**Remark:** The average multiplication factor is 4.7. There is a small deviation in value depending on other parameters and presetting conditions. Practical verification of the result is advised.

#### 8.4.4 RFMAX and High Frequency Protection (HFP)

Normally, the converter does not operate continuously at the preset maximum frequency. This maximum frequency is only used for a short time during soft-start or temporary fault/overload conditions.

When the operating frequency remains at, or close to, maximum frequency for a longer period, a fault condition is assumed and a protection activated.

The HFP senses the voltage at pin RFMAX. This voltage indicates the actual operating frequency. When the frequency is higher than approximately 75 % of the frequency range (RFMAX = 1.83 V), the protection timer is started.

**Remark:** During normal regulation, the maximum frequency leads to only 60 % of the present range and the voltage at pin RFMAX is 1.5 V maximum.

### 8.5 HBC feedback (SNSFB)

A typical power supply application contains mains insulation in the HBC. On the secondary (mains insulated) side, the output voltage is compared to a reference and amplified. The TEA1713 is normally placed on the primary side. The output of the error amplifier is transferred to the primary side via an OPTO coupler. The output of the OPTO coupler on the primary side can be connected directly to SNSFB.

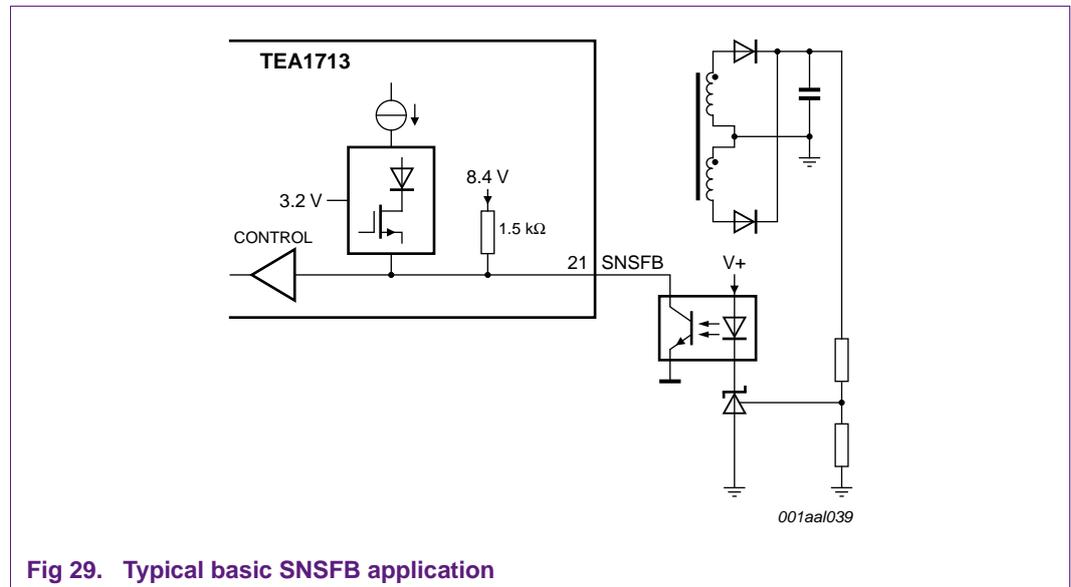


Fig 29. Typical basic SNSFB application

The SNSFB pin supplies the OPTO coupler from an internal voltage source of 8.4 V via an internal series resistor of 1.5 kΩ. This internal series resistance allows spike filtering by an external capacitor at the pin if needed.

The feedback input has a threshold current of 0.66 mA at which the frequency is minimum to ensure sufficient bias current for proper working of the opto coupler. The maximum frequency controlled by SNSFB is reached at 2.2 mA. This is approximately 60 % of the total preset frequency range. The remaining upper part of the frequency range can only be reached by control of SSHBC/EN for soft-start or protection.

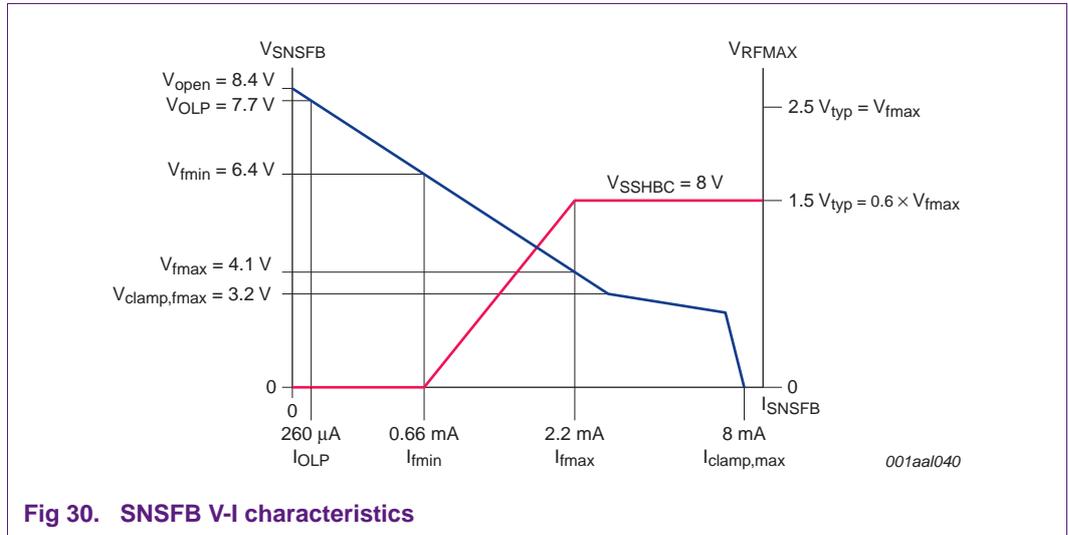


Fig 30. SNSFB V-I characteristics

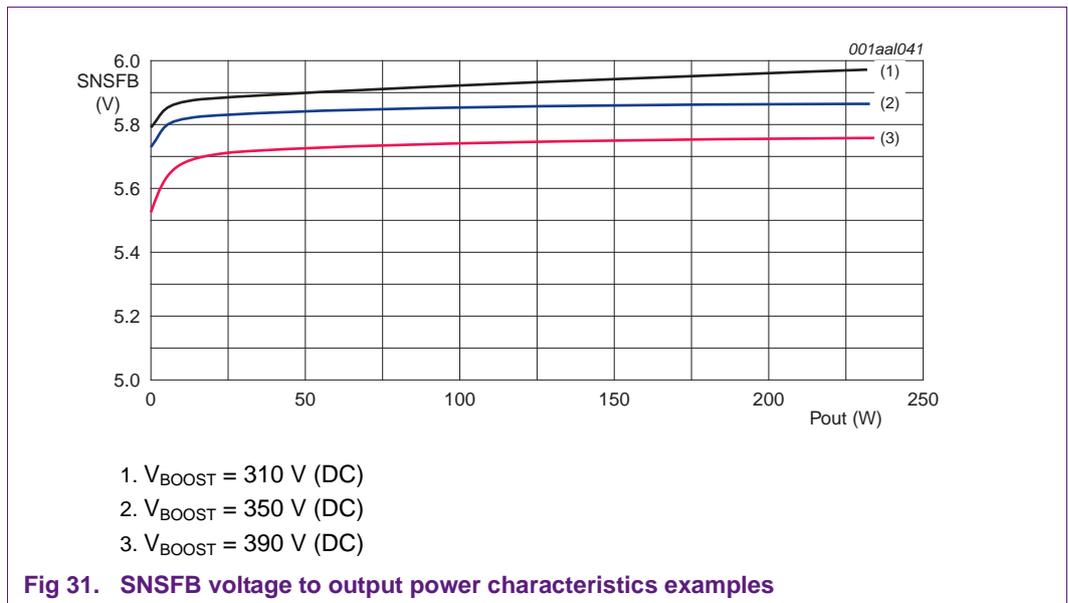


Fig 31. SNSFB voltage to output power characteristics examples

### 8.5.1 HBC Open-Loop Protection (OLP)

The resonant controller of the TEA1713 contains an Open-Loop Protection (OLP). This protection monitors the voltage on SNSFB. When it exceeds 7.7 V, the protection timer is started.

In normal operating conditions, the OPTO coupler current is between 0.66 mA and 2.2 mA which pulls down the voltage at pin SNSFB. Due to an error in the feedback loop, the current can become less than 260 μA which leads to an open-loop protection.


**8.6 SSHBC/EN soft-start and enable**

The SSHBC/EN pin provides the following three functions:

- It enables the PFC (> 1.2 V) and PFC plus HBC (> 2.2 V)
- It performs an HBC frequency sweep during soft-start from 3.2 V to 8 V
- It provides frequency control during protection

Seven internal current sources operate the frequency control depending on the required action.

- Soft-start + OverCurrent Protection: high/low charge (160  $\mu$ A/40  $\mu$ A) + high/low discharge (160  $\mu$ A/40  $\mu$ A)
- Capacitive mode regulation: high/low discharge (1800  $\mu$ A/440  $\mu$ A)
- General: bias discharge (5 mA)

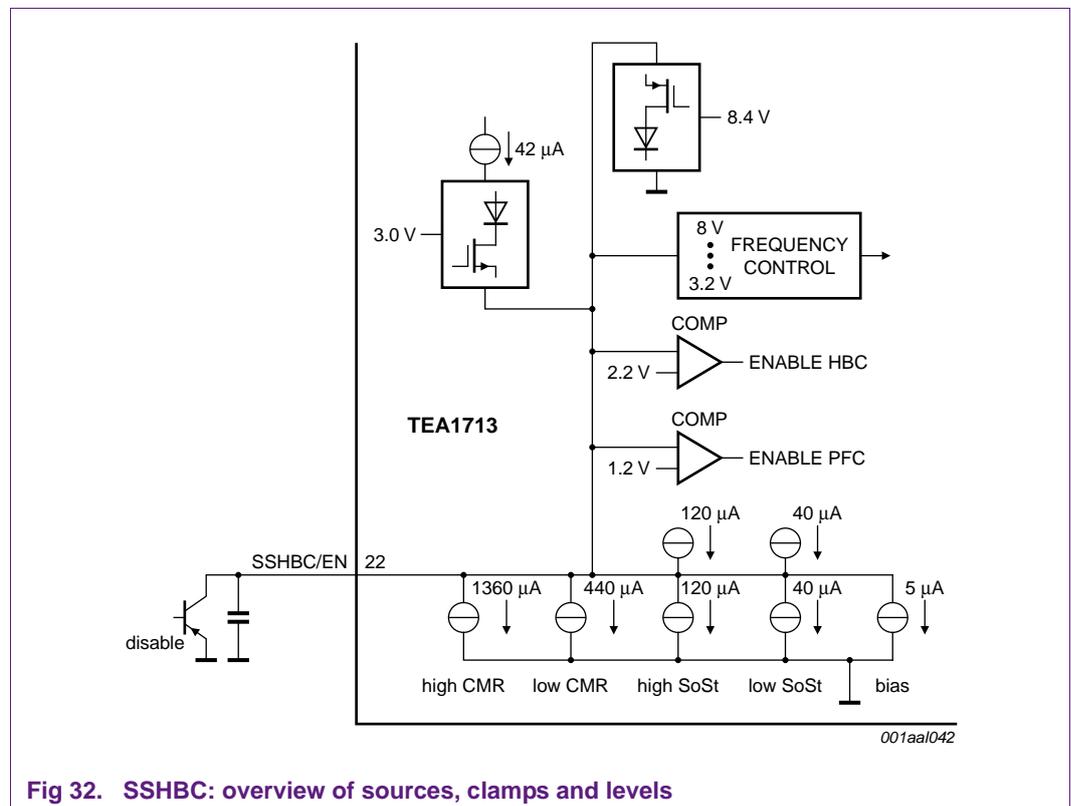

**Fig 32. SSHBC: overview of sources, clamps and levels**

**8.6.1 Switching ON and OFF using an external control function**

The SSHBC/EN can be used to switch the converters on and off using an external control function.

This function is often driven by a microcontroller from the secondary side of the OPTO coupler. The main power supply (PFC+HBC) can be switched off for Standby mode and switched on for normal operation. A separate standby supply must supply the microcontroller functions during Standby mode. It is also possible to switch/keep off the HBC and only have the PFC operational.

The TEA1713 also offers the possibility to switch on/off using the SNSOUT function. This function is intended for Burst mode operation where the duration of the on-states and off-states are short.

#### 8.6.1.1 Switching ON and OFF using SSHBC/EN

When a voltage is present at pin SUPHV or at pin SUPIC, a current from the SSHBC/EN pin charges the external capacitor. If the pin is not pulled-down, this current increases the voltage to 8.4 V. Since this is above the level to enable the operation of PFC (1.2 V) and PFC + HBC (2.2 V), the IC is completely enabled.

The IC can be completely disabled by pulling down the SSHBC/EN pin below 1.2 V. The PFC controller stops switching immediately, but the HBC continues until the low-side stroke is active. The pull-down current must be larger than the current capability from the internal soft-start clamp, i.e. 42  $\mu$ A.

##### PFC only active

By pulling the SSHBC/EN voltage below the enable PFC + HBC operation level (2.2 V), but keeping it above the enable PFC operating level (1.2 V), only the HBC is disabled. This can be used when there is another power converter connected to the boost voltage of the PFC. The low-side power switch of the HBC is on when the HBC is disabled via the SSHBC/EN pin.

##### HBC only active

The TEA1713 is not designed to provide this operation mode but it can be realized by forcing a voltage higher than 2.63 V (but below 5 V) on SNSBOOST. This way the output overvoltage protection of the PFC is activated and the PFC operation stopped (put on hold). The HBC operates because SNSBOOST exceeds its start level of 2.3 V (boost UVP).

This mode of operation is not likely to be required by an application, but it can be useful for starting up and debugging purposes during analyses or evaluation.

#### 8.6.1.2 Hold and continue

The SNSOUT function can be used to start and stop the PFC and HBC. This method is intended for Burst mode operation to switch off the converters for only a short time. It is possible to operate only the HBC in Burst mode or both HBC + PFC simultaneously. The possibilities are similar to SSHBC/EN with the main difference being that HBC continues without soft-start (see [Section 9.1](#)).

#### 8.6.2 Soft-start HBC

SSHBC/EN provides the soft-start function for the resonant converter.

The relation between switching frequency and output current/power is not constant. It is highly dependent on output and boost voltage and the relationship can be complex. The TEA1713 has a soft-start function to ensure that the resonant converter starts or restarts with safe currents.


The soft-start function forces a start at high frequency so that currents are acceptable in all conditions. The soft-start slowly decreases the frequency until the output voltage regulation has taken over the frequency control. The limitation of the output current during start-up also limits the output voltage rise and prevents an overshoot.

During soft-start, in parallel to the soft-start frequency sweep, the SNSCURHBC function monitors the primary current and can activate regulation in a (temporary) overpower situation.

The soft-start uses the voltage on pin SSHBC/EN. an external capacitor on SSHBC/EN sets the timing (duration) of the soft-start event.

As the SSHBC/EN is also used as enable input, the soft-start functionality is above the enable related voltage levels (see [Figure 33](#)).

**8.6.2.1 Soft-start voltage levels**

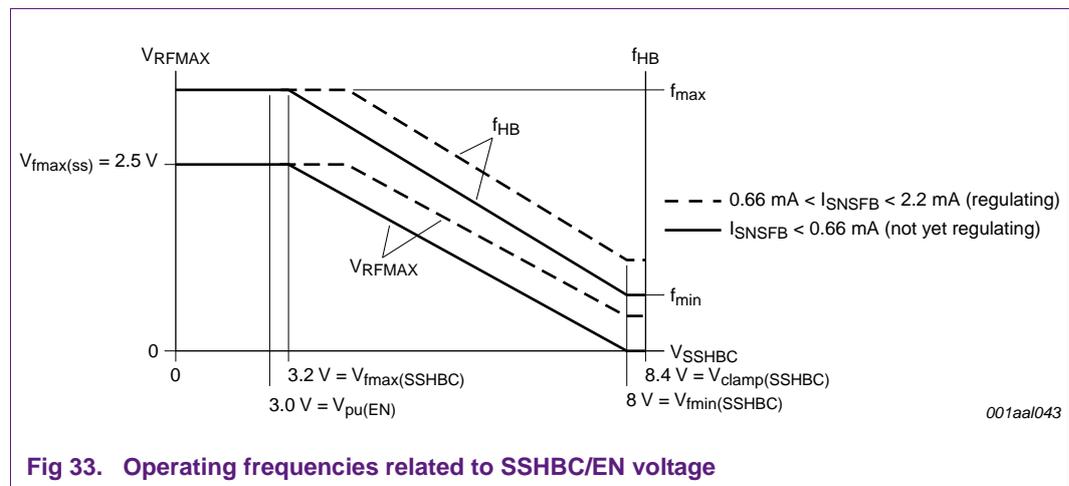

**Fig 33. Operating frequencies related to SSHBC/EN voltage**

At start-up, the SSHBC/EN voltage is low which corresponds to the maximum frequency. During the soft-start procedure, the external capacitor is charged, the SSHBC/EN voltage rises and the frequency decreases. The contribution of the soft-start function ends when SSHBC/EN is above 8 V.

The SSHBC/EN voltage is clamped at 8.4 V and remains at that level during normal operation.

When the voltage on SSHBC/EN is reduced during protection or regulation, the voltage is clamped at 3.0 V. This is to provide a quick response so that the operating frequency can be reduced again. Below 3.2 V the discharge current is reduced to 5  $\mu\text{A}$ .

**8.6.2.2 SSHBC/EN charge and discharge**

Initially, at start-up the soft-start external capacitor on SSHBC/EN is only charged to obtain a decreasing frequency sweep from maximum to operating frequency.

Besides the function to soft-start, SSHBC/EN is also used for regulation purposes such as overcurrent regulation. Therefore the voltage on the capacitor on SSHBC/EN can vary by charging and discharging it by internal current sources.

For example, in case of overcurrent regulation, a continuous alternation between charging and discharging of the SSHBC/EN capacitor occurs. The SSHBC/EN voltage can be regulated in this way overruling the signal on the feedback input SNSFB.

The (dis)charge current can have a high value  $\pm 160 \mu\text{A}$  or a low value  $\pm 40 \mu\text{A}$ . The two-speed soft-start sweep of the TEA1713 allows a combination of a short start-up time of the resonant converter and stable regulation loops such as overcurrent regulation.

In some cases there can be a situation where overcurrent regulation is activated during the soft-start sequence. This results in a feedback controlled or corrected soft-start.

The fast (dis)charge speed is used for the upper frequency range where  $V_{SSHBC/EN}$  is below 5.6 V. In the upper frequency range the current and power in the converter do not react strongly to frequency variations.

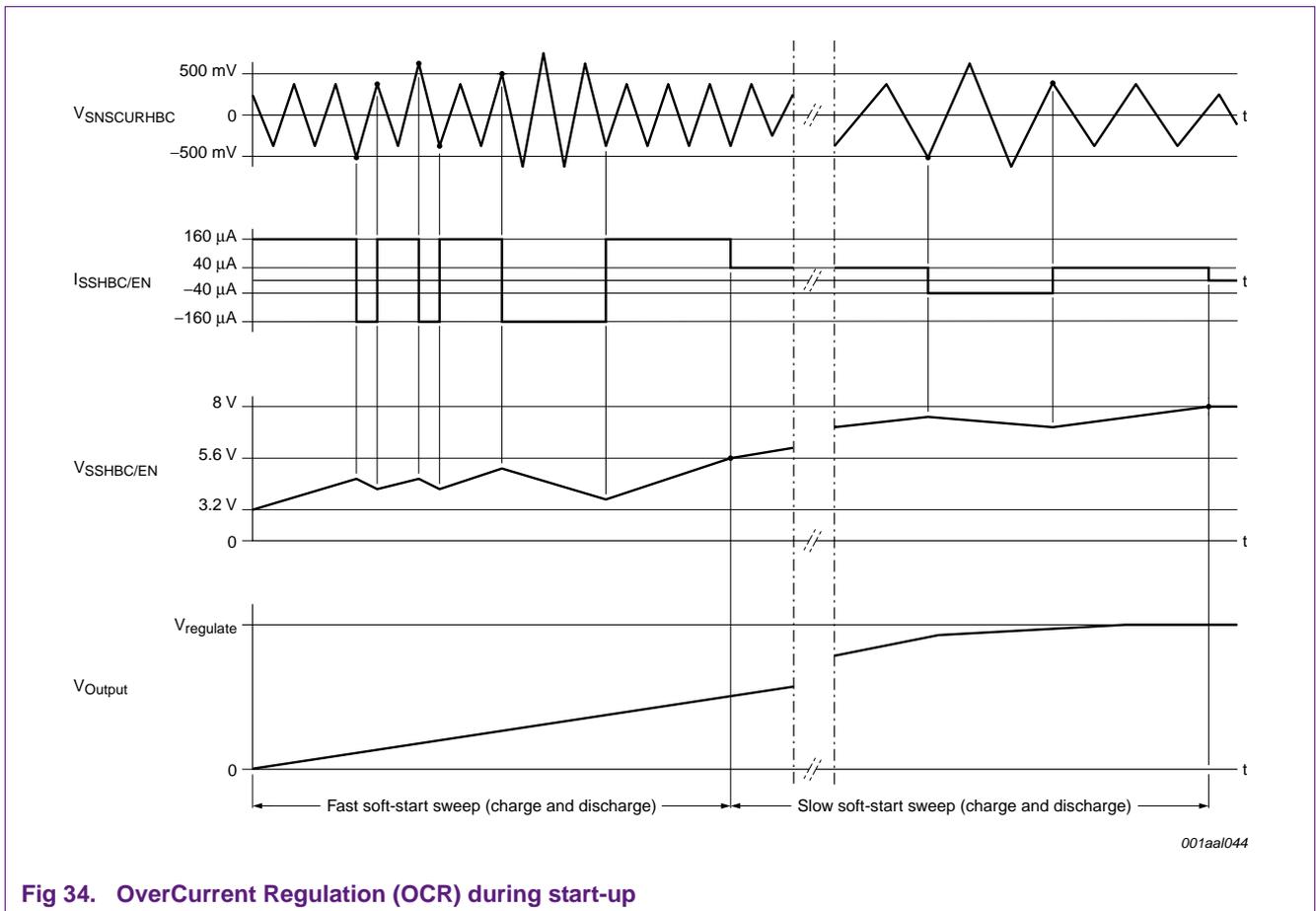


Fig 34. OverCurrent Regulation (OCR) during start-up

The slow (dis)charge speed is used for the lower frequency range where  $V_{SSHBC/EN}$  is above 5.6 V. In the lower frequency range the current in the converter reacts strongly to frequency variations.

**Burst mode**

The soft-start capacitor is not charged or discharged during the non-operation time in Burst mode operation. The soft-start voltage does not change during this time.


**8.6.2.3 SNSFB, SSHBC/EN and soft-start reset - operating frequency control**

the SNSFB and SSHBC/EN can simultaneously control the operating frequency. SSHBC/EN is dominant to provide protection and soft-start capability. Additionally, there is an internal soft-start reset mechanism that overrules both SNSFB and SSHBC/EN control inputs and immediately sets the frequency to maximum.

**8.6.2.4 Soft-start reset**

Some protections require a fast correction of the operating frequency to the maximum value, but they do not have to stop switching. The overcurrent protection is an example (see [Table 4](#)).

When this protection is activated, the control input of the oscillator is disconnected internally from the soft-start capacitor at pin SSHBC/EN and the switching frequency is immediately set to maximum. In most cases, the change to the maximum switching frequency restores safe switching operation. Once the voltage at pin SSHBC/EN has reached 3.2 V, the control input of the oscillator reconnects to the pin and the normal soft-start sweep follows. [Figure 35](#) shows the soft-start reset and the two-speed frequency downward sweep.

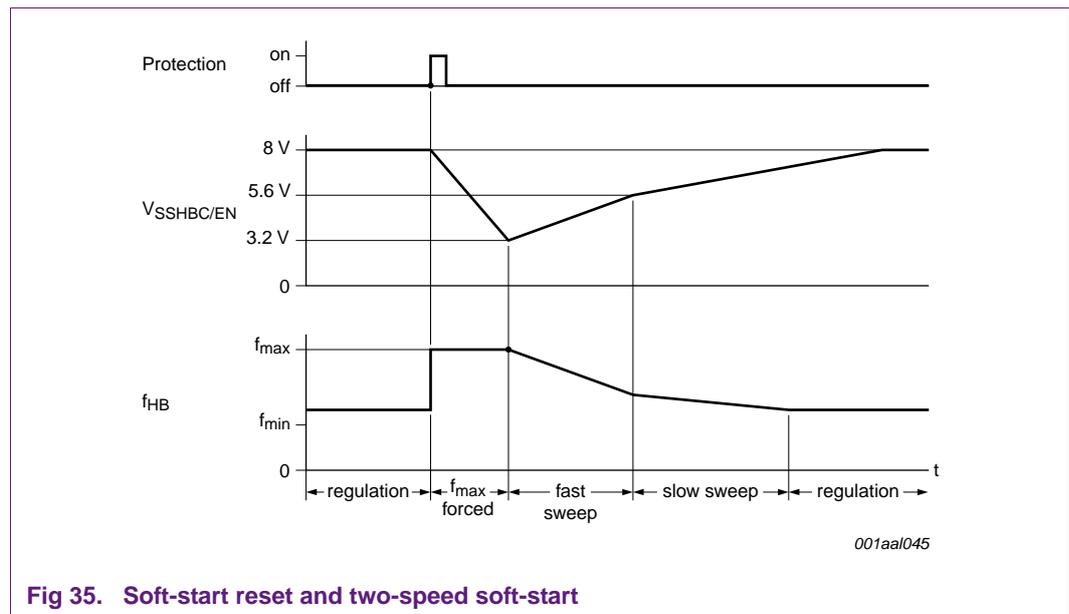

**Fig 35. Soft-start reset and two-speed soft-start**

The soft-start reset is also used to ensure a safe start-up at maximum frequency when the HBC is enabled by SSHBC/EN or after a restart. The soft-start reset is not used when the operation has been stopped for Burst mode.

8.7 HBC overcurrent protection and regulation

Measurement of the primary resonant current indicates the level of output power that is generated by the converter. During a fault or output overload condition, this current often increases considerable. By monitoring this current and then taking appropriate action, the converter can remain operational during a temporary fault or overload condition.

The resonant controller of the TEA1713 has two functions when in an overcurrent condition:

- OverCurrent Regulation (OCR) slowly increases the frequency and the protection timer is started
- OverCurrent Protection (OCP) steps to maximum frequency

A boost voltage compensation function is included to reduce the variation in the preset protection level of the resonant current.

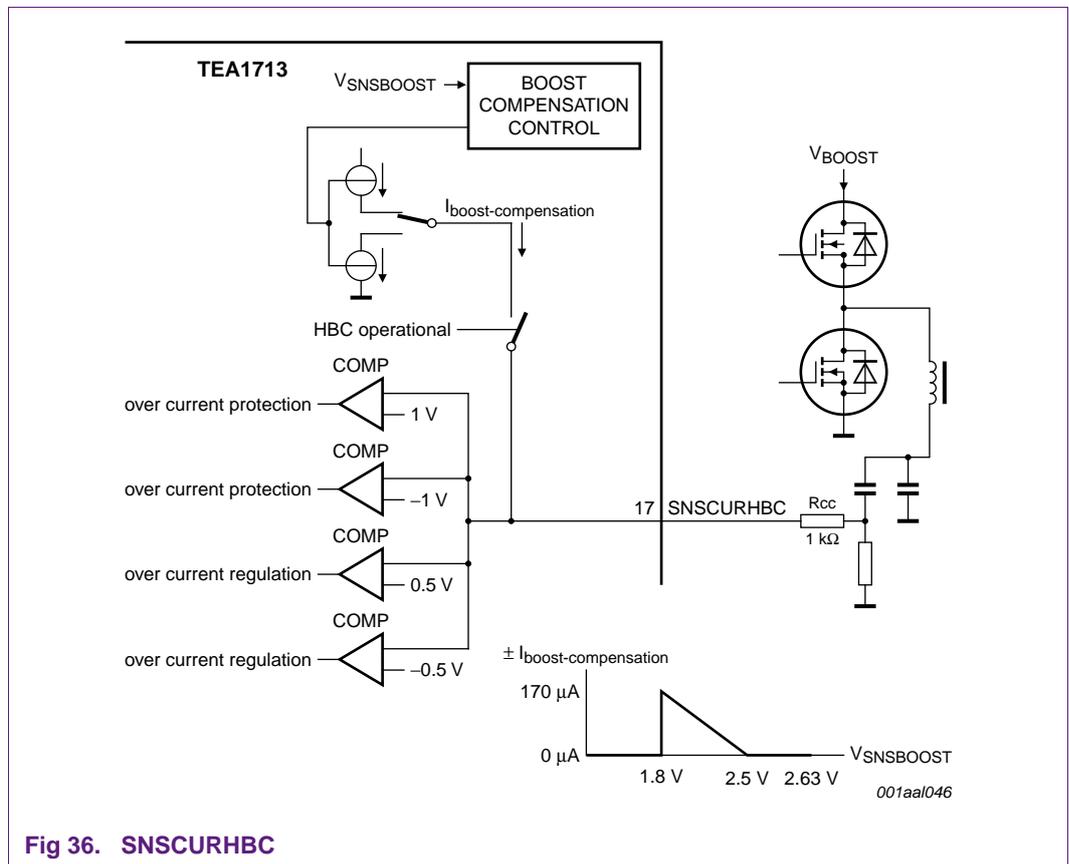


Fig 36. SNSCURHBC

8.7.1 HBC overcurrent regulation

The lowest comparator levels of  $\pm 0.5$  V at the SNSCURHBC pin belong to the OverCurrent Regulation (OCR) level. There is a comparator for both the positive and negative polarity. If either level is exceeded, the frequency is slowly increased. This is accomplished by discharging the soft-start capacitor. Every time the OCR level is exceeded, this state is latched until the next stroke and the soft-start discharge current is

enabled. When both the positive and negative OCR levels are exceeded, the soft-start discharge current flows continuously. In this way the operating frequency is slowly increased until the resonant current value just reaches the value permitted by the preset.

The behavior during OCR can be observed on the SSHBC/EN pin as a resultant regulation voltage.

When an OCR situation is present for a long time, a serious fault condition is assumed. During OCR the protection timer is activated. The charging of the protection timer is active approximately a half period cycle after the  $\pm 0.5$  V level is exceeded. If the detection levels are continuously exceeded, the timer is charged continuously but, if the detection levels are only sometimes exceeded, the timer is charged accordingly (for details on charging/discharging of the protection timer refer to [Section 10.3.3.4](#)). The restart state is activated when RCPROT reaches the protection level of 4 V.

#### 8.7.1.1 Start-up

The overcurrent regulation is effective for limiting the output current during start-up. A smaller soft-start capacitor can be chosen which allows faster start-up. The small soft-start capacitor can result in an excessive output current but the OCR function can slow down the frequency sweep to keep the output current within the limits.

#### 8.7.2 HBC overcurrent protection

In most cases the OverCurrent Regulation is able to keep the current below the set maximum values. However, the OCR can not be fast enough to limit the current for certain error conditions. OverCurrent Protection (OCP) is implemented to protect against those error conditions.

The internal OCP level is set at  $\pm 1$  V for SNSCURHBC. This is significantly higher than the OCR level of  $\pm 0.5$  V. When the OCP level is reached the frequency immediately jumps to the maximum via a soft-start reset procedure, followed by a normal sweep down.

The maximum frequency value for soft-start must be selected to sufficiently limit the output power under these conditions.

The behavior during OCP can be observed on the SSHBC/EN pin as a new soft-start. Depending on the (over)load or fault condition during this new soft-start, OCR or OCP can be reactivated.

#### 8.7.3 SNSCURHBC boost voltage compensation

The primary current, also called resonant current, is sensed via pin SNSCURHBC. It senses the momentary voltage across an external current sense resistor. The use of the momentary current signal allows a fast overcurrent protection and simplifies the stability of the overcurrent regulation. The OCR and OCP comparators compare the SNSCURHBC voltage to the maximum positive and negative values.

The primary current is higher for the same output power when the boost voltage is low. A boost compensation is included to reduce the dependency of the protected output current level for the boost voltage. The boost compensation sources and sinks a current from the SNSCURHBC pin. This current creates a voltage drop across the series resistor  $R_{cc}$ . A typical value for this resistor is 1 k $\Omega$ .

The amplitude of the current depends linearly on the boost voltage. At nominal boost voltage the current is zero and the voltage across the current sense resistor is also present at the SNSCURHBC pin. At the boost start level  $SNSBOOST = 1.8\text{ V}$  and the current is maximum  $170\text{ }\mu\text{A}$ . The direction of the current, sink or source, depends on the active gate signal. The voltage drop created across  $R_{cc}$  reduces the voltage amplitude at the pin, resulting in a higher effective current protection level. The value of  $R_{cc}$  sets the amount of compensation.

8.7.4 Current measurement circuits

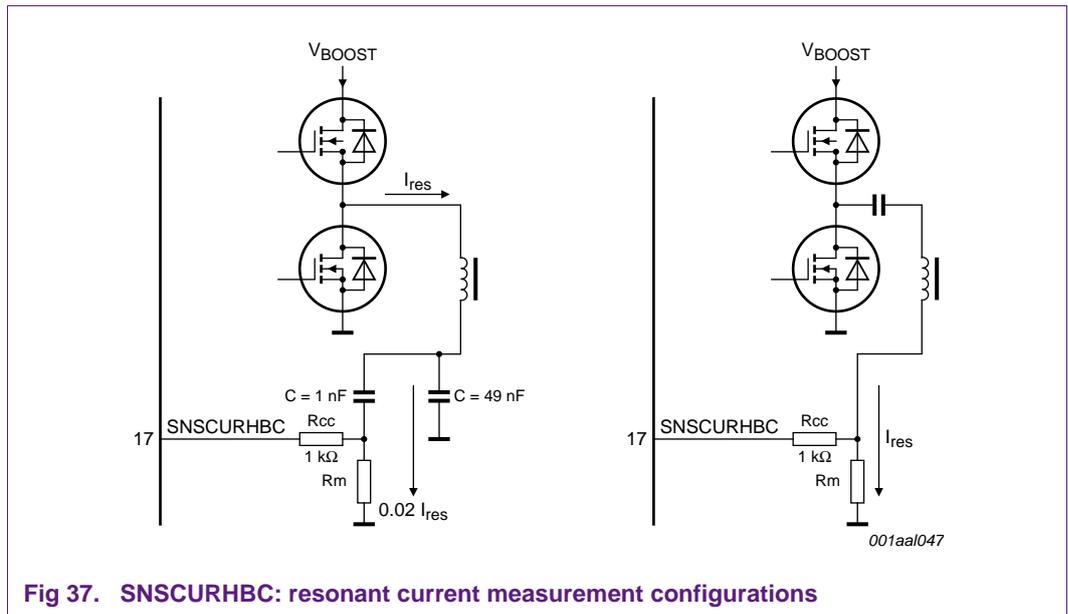


Fig 37. SNSCURHBC: resonant current measurement configurations

8.7.5 SNSCURHBC layout

Because the SNSCURHBC must be able to accurately sense the measurement signal cycle-by-cycle at higher frequencies, it is rather susceptible to disturbances. Place the series resistor  $R_{cc}$  close to the IC to reduce the length of the track that can pick up disturbing signals. This prevents disturbances on this input. As the impedance of the measurement resistor is normally low, the signal track between  $R_{cc}$  and the measurement resistor is not critical regarding disturbance.

## 9. Burst mode operation

Burst mode operation can be used to improve the efficiency at low output loads.

By temporarily interrupting the switching, losses during idle time are minimized. Because the average power needed for the output is low, it is easy for the converter to deliver it during a short conversion time (a burst).

The Burst mode operation of the TEA1713 is based on interrupting the switching while maintaining regulation. With an external comparator, the regulation voltage can be monitored to determine if it stops switching and then continue. Stopping and starting again can be controlled via the SNSOUT pin. When starting again after interruption, no soft-start is applied as the system is still in regulation (close to the regular working point). the regulation-loop of the system (normally by the output voltage) determines the timing of switching on and off. In this way, a small ripple on the output voltage is deliberately created during Burst mode.

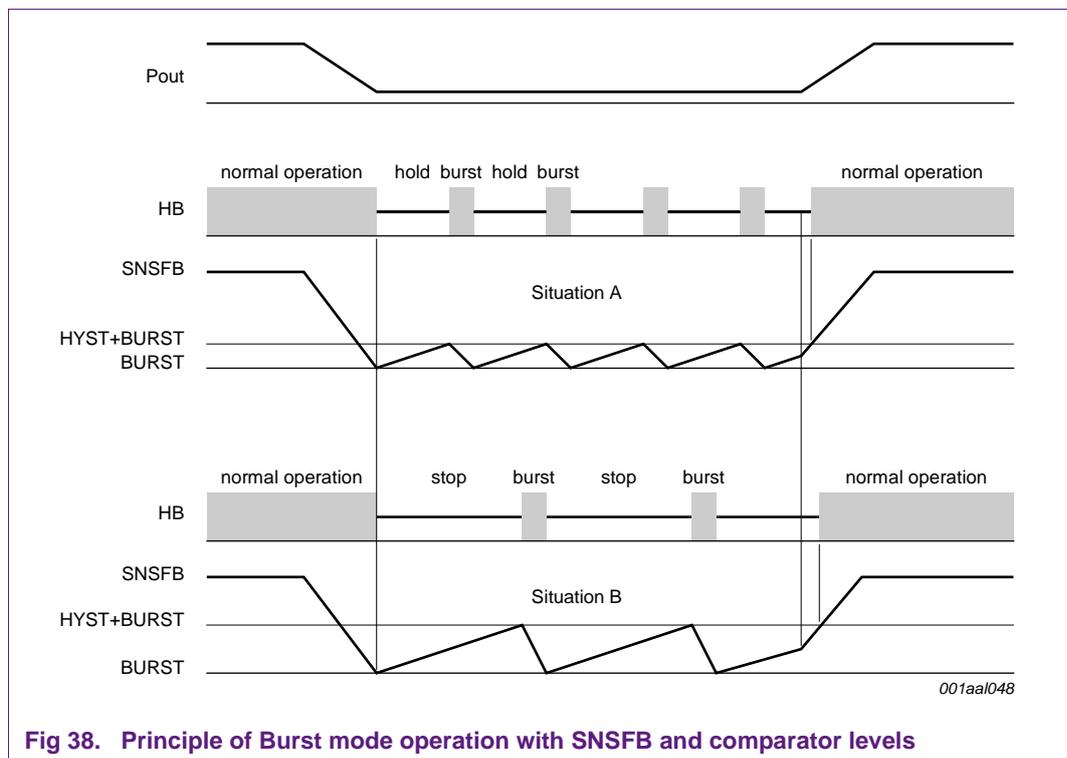


Fig 38. Principle of Burst mode operation with SNSFB and comparator levels

### 9.1 Burst mode controlled by SNSOUT

The HBC and the PFC of the TEA1713 can be operated in Burst mode. In Burst mode the converters operate for a limited time, followed by a period of non-operation. Burst mode operation increases the efficiency during low load conditions.

A simple external circuit that uses the information from the feedback loop can detect the low load condition. The detection circuit pulls down the SNSOUT pin to pause the operation of the TEA1713 for a burst off-time.

SNSOUT has two levels for Burst mode operation:

- Burst-off level for HBC = 1.1 V  
Below this level, only the HBC pauses its operation. Both high-side and low-side power switches are off and the PFC continues full operation. Above this level the HBC resumes operation and it does not execute a soft-start sequence.
- Burst-off level for PFC = 0.4 V  
Below this level, the PFC also pauses its operation via a soft-stop. The HBC is already paused. Above this level the PFC resumes operation with a soft-start.

A current (100  $\mu$ A) from the SNSOUT pin keeps the voltage at an internal clamp voltage of 1.5 V, which is above both Burst mode levels. This avoids Burst mode activation when the output voltage is not yet present. The impedance between the SNSOUT pin and ground must therefore be larger than 20 k $\Omega$ .

### 9.2 External comparator for Burst mode implementation

A comparator circuit between SNSFB and SNSOUT can do the implementation of the Burst mode.

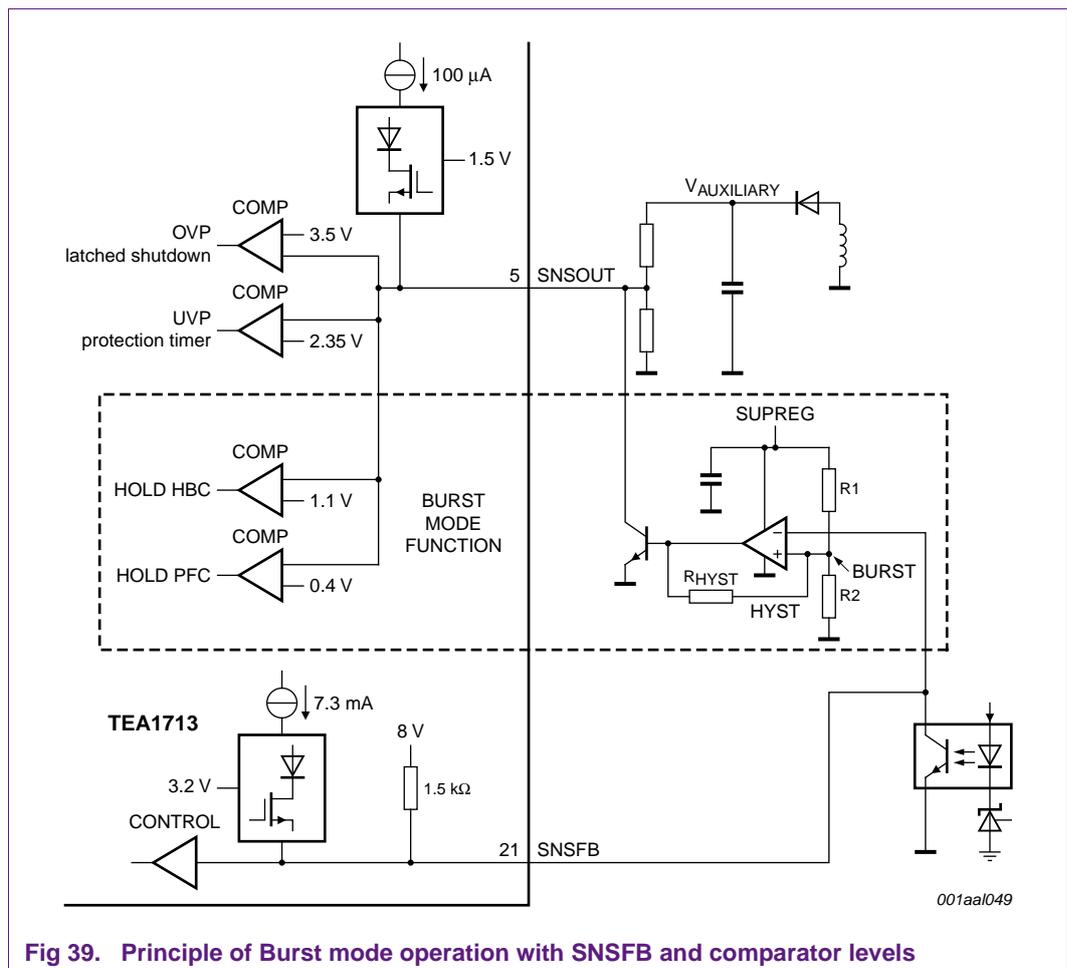


Fig 39. Principle of Burst mode operation with SNSFB and comparator levels

The comparator input monitors the regulation voltage SNSFB to a preset burst voltage value by R1 and R2: BURST. When the HBC power output power is low, the regulation voltage decreases and when it reaches BURST the switching stops by switching SNSOUT to ground. When the switching stops, no energy is converted and the output voltage drops. The regulation voltage then increases again. When the regulation voltage reaches BURST + HYST (voltage hysteresis set by R<sub>HYST</sub>) the switching resumes.

When the power delivered during a burst is larger than needed for the output, the regulation voltage SNSFB quickly decreases, stopping the switching at BURST. The time needed for the regulation voltage to reach BURST, is dependent on the output voltage and its load.

When the HBC output load increases to high levels, normal operation is resumed as the regulation voltage can no longer reach the BURST level.

### 9.3 Advantages of Burst mode for HBC

The main reason of applying Burst mode in a resonant converter is to improve the efficiency at low output power by reducing the power losses.

The graphs in [Figure 40](#) and [Figure 41](#) show the improvement principle in an example of a 250 W resonant converter including (non-bursting) PFC.


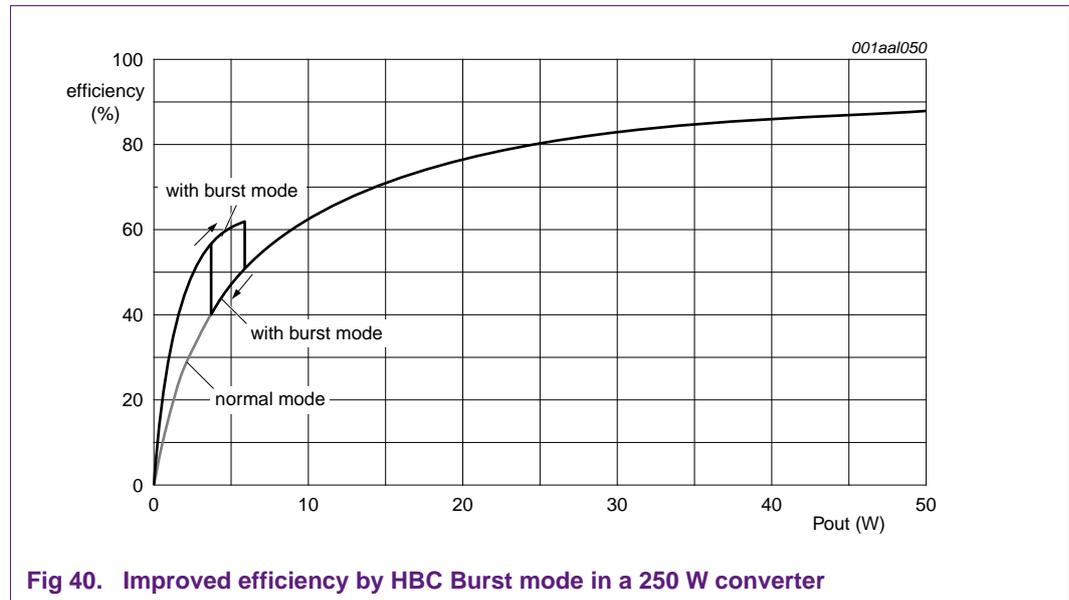



Fig 40. Improved efficiency by HBC Burst mode in a 250 W converter

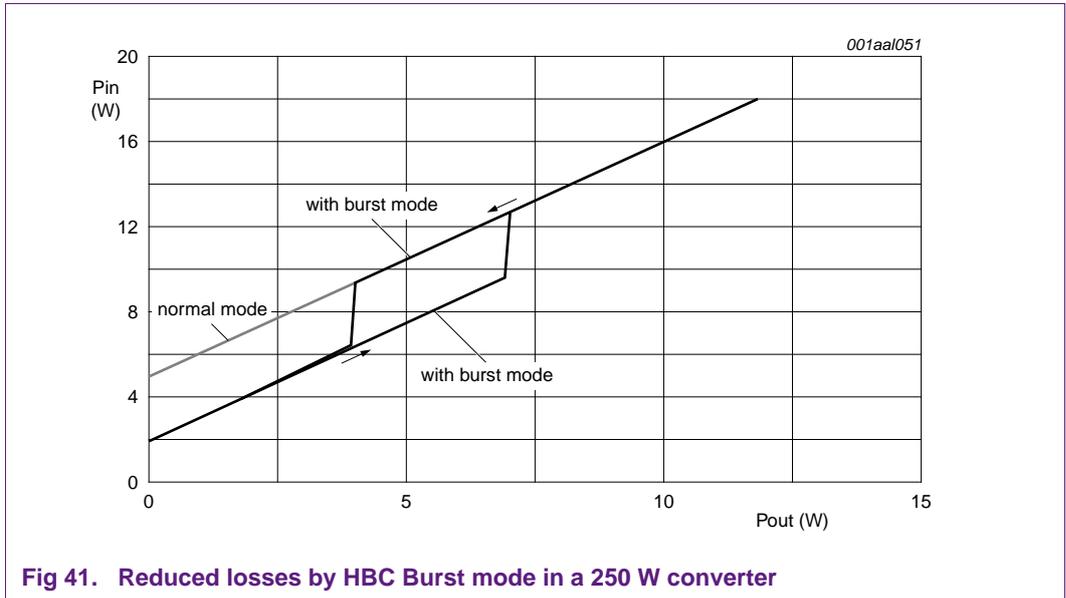

### 9.4 Advantages of Burst mode for HBC and PFC simultaneously

The TEA1713 provides a Burst mode system that simultaneously switches the HBC and PFC. In this way, during the burst period, the power is transferred directly from the input to the output. The HBC determines the repetition time of the burst and the PFC follows. In the burst period, the PFC operates in normal regulation.

PFC bursting obtains extra reduction in power consumption. [Figure 42](#) to [Figure 44](#) show examples of the results.

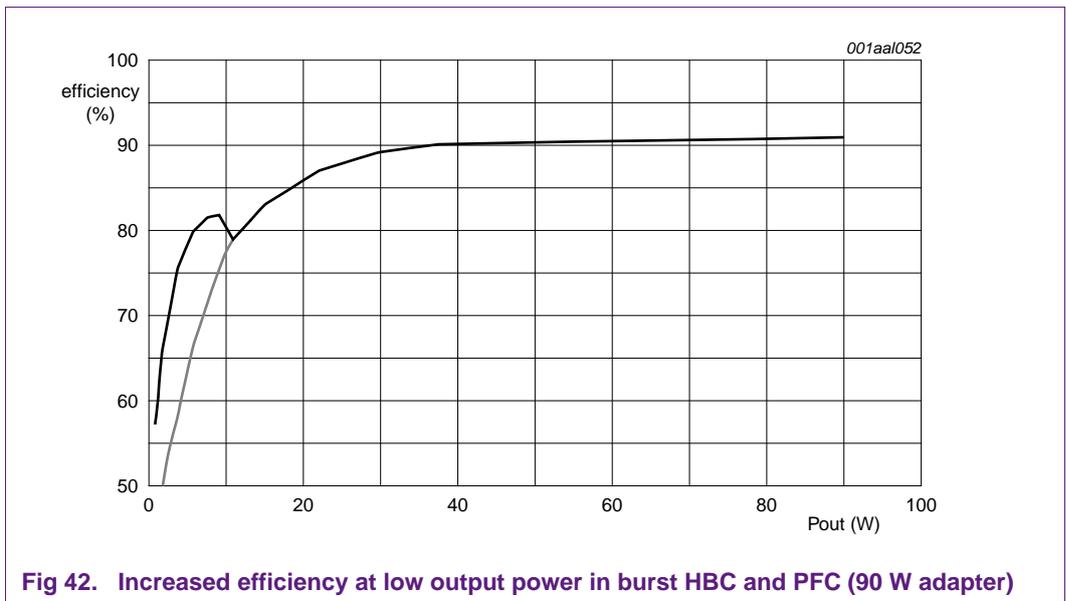

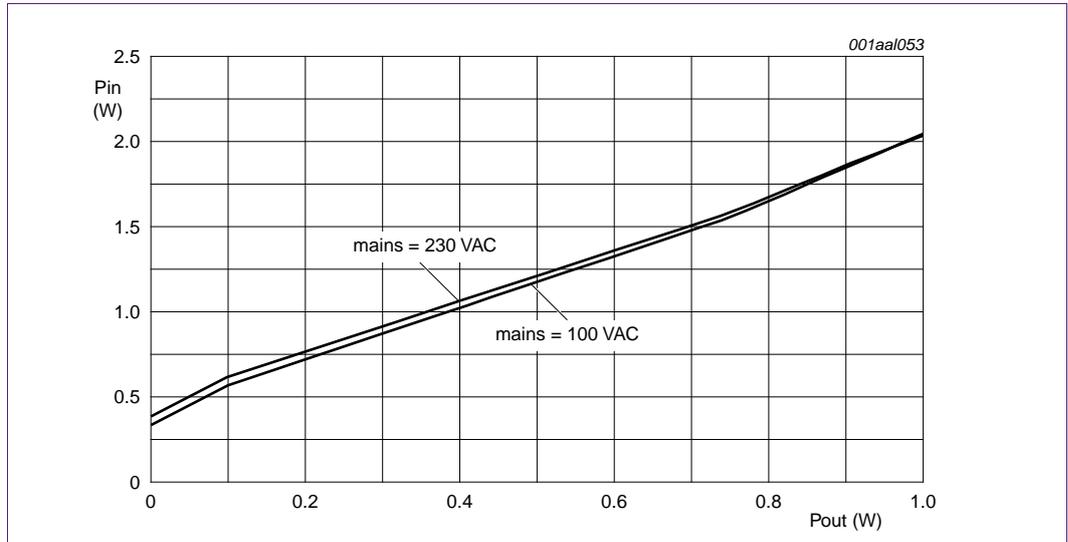


Fig 43. Remaining 90 W adapter losses in Burst mode

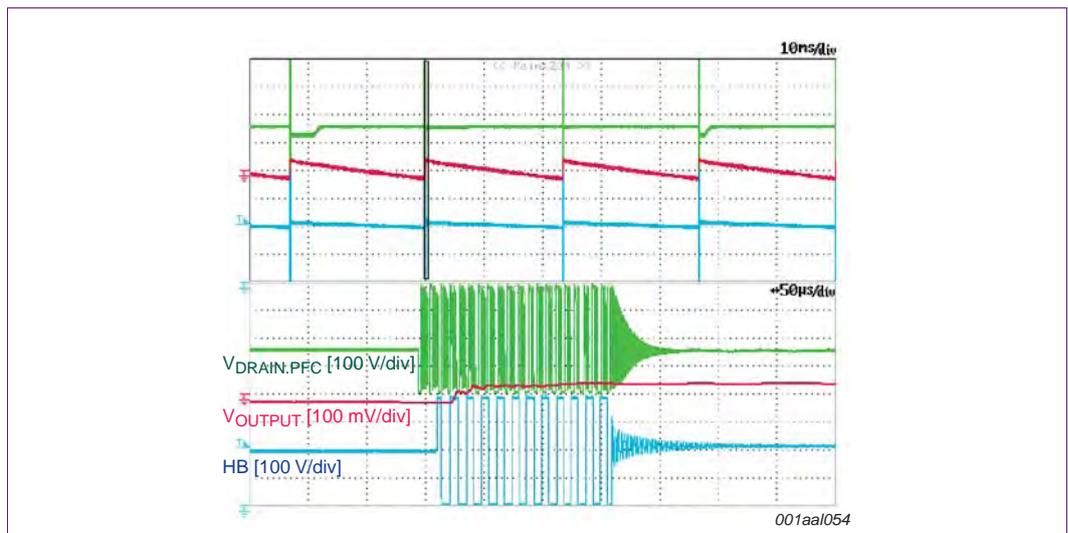



Fig 44. Simultaneous HBC and PFC Burst mode operation (including output voltage ripple)

### 9.5 Choice of burst level and hysteresis level

Set the power levels for bursting using an external comparator for dimensioning the Burst mode. [Figure 39](#) shows a typical comparator circuit with hysteresis.

The basic choice for the voltage level at which the comparator must be active (BURST) can be made experimentally.

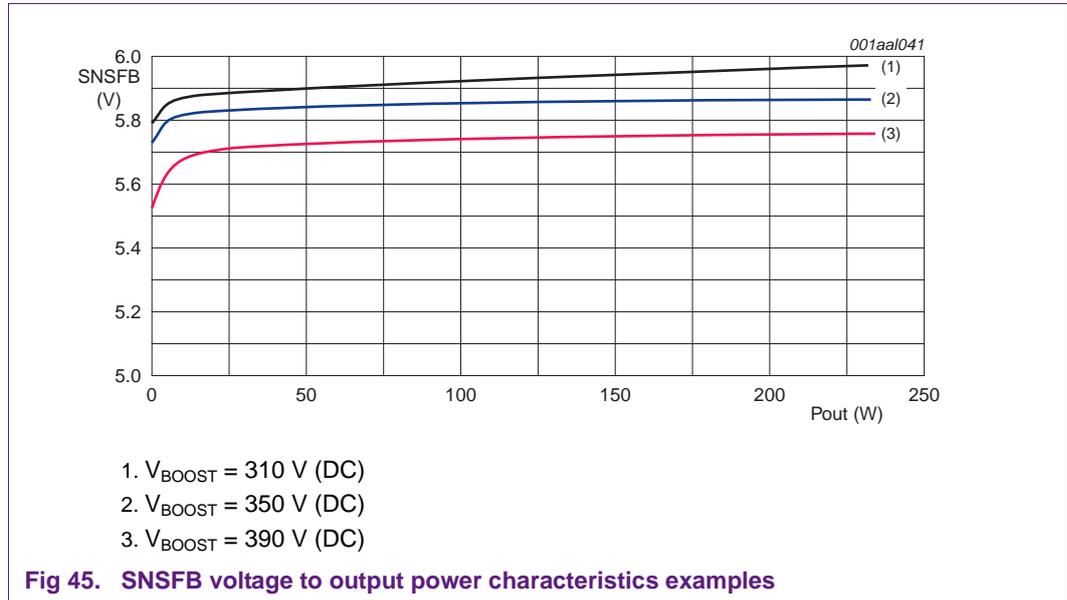It is important to realize that the input voltage of the resonant converter  $V_{boost}$  (see [Figure 46](#)) influences the relationship between the HBC output power level and the SNSFB regulation voltage.




Aspects that influence the voltage levels (BURST and HYST) of Burst mode:

- Input voltage  $V_{\text{boost}}$
- SNSFB voltage regulation levels in combination with the preset frequency range of RFMAX and CFMIN
- Dynamic behavior of the regulation during Burst mode and during normal operation (large load variations)

### 9.6 Output power - operating frequency characteristics

Figure 46 show that it is critical to make a design choice for a certain SNSFB voltage to start bursting. With this kind of characteristic there is a risk that, due to spread, the system can either remain in Burst mode or never reach Burst mode operation at all. The dimensioning of the LLC can be made more suitable for Burst mode. The standard approach is to design the system in such a way that it cannot regulate to no-load, even at the highest frequency. During the lowest loads, the frequency required for regulation must become infinite. A voltage level can then easily be chosen to ensure that Burst mode is activated at the lowest load and that the remaining load conditions operate in Normal mode. Burst mode now enables the system to operate at no-load.

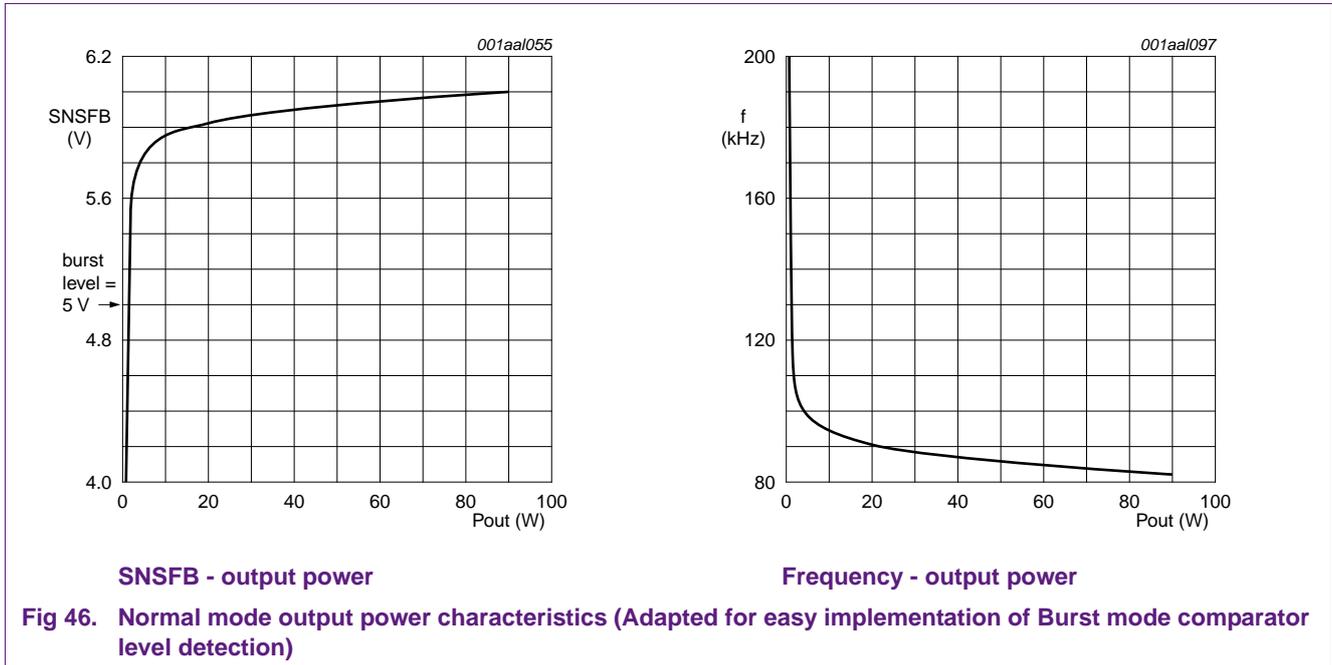

**9.7 Lower SUPHS in burst**

During the idle time SUPHS is not charged.

During normal operation, each time the half-bridge node HB is switched to ground level, the bootstrap function of the external diode between SUPHS and SUPREG charges the SUPHS capacitor. In Burst mode there are periods of non-switching and therefore no charging of SUPHS. During this time, the circuit supplied by SUPHS slowly discharges the supply voltage capacitor. When a new burst starts, the SUPHS voltage is lower than in normal operation. During the first switching cycles, the SUPHS is recharged to its normal level. It is important that, during these first recharge cycles, SUPREG does not drop below the protection level of 10.3 V.

**9.8 Audible noise**


Because the Burst mode is normally used when the output power is low, the converted energy does not contribute much to generate audible noise. The magnetization current however is still present during low loads and is the dominant energy during Burst mode. Switching the converter sequences on and off continuously at a certain speed and duration can lead to audible noise. The main mechanism for producing noise is the interruption of magnetization current sequences leading to a mechanical force. This is especially the case on the core of the resonant transformer which starts acting as a loudspeaker.

When Burst mode is applied during higher output power conditions, the converted energy also contributes and leads to an increased risk of audible noise.

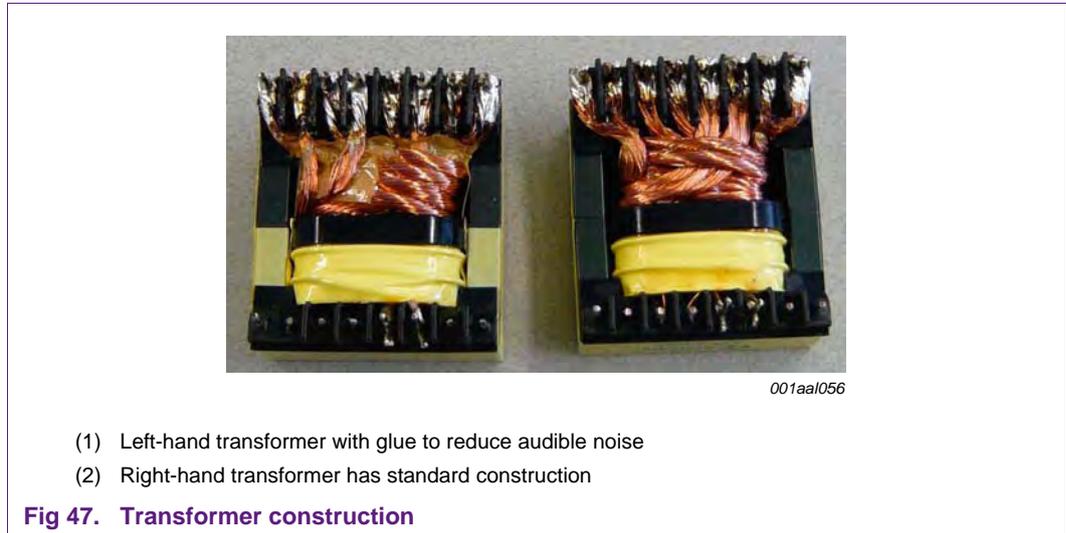**9.8.1 Measurements in the resonant transformer construction**

It is necessary to adapt the mechanical transformer construction to prevent problems with audible noise under specific conditions.

One measure is to adhere the core parts to each other using a material with damping (vibration absorbing) properties. A combination can be made with the air gap construction. Other vibration damping measures can also help when audible noise is a critical issue for a product.



### 9.8.2 Burst power-dependent noise level

The amount of audible noise is related to the amount of energy in each burst.

At low output power, the magnetization current of the resonant converter determines the amount of energy. The amount of transferred energy is low. Use Burst mode only at low power (a few watts output power) to avoid problems with audible noise. When the transition level between Normal mode and Burst mode is chosen at a higher output power, the level of audible noise is larger.

#### Overshoot on feedback voltage

When the output load is increased, the system reverts to normal operation. The transition from Burst mode to Normal mode is based on the feedback voltage. In certain burst conditions the feedback voltage can overshoot. This keeps the system in Burst mode at higher output power levels than intended. As the power level in this situation is larger, the amount of noise is also larger.

### 9.9 PFC converter and resonant converter simultaneous bursting

When in the Burst mode, PFC operation stops while the resonant converter is not switching. In most cases this saves extra energy consumption by reduced switching losses from the PFC converter.

The behavior of the total system (PFC and resonant) in Burst mode can differ from the situation when only the resonant converter would operate in Burst mode. Although this results in good performance, there are a number of interactions.

### 9.9.1 PFC output voltage variations


When bursting the PFC converter, the resonant control system determines the timing. This can result in a situation where the PFC cannot maintain a constant output voltage. The HBC operation limits the time during which the PFC can convert power. This may be too short. The result is either a lower or a varying output voltage. This also has consequences for the resonant converter as its input voltage is not the same. The working conditions change towards a new balance.

The resonant converter must be able to remain operational during these conditions.

It is important to check that the resonant controller has not been stopped because the input voltage provided by SNSBOOST is too low. This can cause an unacceptable voltage decrease in the output of the resonant converter.
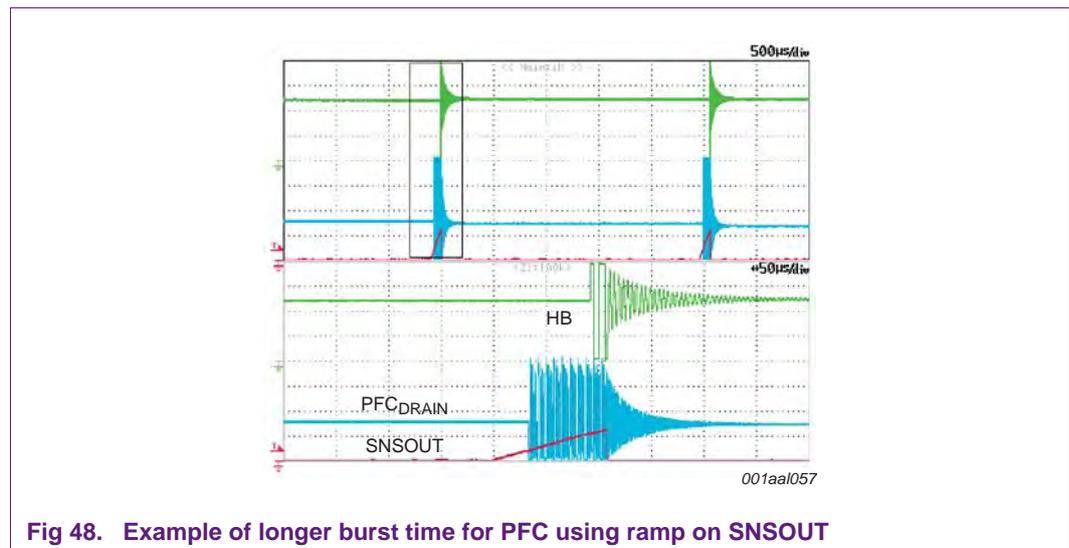
### 9.9.2 PFC burst duration

Normally a square SNSOUT pulse leads to equal operation time for PFC and HBC (see [Figure 44](#)). If a longer PFC operating time is needed for correct balance, it can be achieved by adding a capacitor on SNSOUT to create a ramp signal. The PFC starts at a voltage of 0.4 V, allowing a longer PFC operating time.



### 9.9.3 Switching between burst and normal operation

Interaction between the PFC converter and resonant converter in the Burst mode can lead to a situation where the system alternates between Burst mode and Normal mode for certain output power conditions.

### 9.9.4 Audible noise during mode transition

As a result of the previously mentioned interactions, a stable situation can occur during the following operating modes, alternating in time:

- Resonant burst with short burst time without PFC burst (time too short to start).
- Resonant burst with long burst time and PFC burst.
- Normal operation for resonant and PFC bursts.

Transitions between modes and variations within a certain mode have a corresponding effect on audible noise.

### 9.10 Design guidelines for Burst mode operation

Design for a stable PFC (nominal) output voltage during Burst mode.

Best efficiency is achieved when the number of cycles for each burst is as small as possible (only a few cycles).

Best efficiency is achieved by resistively tuning the comparator circuit to preset the SNSFB burst level and hysteresis.

System and component tolerances play a significant role in variations of performance in production.

The regulation feedback loop can be optimized for Normal mode. Any additional filtering can be done in the comparator circuit. However, use it moderately so control of the situation can be maintained during the Burst mode operation.

### 9.11 Enable/disable Burst mode

In microcontroller operated applications such as TV, a clear separation is made between normal operation and standby operation. An enable/disable function can be added to avoid the resonant converter entering Burst mode when short periods of low load occur during normal operation. An extra enable/disable switch function in the comparator circuit implements the enable/disable function.

### 9.12 Unused Burst mode

When the Burst mode is not required, not applying a circuit to switch SNSOUT leaves the Burst mode function inactive.

## 10. Protection functions

Most protection functions are discussed in the chapters of the systems of which they are a part. [Table 4](#) contains an overview of links to the corresponding places in this document. In the following paragraphs the remaining, more independent, protection functions are discussed.

### 10.1 Protection overview

**Table 4. Overview of protection functions with links**

Part	Symbol	Protection	Action	Link
IC	UVP-SUPIC	undervoltage protection	SUPIC IC disable	<a href="#">Section 5.2.2</a>
IC	UVP-SUPREG	undervoltage protection SUPREG	IC disable	<a href="#">Section 5.5</a>
IC	UVP supplies	undervoltage protection supplies	IC disable and reset	-
IC	SPC-SUPIC	short circuit protection SUPIC	low HV start-up current	<a href="#">Section 5.2.2</a>
IC	OVP output	overvoltage protection output	IC shutdown	<a href="#">Section 10.3.1</a>
IC	UVP output	Under Voltage Protection output	IC restart after protection time	<a href="#">Section 10.3.2</a>
IC	OTP	overtemperature protection	IC disable	<a href="#">Section 10.2.1</a>
PFC	OCR-PFC	overcurrent regulation PFC	PFC switch-off cycle-by-cycle	<a href="#">Section 7.4</a>
PFC	UVP-mains	undervoltage protection mains	PFC hold switching	<a href="#">Section 7.6.1</a>
PFC	OVP-boost	overvoltage protection boost	PFC hold switching	<a href="#">Section 7.5</a>
PFC	SCP-boost	short circuit protection boost	IC restart	<a href="#">Section 7.2.2</a>
HBC	UVP-boost	undervoltage protection boost	HBC disable	<a href="#">Section 8.1</a>
HBC	OLP-HBC	open-loop protection HBC	IC restart after protection time	<a href="#">Section 8.5.1</a>
HBC	HFP-HBC	high frequency protection HBC	IC restart after protection time	<a href="#">Section 8.4.4</a>
HBC	OCR-HBC	overcurrent regulation HBC	HBC frequency increase IC restart after protection time	<a href="#">Section 8.7.1</a>
HBC	OCP-HBC	overcurrent protection HBC	HBC step to maximum frequency	<a href="#">Section 8.7.2</a>
HBC	CMR	Capacitive mode regulation	HBC increase frequency	<a href="#">Section 8.3.2</a>
HBC	ANO	adaptive non-overlap	HBC prevent hazardous switching	<a href="#">Section 8.3.1</a>

### 10.2 IC protection

#### 10.2.1 OverTemperature Protection (OTP)

The TEA1713 contains an accurate internal overtemperature protection. When the junction temperature exceeds the overtemperature level of 140 °C, the IC enters the Thermal hold state. The Thermal hold state is left when the temperature has dropped by 10 °C.

The circuit resumes operation with a complete restart including a soft-start of PFC and HBC.

#### 10.2.2 Latched protection

Only an overvoltage detection on SNSOUT leads to a latched shutdown protection state. The voltage on SNSOUT must exceed 3.5 V to enter a latched shutdown state.



### 10.3.1 OverVoltage Protection (OVP) output

The TEA1713 has an overvoltage protection intended for monitoring the HBC output voltage. It is one of the functions that is combined on the SNSOUT pin.

#### 10.3.1.1 Auxiliary winding

When dealing with a mains insulated converter, the HBC output voltage can be measured via the auxiliary winding of the resonant transformer. A special transformer construction is required to accurately measure the secondary voltage of the primary circuit auxiliary winding.

It is important that this winding has a good coupling with the secondary winding(s) and a minimum coupling with the primary winding. In this way, a good representation of the output voltage situation is obtained (see [Section 5.3.3.1](#) and [Figure 7](#)).

Triple insulated wire can be used to meet the mains insulation requirements.

#### 10.3.1.2 Principle of operation

The voltage is sensed at the SNSOUT pin via an external rectifier and resistive divider. Overvoltage is detected when the SNSOUT voltage exceeds 3.5 V. After detecting OVP the TEA1713 enters the latched protection shutdown state.

#### 10.3.1.3 Connecting external measurement circuits

When latched protection is needed for other detection circuits, it can be added to SNSOUT with a series diode.

### 10.3.2 UnderVoltage Protection (UVP) output

The TEA1713 has an undervoltage protection intended for monitoring the HBC output voltage. It is one of the functions that is combined on the SNSOUT pin.

#### 10.3.2.1 Auxiliary winding

When dealing with a mains insulated converter, the HBC output voltage can be measured via the auxiliary winding of the resonant transformer. A special transformer construction is required to accurately measure the secondary voltage of the primary circuit auxiliary winding.

It is important that this winding has a good coupling with the secondary winding(s) and a minimum coupling with the primary winding to obtain a good representation of the output voltage situation (see [Section 5.3.3.1](#) and [Figure 7](#)).

Triple insulated wire can be used to meet the mains insulation requirements.

#### 10.3.2.2 Principle of operation

The voltage is sensed at the SNSOUT pin via an external rectifier and resistive divider. Undervoltage is detected when the SNSOUT voltage drops below 2.35 V. When detecting UVP the TEA1713 starts the protection timer by charging it with 100  $\mu$ A.

When the undervoltage state remains until the timer reaches the protection level, the controller stops and then the restart timer restarts it.

At start-up, the SNSOUT voltage normally starts at a level lower than 2.35 V. The timer setting must allow sufficient time for start-up to charge the SNSOUT voltage to a value above 2.35 V, preventing undesired protection during start-up.

In applications where the TEA1713 is supplied from an auxiliary winding (to SUPIC), the SUPIC monitoring can also activate a protection when an error condition results in a drop of the output voltage (see [Section 5.2.2](#)).

#### 10.3.2.3 Severe voltage drop

When the voltage on SNSOUT drops to a low voltage, the Hold HBC and Hold PFC functions on this input pin stop the HBC and PFC.

#### 10.3.2.4 Connecting external measurement circuits

When restart protection is needed for other detection circuits, it can be added on SNSOUT with a series diode.

### 10.3.3 OVP and UVP combinations

#### 10.3.3.1 Circuit configurations

The following list contains examples of configurations for which certain functionality on the SNSOUT pin is disabled.

- OVP functional and UVP disabled (see [Section 10.3.3.2](#))
- UVP functional and OVP disabled (see [Section 5.3.3.3](#))
- Both OVP and UVP disabled (see [Section 10.3.3.4](#))

**Remark:** In the examples given, Burst mode operation can still be implemented independent of the UVP and/or OVP functionality.

#### 10.3.3.2 OVP functional and UVP disabled

In some applications preventing the activation of the undervoltage protection on SNSOUT by disabling UVP can be required. This can be realized by adding a circuit that prevents the voltage on SNSOUT from dropping below 2.35 V.

As a practical example, the voltage on SNSOUT can be prevented from dropping below a preset voltage by externally adding a low impedance resistive divider, with a fixed voltage and connecting it to SNSOUT via a diode. This simple circuit is not accurate but it does provide the basic capability to disable the UVP function of SNSOUT.

**Remark:** The diode is blocking for higher voltage values on SNSOUT so that the overvoltage protection is still functional.

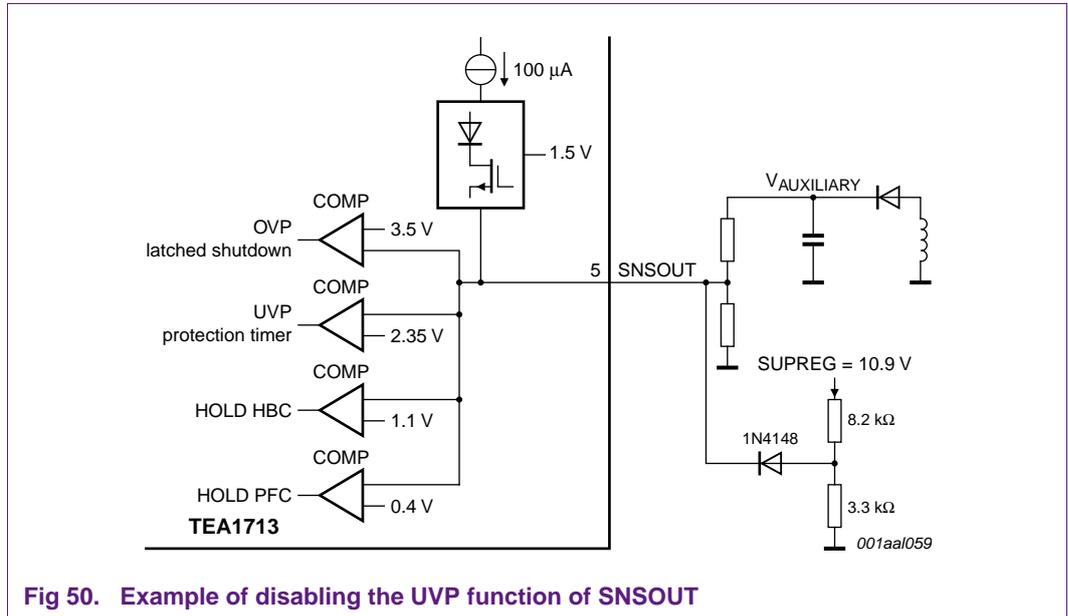


Fig 50. Example of disabling the UVP function of SNSOUT


10.3.3.3 UVP functional and OVP disabled

In some applications preventing the activation of the overvoltage protection on SNSOUT by disabling OVP can be required. This can be realized by adding a circuit that prevents the voltage on SNSOUT from exceeding 3.5 V.

As a practical example, the voltage on SNSOUT can be prevented from exceeding the preset voltage by externally adding a low impedance resistive divider, with a fixed voltage, and connecting it to SNSOUT via a diode. This simple circuit is not accurate but it does provide the basic capability to disable the OVP function of SNSOUT.


**Remark:** The diode is blocking for lower voltage values on SNSOUT so that the undervoltage protection is still functional.

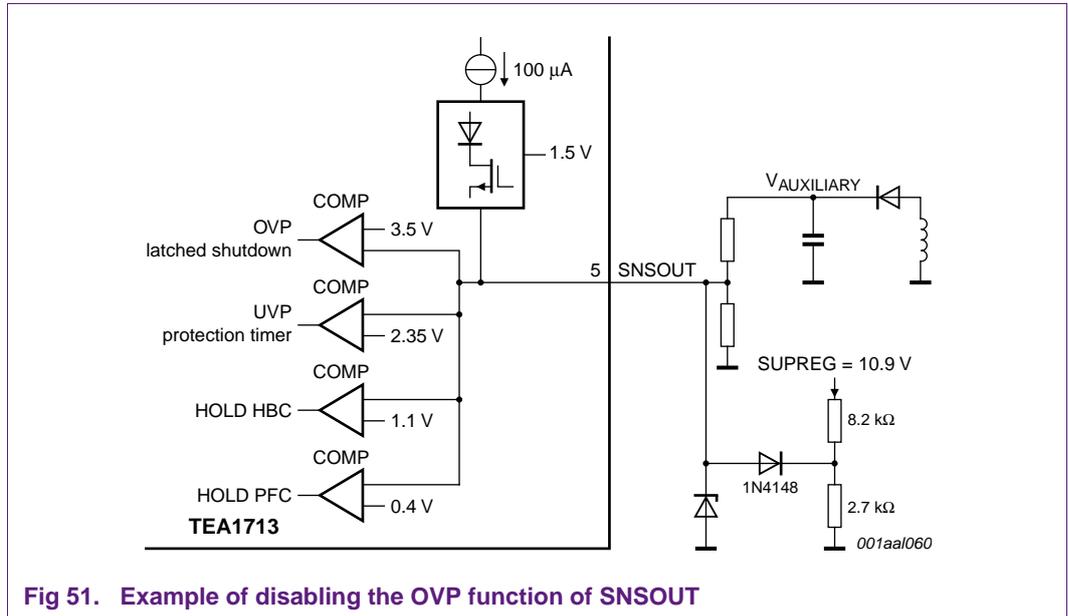Another possibility is to add a Zener diode function on SNSOUT to limit the voltage on this pin.



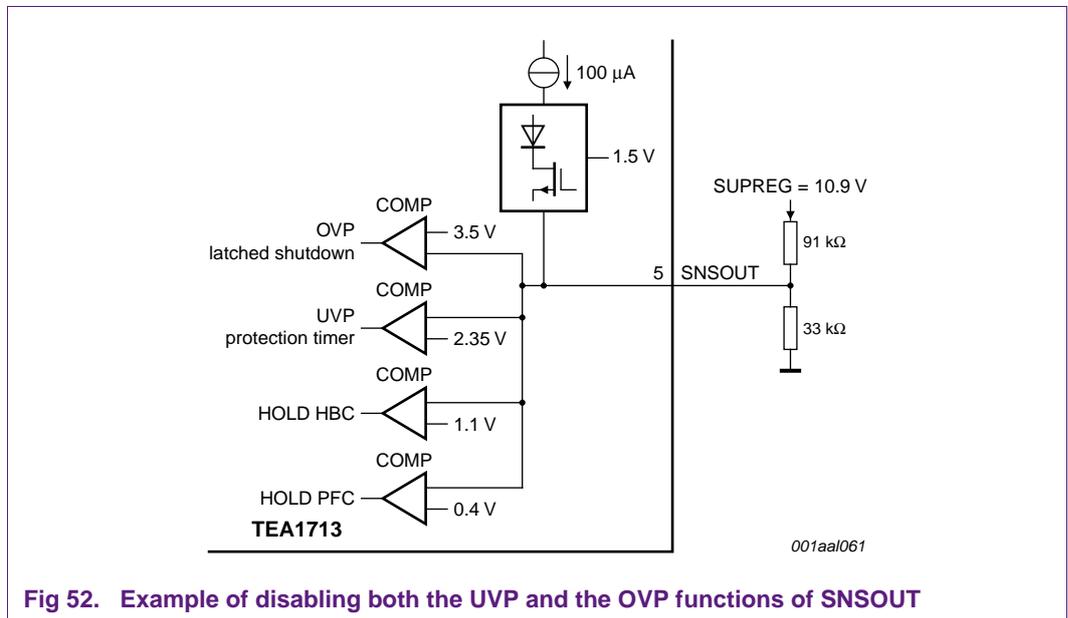**10.3.3.4 Both OVP and UVP disabled**

When neither OVP or UVP functionality is required, a fixed voltage between 2.35 V and 3.5 V can be applied to SNSOUT. This can be obtained from a resistive divider that is referenced to the SUPREG.



### 10.4 Protection timer

The TEA1713 has a programmable timer that is used for the timing of several forms of protection. The timer is used in two ways:

- As a protection timer
- As a restart timer

The values for both types of timer can be independently preset by an external resistor and capacitor connected to RCPROT.

#### 10.4.1 Block diagram of the RCPROT function

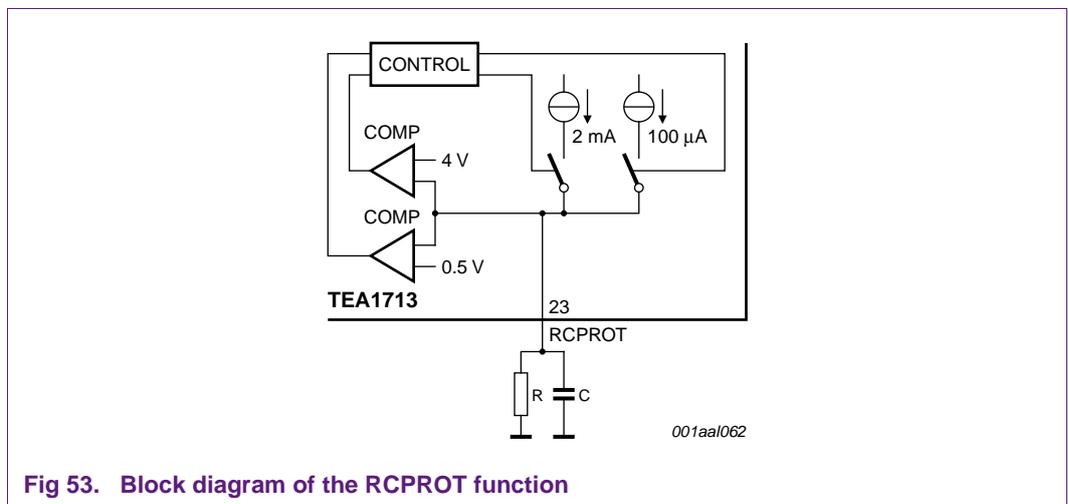


Fig 53. Block diagram of the RCPROT function

#### 10.4.2 RCPROT working as protection timer

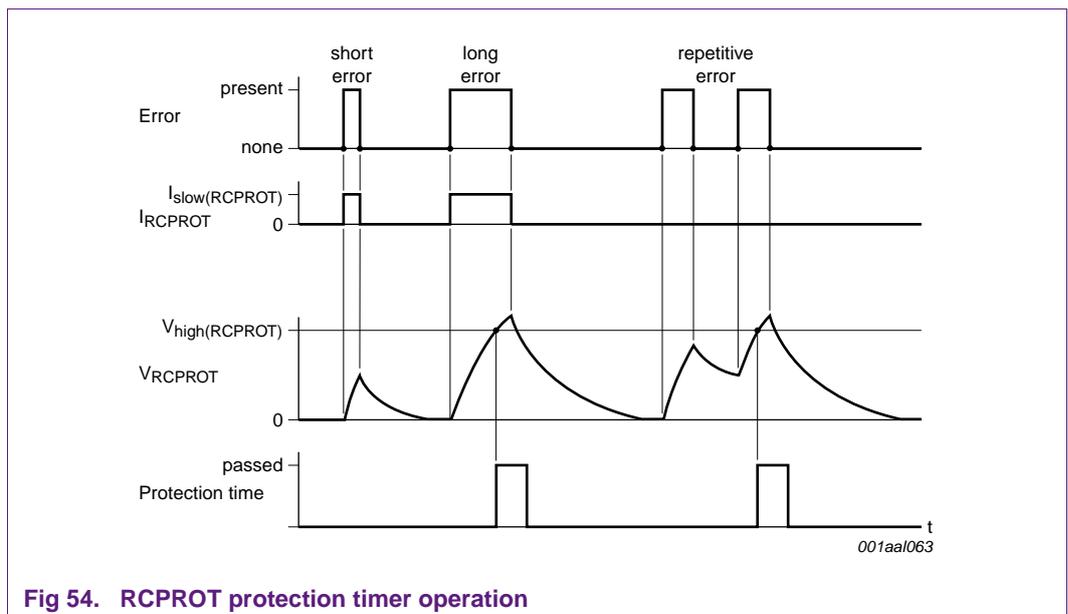


Fig 54. RCPROT protection timer operation

Figure 54 shows the operation of the protection timer. When an error condition occurs, a fixed current of 100  $\mu\text{A}$  flows from the RCPROT pin and charges the external capacitor. The voltage rises exponentially due to the external resistor. The protection time is passed when the upper switching level of 4 V has been reached. The appropriate protective action is then executed, the current source is stopped and the external resistor discharges RCPROT.

If the error condition ends before 4 V has been reached, the current source is stopped and the pin discharges through the external resistor and no further action is taken.

If the error condition is permanent, the system fluctuates between stop and restart.

The following events activate the protection timer:

- Overcurrent regulation SNSCURHBC
- High frequency protection RFMAX
- Open-loop protection SNSFB
- Undervoltage protection SNSOUT

The activation of protection (and restart) can be forced by increasing the RCPROT voltage to above the 4 V (but no higher than 12 V) using an external circuit.

### 10.4.3 RCPROT working as a restart timer

During certain error conditions, it may be desirable to temporarily disable the IC. This is especially useful when an error can overheat components. A temporary disable allows power supply components to cool down, after which the IC must automatically restart. The restart timer determines the time to restart.

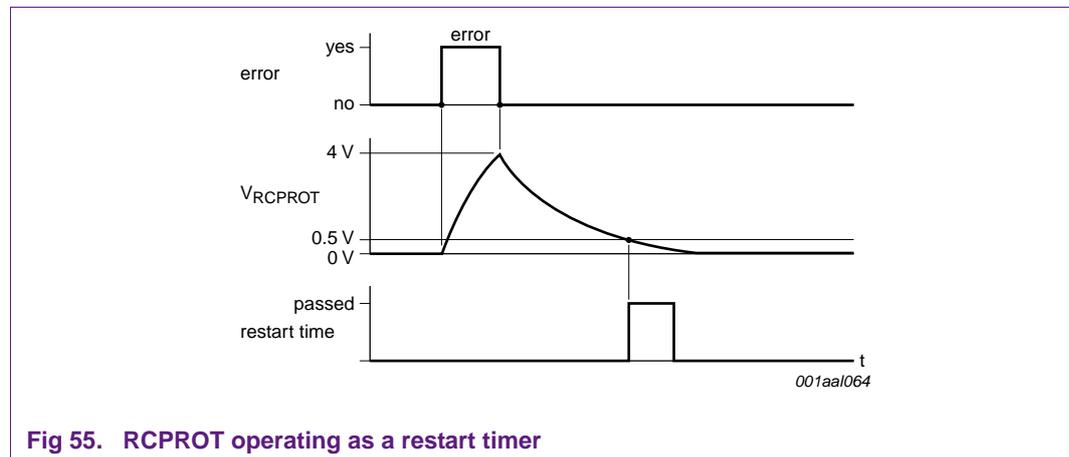


Fig 55. RCPROT operating as a restart timer

Normally, the capacitor is discharged to 0 V but when a restart is requested, a current of 2.2 mA quickly charges the external capacitor until it reaches the upper switching level of 4 V. After this, the RCPROT pin becomes high ohmic and the external resistor discharges the external capacitor. The restart time is exceeded when the lower switching level of 0.5 V has been reached. The IC is then restarted and the RCPROT pin is further discharged. This condition is only activated in the case of short circuit protection of the SNSBOOST.

#### 10.4.4 Dimensioning the timer function

The required restart time  $t_{\text{restart}}$  determines the time constant  $t_{\text{RCPROT}}$  made by the values of R and C.

$$t_{\text{RCPROT}} = \frac{-t_{\text{restart}}}{\ln\left\langle \frac{V_{\text{low(RCPROT)}}}{V_{\text{high(RCPROT)}}} \right\rangle} = \frac{-t_{\text{restart}}}{\ln\left\langle \frac{0.5}{4} \right\rangle} = 0.48 \times t_{\text{restart}} \quad (38)$$

With this time constant and the required protection time  $t_{\text{protection}}$ , the value of R and C can be calculated as follows:

$$R = \frac{V_{\text{high(RCPROT)}}}{I_{\text{slow(RCPROT)}} \times \left\langle 1 - e^{-\frac{t_{\text{protection}}}{t_{\text{RCPROT}}}} \right\rangle} = \frac{4}{100 \mu\text{A} \times \left\langle 1 - e^{-\frac{t_{\text{protection}}}{t_{\text{RCPROT}}}} \right\rangle} \quad (39)$$

$$C = \frac{t_{\text{RCPROT}}}{R} \quad (40)$$

Example:

- $t_{\text{restart}} = 500 \text{ ms}$
- $t_{\text{protection}} = 30 \text{ ms}$
- $t_{\text{RCPROT}} = 240 \text{ ms}$
- $R = 341 \text{ k}\Omega$
- $C = 705 \text{ nF}$

## 11. Miscellaneous advice and tips

### 11.1 PCB layout

#### 11.1.1 General setup

The TEA1713 contains two largely independent converter controllers in one package. General advice is to physically separate the PFC and HBC circuits on the PCB to avoid mutual interference.

#### 11.1.2 Grounding

Connect SGND + PGND directly under the IC (on the ground plane if possible) to avoid false signal detection by driver current disturbance (see [Figure 58](#)).

A star grounding construction provides the lowest risk of mutual converter disturbance or signal detection disturbance. In this system, the central star point can be chosen at the  $V_{boost}$  capacitor ground.

Avoid High currents on grounding tracks that are meant for signal measurement.

#### 11.1.3 Current loops

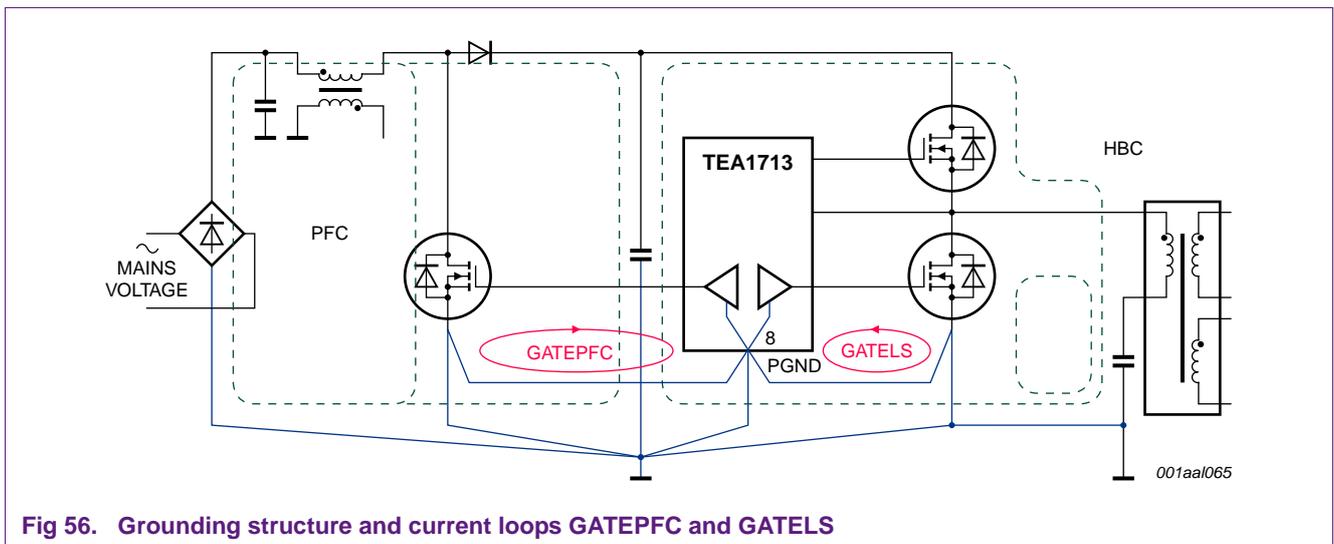


Fig 56. Grounding structure and current loops GATEPFC and GATELS

11.1.4 Grounding layout example

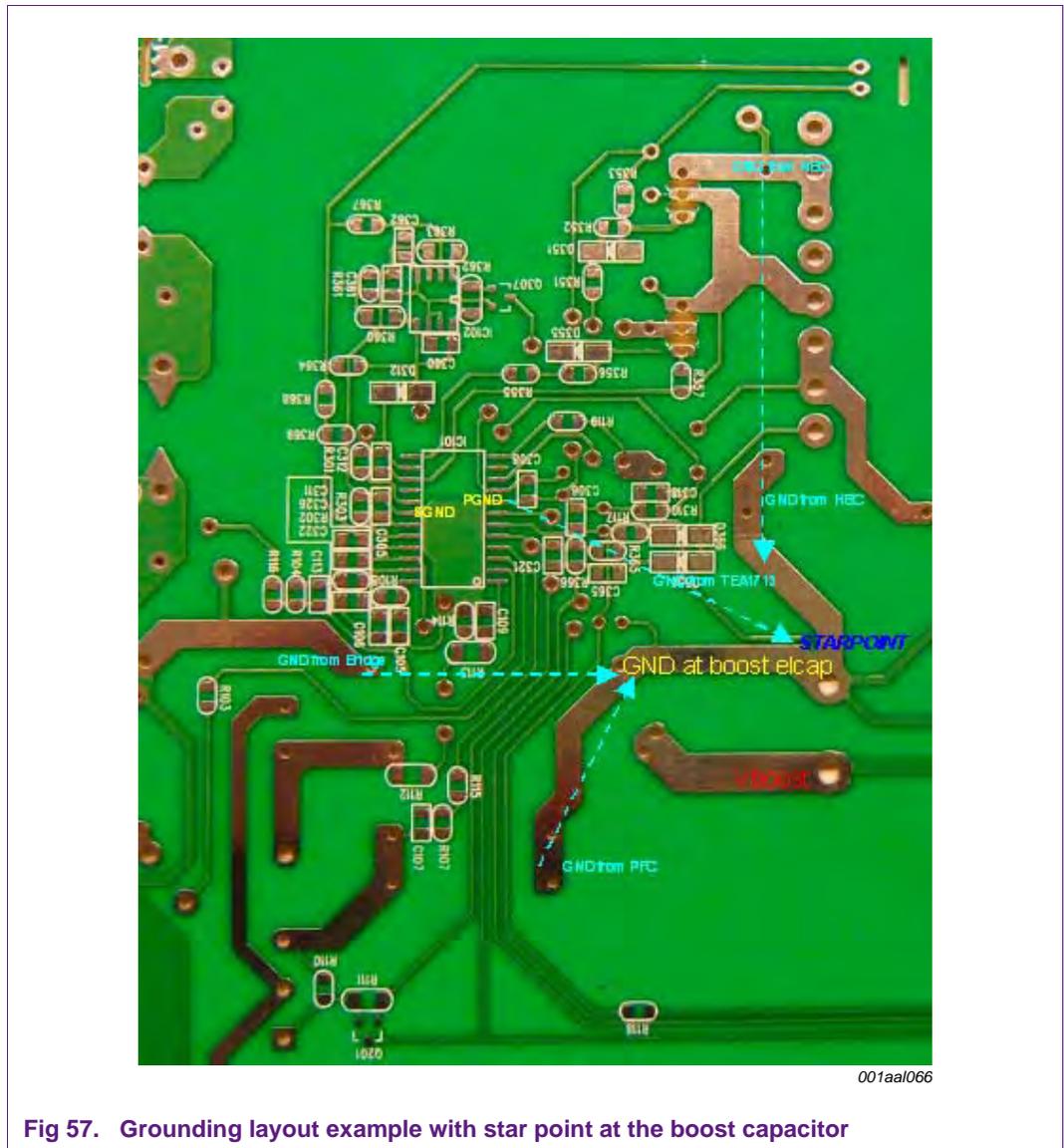


Fig 57. Grounding layout example with star point at the boost capacitor


11.1.5 Miscellaneous

11.1.5.1 Connecting SNSCURHBC (pin 17)

Place a series resistor in the SNSCURHBC connection as close as possible to pin 17. This is important for avoiding disturbance pickup. Also avoid capacitive coupling between the connection to pin 17 and the HB track (to pin 15) that contains high dV/dt signals.

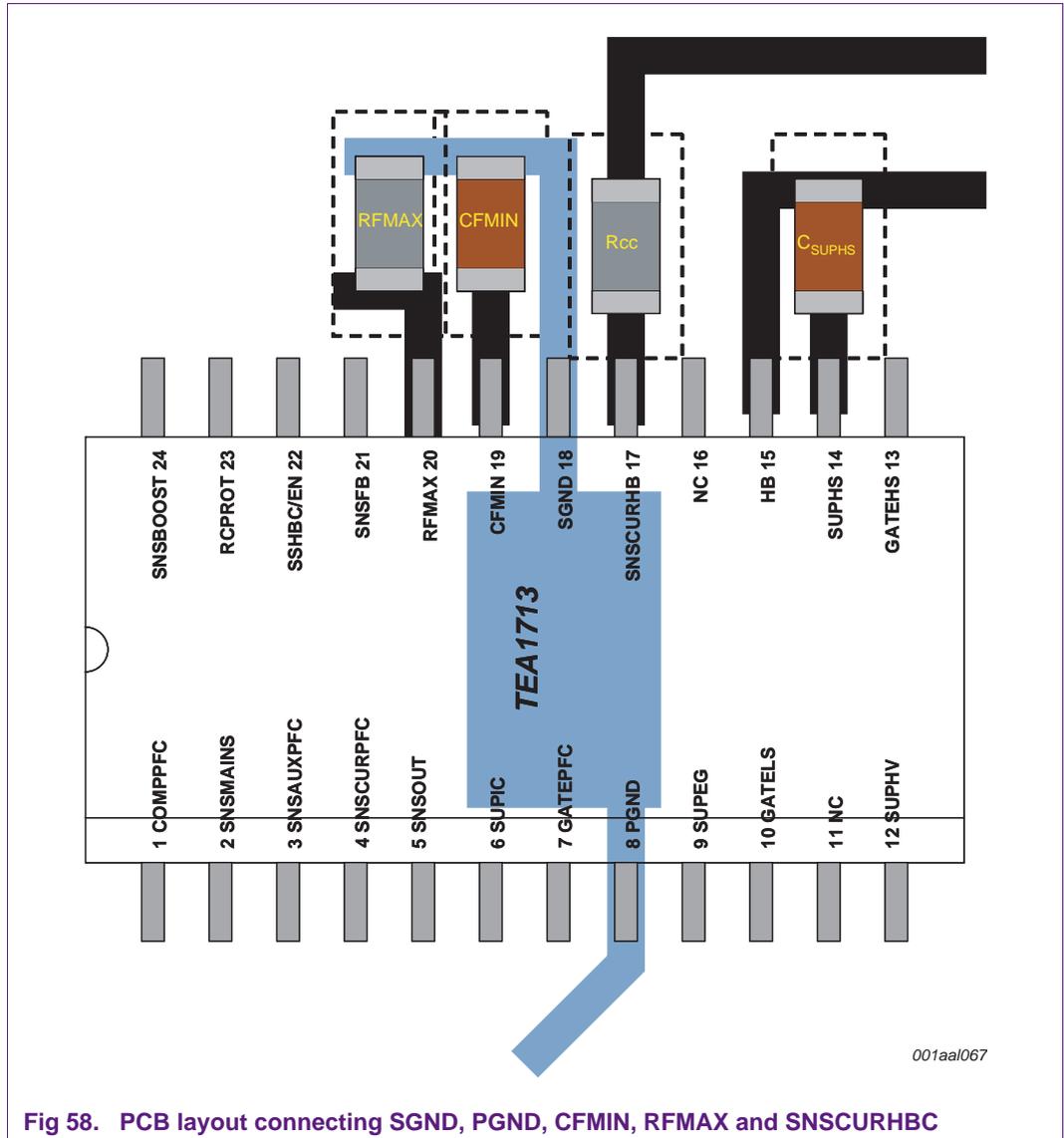11.1.5.2 CFMIN (pin 19) and RFMAX (pin 20)

Connect the oscillator capacitor on CFMIN from pin 19 to SGND pin 18 with short tracks to prevent pickup of disturbances by an external field. Although less critical, a similar construction can be used for RFMAX.



## 11.2 Starting/debugging partial circuits

When starting a newly built application for the first time or when an error is observed during operation, it is possible to activate circuit parts step by step. This enables errors to be located more easily and an evaluation can be performed under conditions that restrict the influences from other circuit parts.

The following provides a step-by-step sequence for debugging:

1. HBC only, with protection disabled
2. HBC only, with protection disabled and variable DC input voltage
3. HBC only, with protection enabled
4. PFC only
5. PFC + HBC complete application

The best approach is to check the HBC converter first and then the PFC converter.

### 11.2.1 HBC only

[Figure 59](#) shows a suggestion for the setup (temporary additions to the existing application to force operation) and the sequence for disabling/enabling the different functions. A moderate (current) load can be applied to the converters output to ascertain the correct functioning.

**Remark:** A latching, overvoltage detection on SNSOUT ( $> 3.5$  V), can still prevent operation.

CFMIN, GATELS, GATEHS and HB can be monitored to continuously assess the functioning of the converter/controller.

When the PFC function is disabled,  $V_{\text{BOOST}}$  can often be applied by simply applying a DC or AC voltage to the mains input connections.

Check the regulation by increasing the input voltage  $V_{\text{BOOST}}$  for the following situations in the sequence given:

1. Initially at  $V_{\text{BOOST}} = 0$  V: the running frequency is low with a short on-time and a long off-time. This is due to the HB detection not working properly at low voltage and the internal slope detection (HB) not detecting a proper (fast) slope. In this situation a quick check of the working of the PFC can be done by lowering the external supply voltage of 2.7 V on SNSMAINS and SNSBOOST to a value below 2.5 V. This allows the gate-drive pulses on GATEPFC to be seen. By varying the voltage, changes are shown in on-time. After this check, revert the voltage to 2.7 V to continue the HBC-only start-up (see [Section 11.2.2.1](#)).
2. Increasing the value of  $V_{\text{BOOST}}$  at a certain input voltage the HB detection works correctly and the frequency to drive maximum power is minimal. If the HB slope remains slow, the output current is probably low. Increasing the output current probably results in proper HB switching.
3. When the  $V_{\text{BOOST}}$  input voltage has reached a level closer to the nominal working voltage, the correct output voltage is reached (depending on the output load), and regulation starts working. This results in increasing the frequency with increasing the input voltage until the nominal working voltage of  $V_{\text{BOOST}}$  is set.
4. When the basic functioning of the HBC, including SNSFB regulation, is working well, protection can be added one by one. Proper functioning or a need for change can be evaluated.
5. When a self-supplying application is used, the external supply voltage can be removed when the system works well at nominal  $V_{\text{BOOST}}$  voltage. The system can now start with the internal high voltage start-up supply and an auxiliary winding can take over the SUPIC supply.

**Remark:** If, during debugging or starting, a protection has been activated, switching the SUPIC supply off and on to reset a latched protection state can be required.



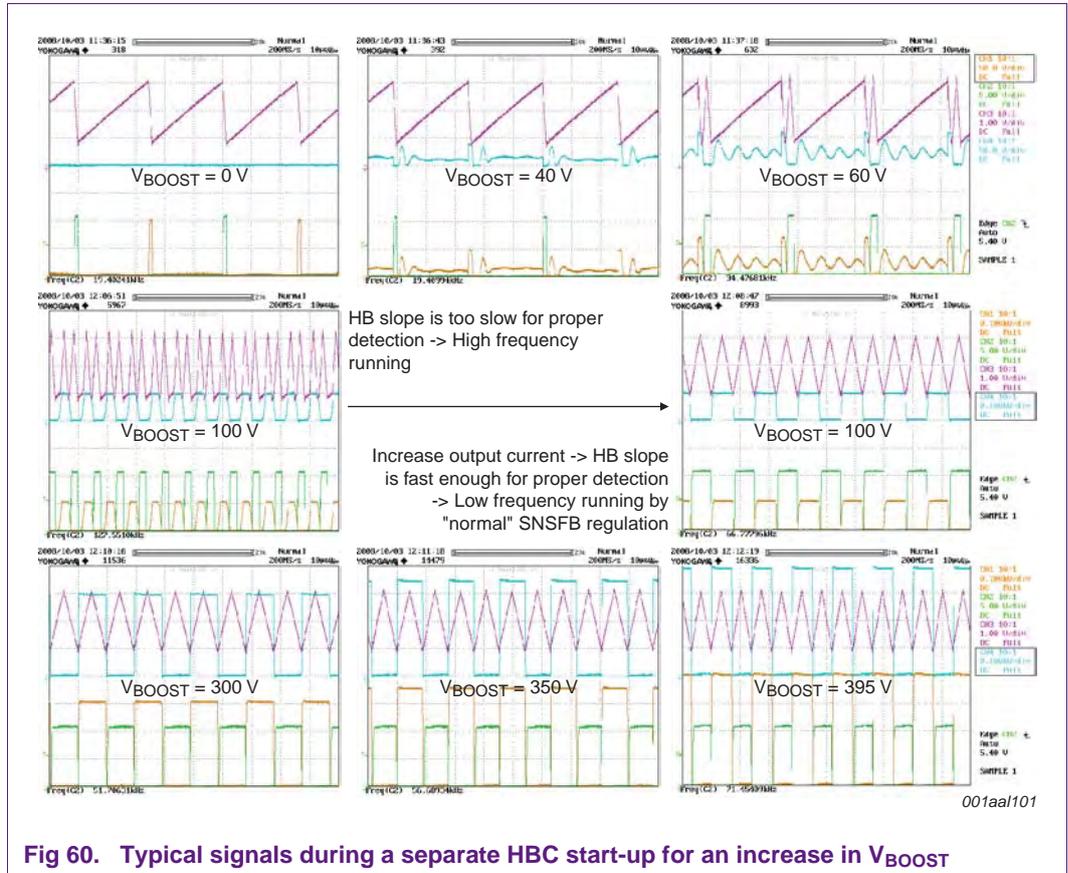


Fig 60. Typical signals during a separate HBC start-up for an increase in VBOOST

The following list provides an association between pins and the protection states for which they are being monitored:

- SSHBC/EN:
 

When the TEA1713 lowers the voltage to this pin, it indicates a protection with correction to high frequency.
- RFMAX:
 

The voltage level on RFMAX indicates the oscillator frequency, which can cause a high frequency protection.
- CFMIN:
 

A (partially) slow oscillator signal cannot observe proper detection of HB slope or a possible Capacitive mode detection.
- PGND and SGND:
 

If the TEA1713 detects HB operation while there is zero input voltage, it indicates that the connection between these pins at the IC is not present. Gate currents lead to false HB-slope detection.
- SNSCURHBC:
 


Any disturbances on this pin (voltage spikes) can lead to an increase of frequency while the original measurement voltage/signal is OK.

- **SNSOUT:**  
The voltage on this pin must be between 2.35 V and 3.5 V for normal operation. A voltage can be forced on pin SNSOUT to avoid protection. But it is often related (by a resistive divider) to the SUPIC and is correct when SUPIC is supplied externally.
- **RCPROT:**  
Several protection functions charges the timer.

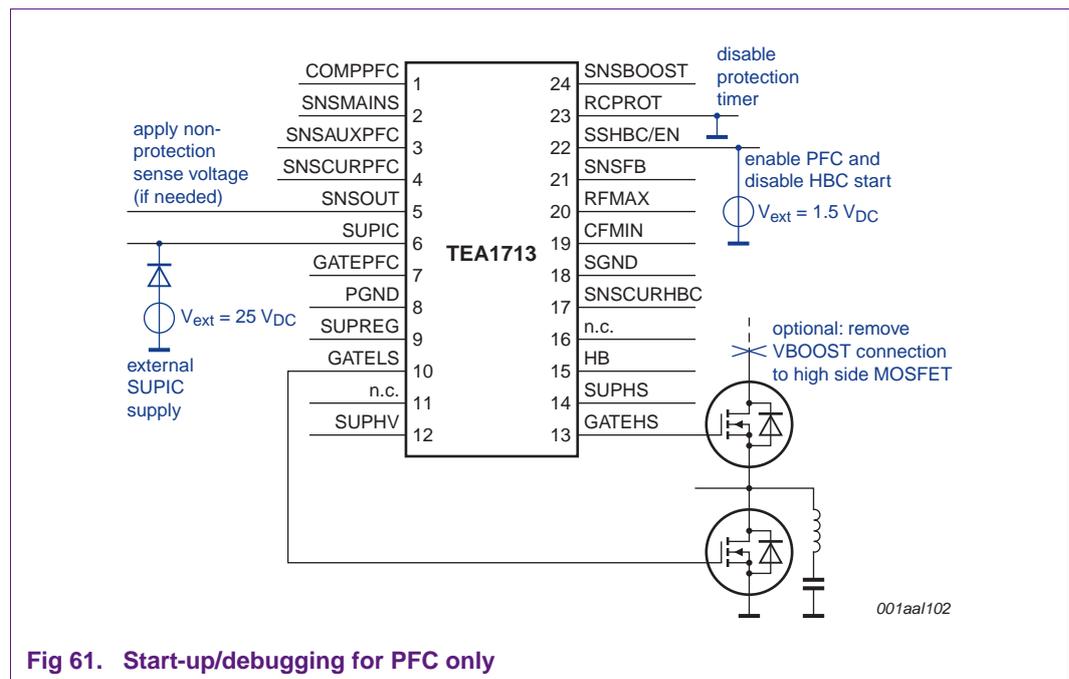**11.2.2 PFC only**

Keeping SSHBC/EN below or forcing it to drop below 2.2 V can disable the HBC function. A voltage higher than 1.2 V can enable the PFC function. Applying an additional voltage (from an external supply) of approximately 1.5 V on SSHBC/EN enables PFC only operation.

The setup is similar to the HBC only operation setup, but for extra safety, the  $V_{BOOST}$  connection to the high side switch of the HBC can be disconnected. In addition, a small load can be connected on  $V_{BOOST}$  to prevent voltage overshoot and control the output power capability.



**11.2.2.1 Operational check without mains voltage**

Without mains input voltage, by lowering the (external) voltage on SNSMAINS and SNSBOOST to below 2.5 V, drive pulses can be observed on GATEPFC. Lower voltages lead to a longer on-time. Below 0.89 V, pulses stop because of SNSMAINS undervoltage protection and restarts when the level increases above 1.15 V.

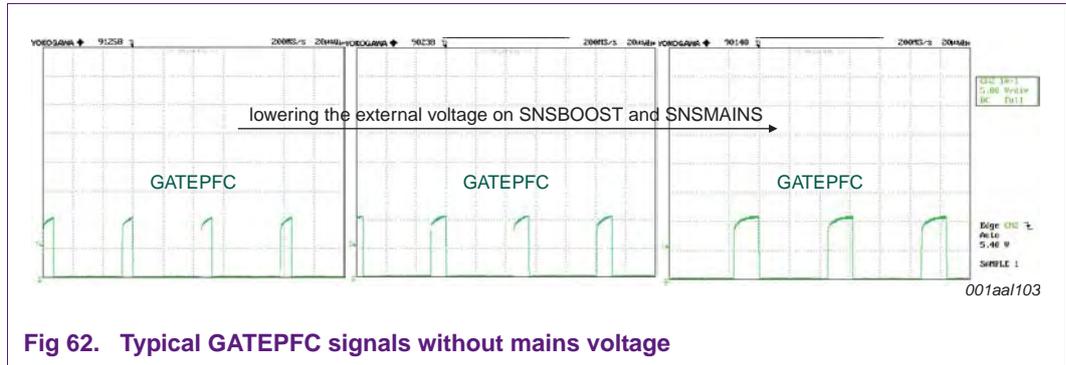


Fig 62. Typical GATEPFC signals without mains voltage

11.2.2.2 Operational check with mains voltage

There is no simple step by step method of gradually increasing the mains voltage to start PFC operation. So full mains voltage is applied to check PFC functionality. While doing this, remove any external voltage source on SNSMAINS and SNSBOOST.

If a problem is expected of an output voltage that can be too high, the output measurement resistor from SNSBOOST to ground can be (temporarily) increased in value. This leads to a lower output voltage regulation setting.

Supply a DC voltage to the mains input instead of the usual AC voltage to be able to observe proper PFC operation more easily with an oscilloscope. This results in more stable signals for evaluation.

11.2.3 HBC and PFC operation

When both converters work properly independently, they can be checked working simultaneously. Remove the additions used for start-up and debugging.

**Remark:** A (normal) ripple voltage on  $V_{BOOST}$  results in some continuous frequency variations in the HBC for compensation. At high output power, the voltage ripple on  $V_{BOOST}$  is larger.

## 12. Application examples and topologies

---

### 12.1 Examples of IC evaluation and test setup

Examples of a test/evaluation setup are provided in [Figure 63](#) and [Figure 64](#). This setup can be used to:

- Check if an IC is still functional (not defect).
- Evaluate specific IC function(s) or pin properties with limited interference from the total system.





## 12.2 Example of a 250 W LCD TV application



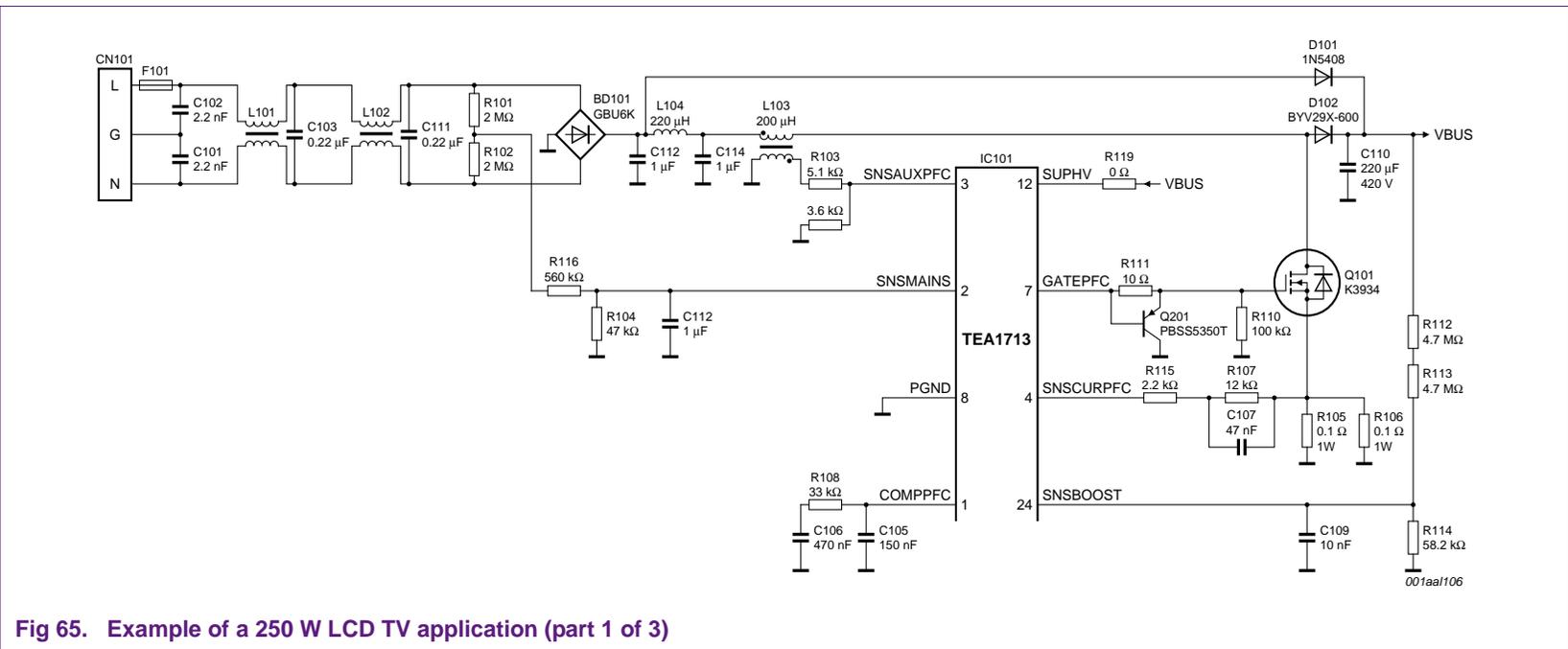


Fig 65. Example of a 250 W LCD TV application (part 1 of 3)

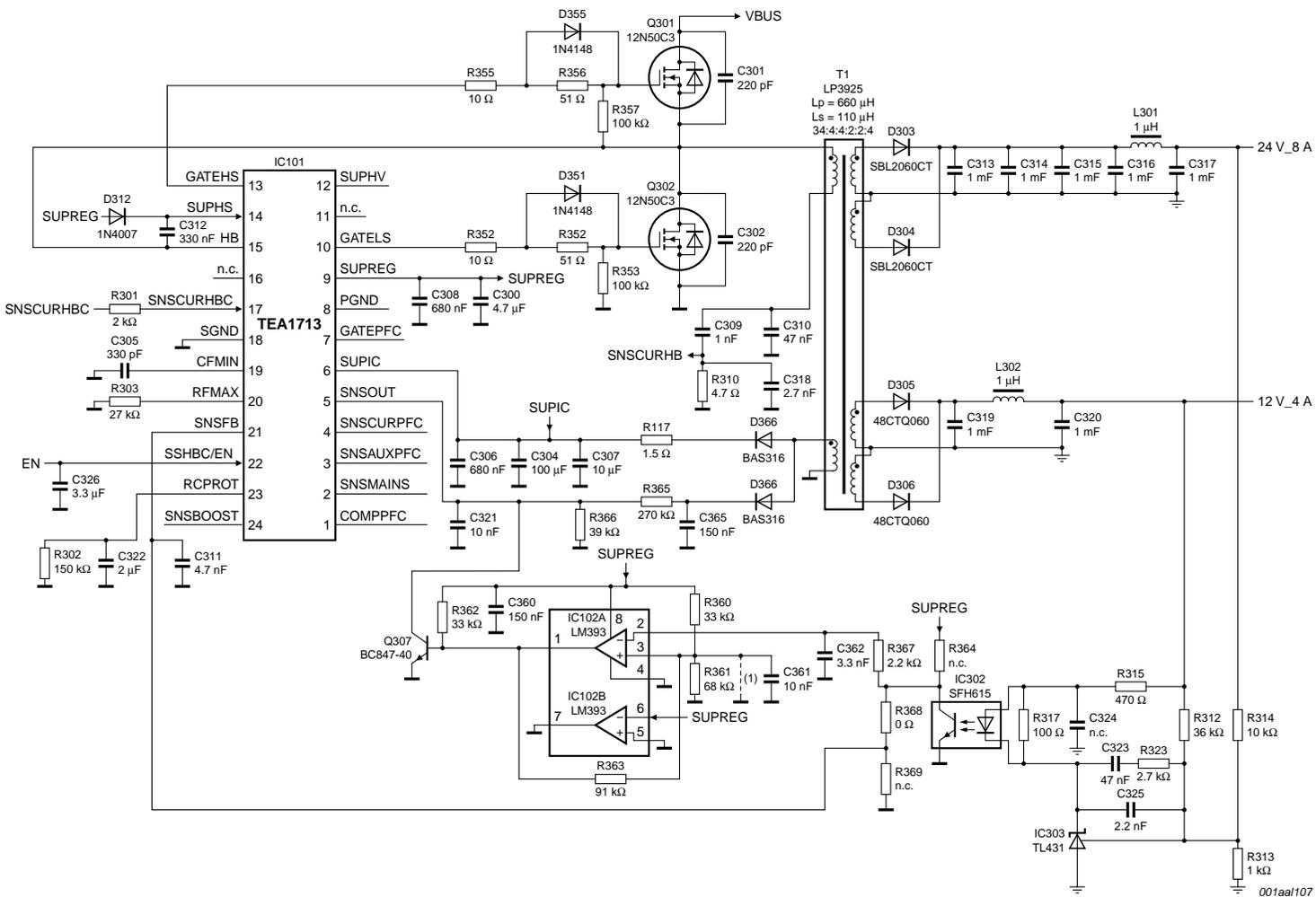

(1) Remove to enable Burst mode operation

Fig 66. Example of a 250 W LCD TV application (part 2 of 3)

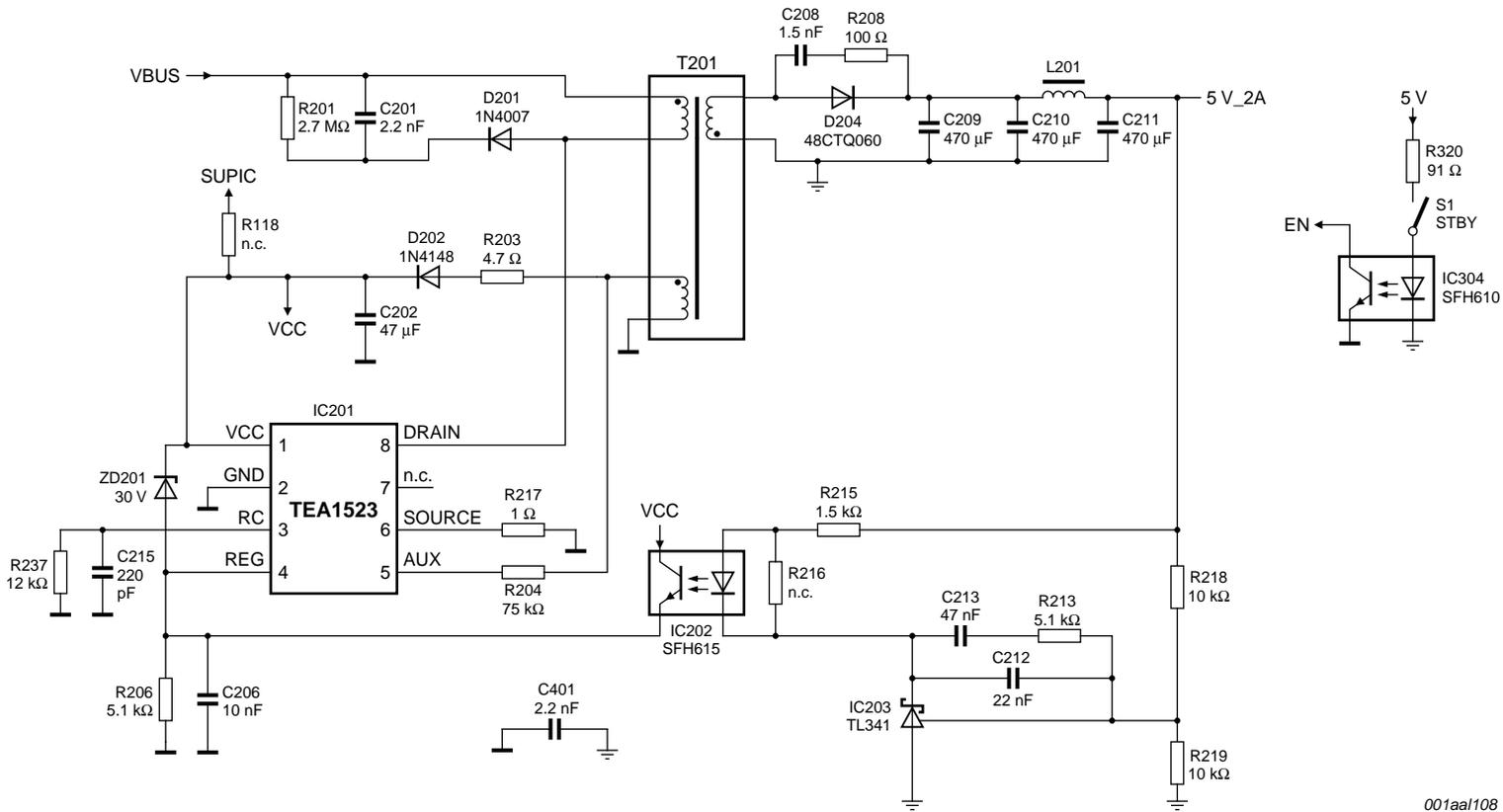

001aa1108

Fig 67. Example of a 250 W LCD TV application (part 3 of 3)

12.3 Example of a 90 W notebook adapter application

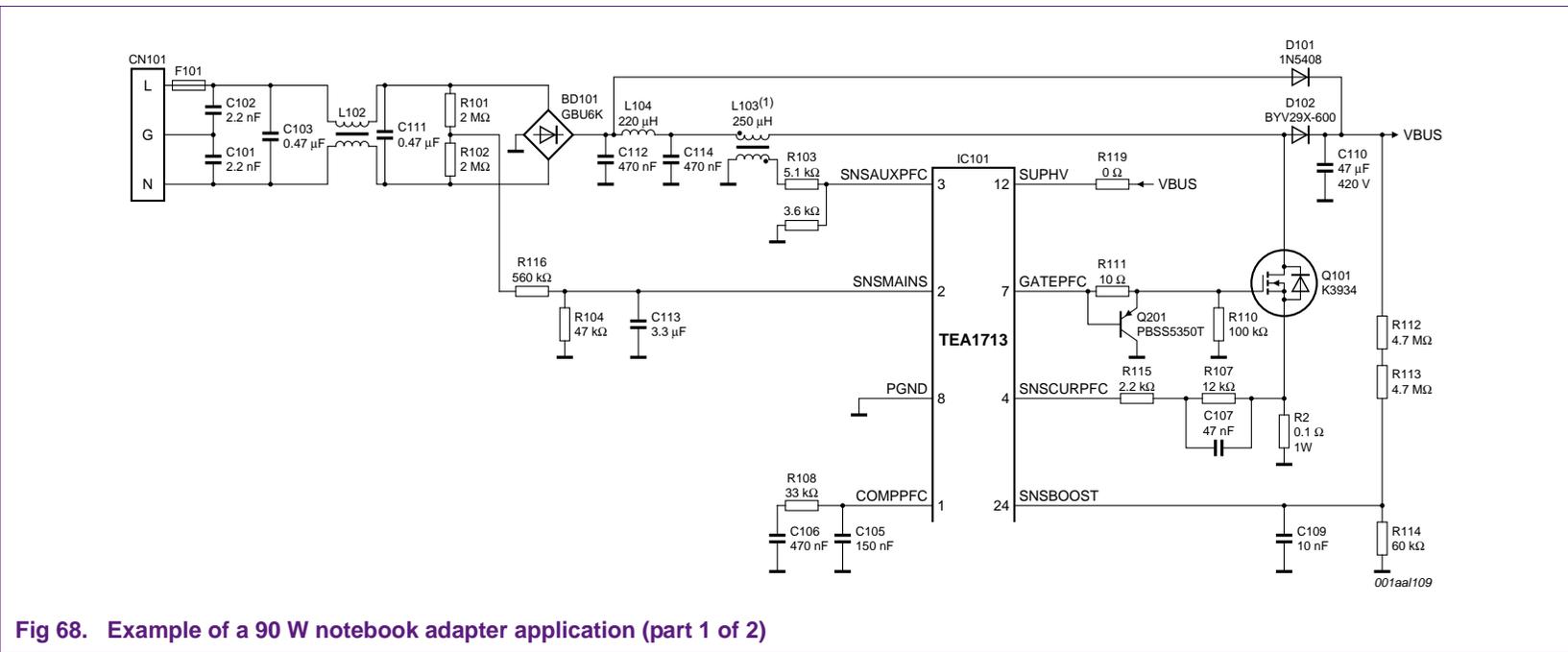


Fig 68. Example of a 90 W notebook adapter application (part 1 of 2)

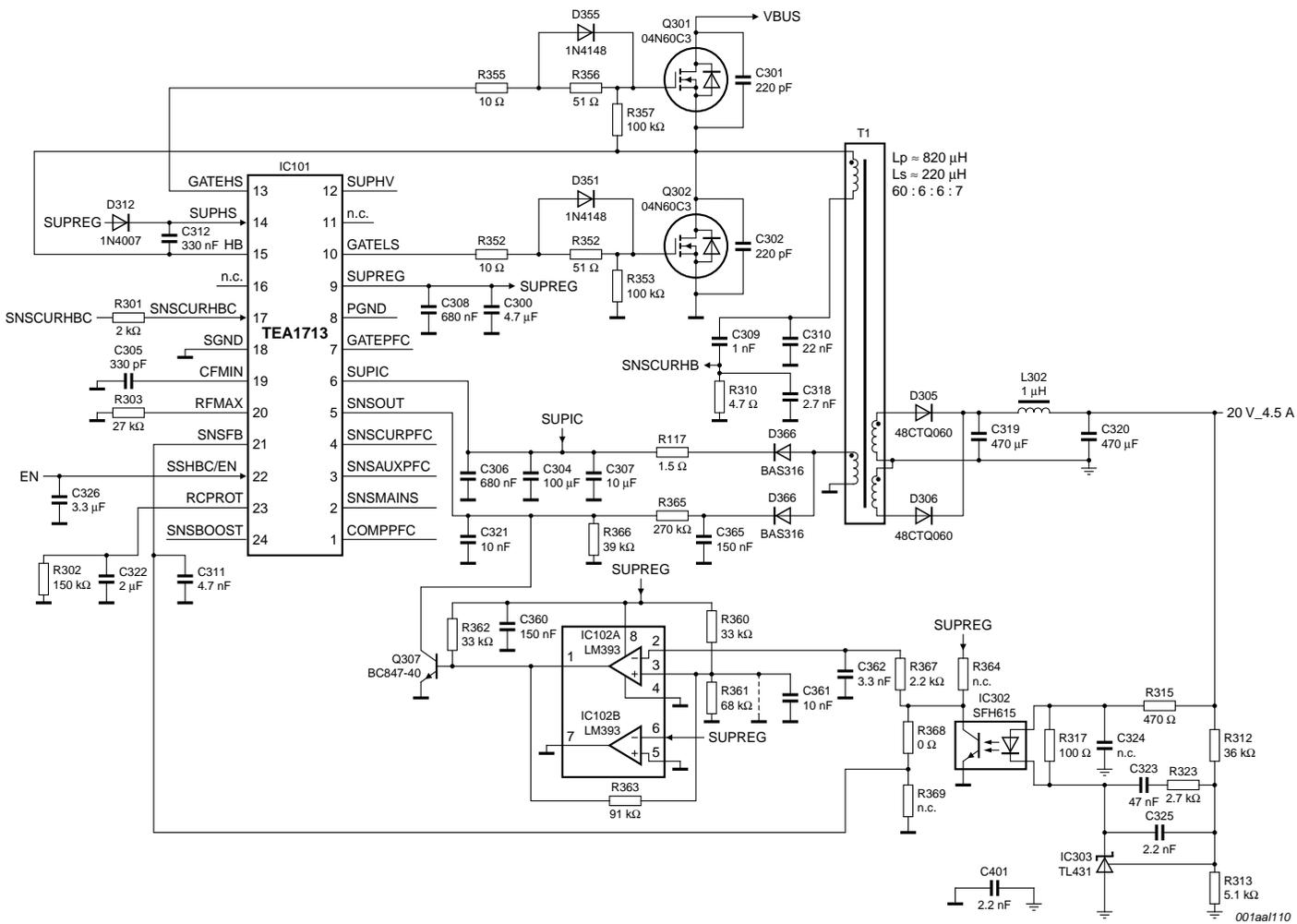


Fig 69. Example of a 90 W notebook adapter application (part 2 of 2)

### 13. Differences between TEA1713T and TEA1713LT

It is often required for stand-alone, single output power supplies like adapters, to have an extended amount of protections leading to a latched protection instead of a safe restart. For this reason the TEA1713LT product version was derived from the TEA1713T.

The functional differences in the TEA1713LT are:

- **SNSOUT UVP (pin 5):**  
In the TEA1713LT the UVP function on pin SNSOUT is disabled because the function is often not required. Disabling the UVP function provides more design flexibility and prevent false triggering.
- **SNSFB OLP-HBC (pin 21):**  
In the TEA1713LT the open-loop protection on SNSFB leads to a latched protection after the protection timer (RCPROT) has triggered the protection. In the TEA1713T the system continues with a safe restart.
- **RFMAX HFP-HBC (pin 20):**  
In the TEA1713LT the high frequency protection on RFMAX leads to a latched protection after the protection timer (RCPROT) has triggered the protection. In the TEA1713T the system continues with a safe restart.
- **SNSCURHBC OCR-HBC (pin 17):**  
In the TEA1713LT the overcurrent regulation on SNSCURHBC leads to a latched protection after the protection timer (RCPROT) has triggered the protection. In the TEA1713T the system continues with a safe restart.  
The OCP increases the frequency during the period until the protection timer is finished. This procedure is the same for TEA1713LT and TEA1713T
- **SNSCURHBC OCP-HBC (pin 17):**  
In the TEA1713LT version the overcurrent protection function on SNSCURHBC is disabled because the OCR is a latched protection. Disabling the OCP function provides more design flexibility and prevents false triggering.

## 14. Abbreviations

**Table 5. Abbreviations**

Acronym	Description
ADT	Adaptive Dead Time
BCD	Bipolar CMOS DMOS
CMR	Common Mode Rejection
EMC	ElectroMagnetic Compatibility
EMI	ElectroMagnetic Interference (or Immunity)
HB	Half-Bridge
HBC	Half-Bridge Converter (or Controller)
HFP	High-Frequency Protection
HV	High-Voltage
IC	Integrated Circuit
LCD	Liquid Crystal Display
LLC	Resonant tank or Converter ( $L_m + L_r + C_r$ in series)
OCP	OverCurrent Protection
OCR	OverCurrent Regulation
OLP	Open-Loop Protection
OPTO	Opto coupler
OTP	OverTemperature Protection
OVP	OverVoltage Protection
PCB	Printed-Circuit Board
PFC	Power Factor Converter/Controller/Correction
PWM	Pulse Width Modulation
SCP	Short Circuit Protection
SOI	Silicon-On-Insulator
UVP	UnderVoltage Protection

## 15. Legal information

### 15.1 Definitions

**Draft** — The document is a draft version only. The content is still under internal review and subject to formal approval, which may result in modifications or additions. NXP Semiconductors does not give any representations or warranties as to the accuracy or completeness of information included herein and shall have no liability for the consequences of use of such information.

### 15.2 Disclaimers

**Limited warranty and liability** — Information in this document is believed to be accurate and reliable. However, NXP Semiconductors does not give any representations or warranties, expressed or implied, as to the accuracy or completeness of such information and shall have no liability for the consequences of use of such information.

In no event shall NXP Semiconductors be liable for any indirect, incidental, punitive, special or consequential damages (including - without limitation - lost profits, lost savings, business interruption, costs related to the removal or replacement of any products or rework charges) whether or not such damages are based on tort (including negligence), warranty, breach of contract or any other legal theory.

Notwithstanding any damages that customer might incur for any reason whatsoever, NXP Semiconductors' aggregate and cumulative liability towards customer for the products described herein shall be limited in accordance with the *Terms and conditions of commercial sale* of NXP Semiconductors.

**Right to make changes** — NXP Semiconductors reserves the right to make changes to information published in this document, including without limitation specifications and product descriptions, at any time and without notice. This document supersedes and replaces all information supplied prior to the publication hereof.

**Suitability for use** — NXP Semiconductors products are not designed, authorized or warranted to be suitable for use in life support, life-critical or safety-critical systems or equipment, nor in applications where failure or malfunction of an NXP Semiconductors product can reasonably be expected to result in personal injury, death or severe property or environmental damage. NXP Semiconductors accepts no liability for inclusion and/or use of NXP Semiconductors products in such equipment or applications and therefore such inclusion and/or use is at the customer's own risk.

**Applications** — Applications that are described herein for any of these products are for illustrative purposes only. NXP Semiconductors makes no representation or warranty that such applications will be suitable for the specified use without further testing or modification.

Customers are responsible for the design and operation of their applications and products using NXP Semiconductors products, and NXP Semiconductors accepts no liability for any assistance with applications or customer product

design. It is customer's sole responsibility to determine whether the NXP Semiconductors product is suitable and fit for the customer's applications and products planned, as well as for the planned application and use of customer's third party customer(s). Customers should provide appropriate design and operating safeguards to minimize the risks associated with their applications and products.

NXP Semiconductors does not accept any liability related to any default, damage, costs or problem which is based on any weakness or default in the customer's applications or products, or the application or use by customer's third party customer(s). Customer is responsible for doing all necessary testing for the customer's applications and products using NXP Semiconductors products in order to avoid a default of the applications and the products or of the application or use by customer's third party customer(s). NXP does not accept any liability in this respect.

**Export control** — This document as well as the item(s) described herein may be subject to export control regulations. Export might require a prior authorization from competent authorities.

**Evaluation products** — This product is provided on an "as is" and "with all faults" basis for evaluation purposes only. NXP Semiconductors, its affiliates and their suppliers expressly disclaim all warranties, whether express, implied or statutory, including but not limited to the implied warranties of non-infringement, merchantability and fitness for a particular purpose. The entire risk as to the quality, or arising out of the use or performance, of this product remains with customer.

In no event shall NXP Semiconductors, its affiliates or their suppliers be liable to customer for any special, indirect, consequential, punitive or incidental damages (including without limitation damages for loss of business, business interruption, loss of use, loss of data or information, and the like) arising out of the use of or inability to use the product, whether or not based on tort (including negligence), strict liability, breach of contract, breach of warranty or any other theory, even if advised of the possibility of such damages.

Notwithstanding any damages that customer might incur for any reason whatsoever (including without limitation, all damages referenced above and all direct or general damages), the entire liability of NXP Semiconductors, its affiliates and their suppliers and customer's exclusive remedy for all of the foregoing shall be limited to actual damages incurred by customer based on reasonable reliance up to the greater of the amount actually paid by customer for the product or five dollars (US\$5.00). The foregoing limitations, exclusions and disclaimers shall apply to the maximum extent permitted by applicable law, even if any remedy fails of its essential purpose.

### 15.3 Trademarks

Notice: All referenced brands, product names, service names and trademarks are the property of their respective owners.

16. Contents

<b>1</b>	<b>Introduction</b>	<b>3</b>	5.5.4	Supply voltage for the output drivers: SUPHS	25
1.1	Scope and setup	3	5.5.4.1	Initial charging of SUPHS	25
1.2	Related documents	4	5.5.4.2	Current load on SUPHS	25
<b>2</b>	<b>TEA1713 highlights and features</b>	<b>5</b>	5.5.4.3	Lower voltage on SUPHS	26
2.1	Resonant conversion	5	5.5.5	SUPREG power consumed by MOSFET drivers	26
2.2	Power factor correction conversion	5	5.5.5.1	GATELS and GATEHS (driving a total of two MOSFETs)	26
2.3	TEA1713 resonant power supply control IC with PFC	6	5.5.5.2	GATEPFC	27
2.4	Features	6	5.5.6	SUPREG supply voltage for other circuits	27
2.4.1	General features	6	5.5.6.1	Current available for supplying an external circuit from SUPREG	27
2.4.2	Power factor controller features	7	5.5.6.2	An estimation by measurement	27
2.4.3	Resonant half-bridge controller features	7	5.6	Value of the capacitors on SUPIC, SUPREG and SUPHS	28
2.4.4	Protection features	7	5.6.1	Value of the capacitor on SUPIC	28
2.5	Protection	7	5.6.1.1	General	28
2.6	Typical areas of application	7	5.6.1.2	Start-up	28
<b>3</b>	<b>Pin overview with functional description</b>	<b>8</b>	5.6.1.3	Normal operation	28
<b>4</b>	<b>Application diagram and block diagrams</b>	<b>12</b>	5.6.1.4	Burst mode operation	28
<b>5</b>	<b>Supply functions</b>	<b>16</b>	5.6.2	Value of the capacitor for SUPREG	29
5.1	Basic supply system overview	16	5.6.3	Value of the capacitor for SUPHS	29
5.1.1	TEA1713 supplies	16	<b>6</b>	<b>MOSFET drivers GATEPFC, GATELS and GATEHS</b>	<b>30</b>
5.1.2	Supply monitoring and protection	17	6.1	GATEPFC	30
5.2	SUPIC - the low voltage IC supply	17	6.2	GATELS and GATEHS	30
5.2.1	SUPIC start-up	17	6.3	Supply voltage and power consumption	30
5.2.1.1	SUPHV $\geq 25 V_{max}$	17	6.4	General subjects on MOSFET drivers	31
5.2.1.2	SUPHV not connected/used	17	6.4.1	Switch on	31
5.2.2	SUPIC stop, UVP and SCP	17	6.4.2	Switch off	31
5.2.3	SUPIC current consumption	18	6.5	Specifications	32
5.3	SUPIC supply using HBC transformer auxiliary winding	18	6.6	Mutual disturbance of PFC and HBC	33
5.3.1	Start-up by SUPHV	18	<b>7</b>	<b>PFC functions</b>	<b>34</b>
5.3.2	Block diagram for SUPIC start-up	19	7.1	PFC output power and voltage control	34
5.3.3	Auxiliary winding on the HBC transformer	19	7.2	PFC regulation	35
5.3.3.1	SUPIC and SNSOUT by auxiliary winding	20	7.2.1	Sensing $V_{BOOST}$	35
5.3.3.2	Auxiliary supply voltage variations by output current	20	7.2.2	SNSBOOST open and short circuit pin detection	35
5.3.3.3	Voltage variations by auxiliary winding position: primary side component	20	7.2.3	PFCCOMP in the PFC voltage control loop	36
5.3.4	Difference between UVP on SNSOUT and SNSCURHBC OCP/OCR	21	7.2.4	Mains compensation in the PFC voltage control loop	37
5.4	SUPIC supply by external voltage	22	7.3	PFC demagnetization and valley sensing	37
5.4.1	Start-up	22	7.3.1	PFC auxiliary sensing circuit	38
5.4.2	Stop	22	7.3.2	PFC frequency limit	39
5.5	SUPREG	22	7.4	PFC OverCurrent Regulation/Protection (OCR/OCP)	39
5.5.1	Block diagram of SUPREG regulator	24	7.4.1	PFC soft-start and soft-stop	40
5.5.2	SUPREG during start-up	24			
5.5.3	Supply voltage for the output drivers: SUPREG	24			

continued >>

7.4.1.1	Soft-start . . . . .	40	9.4	Advantages of Burst mode for HBC and PFC simultaneously . . . . .	65
7.4.1.2	Soft-stop . . . . .	40	9.5	Choice of burst level and hysteresis level . . . . .	66
7.4.2	SNSCURPFC open and short protection . . . . .	40	9.6	Output power - operating frequency characteristics . . . . .	67
7.5	PFC boost OverVoltage Protection (OVP) . . . . .	41	9.7	Lower SUPHS in burst . . . . .	68
7.6	PFC mains UnderVoltage Protection (brownout protection) . . . . .	41	9.8	Audible noise . . . . .	68
7.6.1	Undervoltage or brownout protection level . . . . .	42	9.8.1	Measurements in the resonant transformer construction . . . . .	68
7.6.2	Discharging the mains input capacitor . . . . .	42	9.8.2	Burst power-dependent noise level . . . . .	69
7.6.3	SNSMAINS open pin detection . . . . .	43	9.9	PFC converter and resonant converter simultaneous bursting . . . . .	69
<b>8</b>	<b>HBC functions . . . . .</b>	<b>44</b>	9.9.1	PFC output voltage variations . . . . .	70
8.1	HBC UVP boost . . . . .	44	9.9.2	PFC burst duration . . . . .	70
8.2	HBC switch control . . . . .	44	9.9.3	Switching between burst and normal operation . . . . .	70
8.3	HBC adaptive non-overlap . . . . .	44	9.9.4	Audible noise during mode transition . . . . .	70
8.3.1	Inductive mode (normal operation) . . . . .	44	9.10	Design guidelines for Burst mode operation . . . . .	71
8.3.2	Capacitive mode . . . . .	46	9.11	Enable/disable Burst mode . . . . .	71
8.3.3	Capacitive Mode Regulation (CMR) . . . . .	47	9.12	Unused Burst mode . . . . .	71
8.4	HBC oscillator . . . . .	49	<b>10</b>	<b>Protection functions . . . . .</b>	<b>72</b>
8.4.1	Presettings . . . . .	49	10.1	Protection overview . . . . .	72
8.4.2	Operational control . . . . .	49	10.2	IC protection . . . . .	72
8.4.3	CFMIN and RFMAX . . . . .	50	10.2.1	OverTemperature Protection (OTP) . . . . .	72
8.4.3.1	Minimum frequency setting for CFMIN . . . . .	50	10.2.2	Latched protection . . . . .	72
8.4.3.2	Maximum frequency setting for RFMAX . . . . .	51	10.2.2.1	Resetting a latched protection shutdown state . . . . .	73
8.4.4	RFMAX and High Frequency Protection (HFP) . . . . .	51	10.3	SNSOUT protection . . . . .	73
8.5	HBC feedback (SNSFB) . . . . .	52	10.3.1	OverVoltage Protection (OVP) output . . . . .	74
8.5.1	HBC Open-Loop Protection (OLP) . . . . .	53	10.3.1.1	Auxiliary winding . . . . .	74
8.6	SSHBC/EN soft-start and enable . . . . .	54	10.3.1.2	Principle of operation . . . . .	74
8.6.1	Switching ON and OFF using an external control function . . . . .	54	10.3.1.3	Connecting external measurement circuits . . . . .	74
8.6.1.1	Switching ON and OFF using SSHBC/EN . . . . .	55	10.3.2	UnderVoltage Protection (UVP) output . . . . .	74
8.6.1.2	Hold and continue . . . . .	55	10.3.2.1	Auxiliary winding . . . . .	74
8.6.2	Soft-start HBC . . . . .	55	10.3.2.2	Principle of operation . . . . .	74
8.6.2.1	Soft-start voltage levels . . . . .	56	10.3.2.3	Severe voltage drop . . . . .	75
8.6.2.2	SSHBC/EN charge and discharge . . . . .	56	10.3.2.4	Connecting external measurement circuits . . . . .	75
8.6.2.3	SNSFB, SSHBC/EN and soft-start reset - operating frequency control . . . . .	58	10.3.3	OVP and UVP combinations . . . . .	75
8.6.2.4	Soft-start reset . . . . .	58	10.3.3.1	Circuit configurations . . . . .	75
8.7	HBC overcurrent protection and regulation . . . . .	59	10.3.3.2	OVP functional and UVP disabled . . . . .	75
8.7.1	HBC overcurrent regulation . . . . .	59	10.3.3.3	UVP functional and OVP disabled . . . . .	76
8.7.1.1	Start-up . . . . .	60	10.3.3.4	Both OVP and UVP disabled . . . . .	77
8.7.2	HBC overcurrent protection . . . . .	60	10.4	Protection timer . . . . .	78
8.7.3	SNSCURHBC boost voltage compensation . . . . .	60	10.4.1	Block diagram of the RCROT function . . . . .	78
8.7.4	Current measurement circuits . . . . .	61	10.4.2	RCROT working as protection timer . . . . .	78
8.7.5	SNSCURHBC layout . . . . .	61	10.4.3	RCROT working as a restart timer . . . . .	79
<b>9</b>	<b>Burst mode operation . . . . .</b>	<b>62</b>	10.4.4	Dimensioning the timer function . . . . .	80
9.1	Burst mode controlled by SNSOUT . . . . .	62	<b>11</b>	<b>Miscellaneous advice and tips . . . . .</b>	<b>81</b>
9.2	External comparator for Burst mode implementation . . . . .	63	11.1	PCB layout . . . . .	81
9.3	Advantages of Burst mode for HBC . . . . .	64	11.1.1	General setup . . . . .	81

continued &gt;&gt;

11.1.2	Grounding . . . . .	81
11.1.3	Current loops . . . . .	81
11.1.4	Grounding layout example . . . . .	82
11.1.5	Miscellaneous . . . . .	82
11.1.5.1	Connecting SNSCURHBC (pin 17) . . . . .	82
11.1.5.2	CFMIN (pin 19) and RFMAX (pin 20) . . . . .	82
11.2	Starting/debugging partial circuits . . . . .	83
11.2.1	HBC only . . . . .	84
11.2.2	PFC only . . . . .	87
11.2.2.1	Operational check without mains voltage . . . . .	87
11.2.2.2	Operational check with mains voltage . . . . .	88
11.2.3	HBC and PFC operation . . . . .	88
<b>12</b>	<b>Application examples and topologies . . . . .</b>	<b>89</b>
12.1	Examples of IC evaluation and test setup . . . . .	89
12.2	Example of a 250 W LCD TV application . . . . .	92
12.3	Example of a 90 W notebook adapter application . . . . .	95
<b>13</b>	<b>Differences between TEA1713T and TEA1713LT . . . . .</b>	<b>97</b>
<b>14</b>	<b>Abbreviations . . . . .</b>	<b>98</b>
<b>15</b>	<b>Legal information . . . . .</b>	<b>99</b>
15.1	Definitions . . . . .	99
15.2	Disclaimers . . . . .	99
15.3	Trademarks . . . . .	99
<b>16</b>	<b>Contents . . . . .</b>	<b>100</b>

Please be aware that important notices concerning this document and the product(s) described herein, have been included in section 'Legal information'.

© NXP B.V. 2011.

All rights reserved.

For more information, please visit: <http://www.nxp.com>

For sales office addresses, please send an email to: [salesaddresses@nxp.com](mailto:salesaddresses@nxp.com)

Date of release: 26 September 2011

Document identifier: AN10881